

Module - 2

Mohd. Irfan.

1) State Kirchoff's Law.

There are basically two laws under Kirchoff's Law.

→ Kirchoff's Current Law (Kirchoff's 1st law):-

KCL states that the total current in a closed circuit, the entering current at a node is equal to the current leaving at the node or the algebraic sum of current at node in an electronic circuit is equal to zero.

→ Kirchoff's Voltage Law (Kirchoff's 2nd Law).-

KVL states that, the algebraic sum of the voltage in a closed circuit is equal to zero or the net algebraic sum of voltage at node is equal to zero. Hence the sum of the voltage difference across all the elements in a circuit is always zero.

2) Calculate eq. resistance of circuit if applied voltage is 23V and current flowing through circuit is 4A, receiving power of 92W.

Given power = 92W

$$\text{Voltage} = 23V$$

$$\text{current} = 4A.$$

so to find out resistance we need to apply ohm's law.

$$\text{Power} = \text{Voltage} \times \text{Current}$$

$$92 = 23 \times 4$$

$$92 = R$$

Ohm's law states that the current through a conductor between two points is directly proportional to the potential diff across those two points. Introducing the concept of proportionality, the resistance, one arrives at the mathematical equation $\bullet I = V/R$.

According to Ohm's law:- $I = \frac{V}{R}$, $\rightarrow ①$

substituting the value of $I \& V$ in ①.

$$4 = \frac{23}{R}, \text{ so } R = \frac{23}{4} = 5.75 \Omega$$

3) If charge developed between two plates is 2C and capacitance is $4.5\mu F$, determine the voltage applied to the plates.

$$\text{Given, } Q = 2C$$

charge

$$C [\text{capacitance}] = 4.5 \times 10^{-6} F. \quad [1\mu = 10^{-6}]$$

We know that charge stored a supply voltage in a capacitor.

$$Q \propto V$$

$$Q = CV \rightarrow ②$$

substitute value of $Q \& C$ in ②

$$2 = 4.5 \times 10^{-6} \times V$$

$$V = \frac{2}{4.5 \times 10^{-6}} \text{ volts.}$$

$$V = \frac{2 \times 10^6}{45} \text{ volts}$$

$$\frac{2 \times 10^6}{45} \text{ volts} = 0.044 \times 10^7 \text{ volts.}$$

$$= 4.4 \times 10^5 \text{ Volts.}$$

4) If three capacitors are connected in series which are $2F$, $3F$ and $6F$. Calculate eqⁿ capacitance.

When the capacitors are connected in series.

The expression to equivalence capacitance is given as follows.

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots - \frac{1}{C_n} \rightarrow ①$$

Here, $n=3$ so

$$eq \Rightarrow \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \rightarrow$$

so, substitute value of C_1 , C_2 & C_3 in eq. ①.

Given $C_1 = 2F$

$C_2 = 3F$

$C_3 = 6F$

$$\frac{1}{C_{eq}} = \left[\frac{1}{2} + \frac{1}{3} + \frac{1}{6} \right] \frac{1}{F}$$

$$\frac{1}{C_{eq}} = \frac{3+2+1}{6} = \frac{6}{6} = 1$$

$$C_{eq} = 1F$$

5) If three inductor are in parallel with $20mH$, $25mH$ and $50mH$, then determine the equivalent inductance.

When the inductors are connected in parallel.

The expression to equivalence inductance is given as follows.

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots - \frac{1}{L_n}$$

Here, $n=3$ so the eqⁿ is

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} \rightarrow ①$$

The given inductances are :-

$$L_1 = 20mH$$

$$L_2 = 25mH$$

$$L_3 = 50mH$$

So substitute the values of L_1, L_2, L_3 in eq. ①

$$\frac{1}{L_{eq}} = \left[\frac{1}{20} + \frac{1}{25} + \frac{1}{50} \right] \frac{1}{mH}$$

$$\begin{matrix} 20, 25, 50 \\ 4, 5, 6 \end{matrix}$$

$$\begin{matrix} 2, 5, 3 \\ 5 \times 5 \times 2 \times 2 \times 3 \\ = 300 \end{matrix}$$


$$\frac{1}{L_{eq}} = \left[\frac{15+12+10}{300} \right] \frac{1}{mH}$$

$$\frac{1}{L_{eq}} = \left[\frac{37}{300} \right] \frac{1}{mH}$$

$$L_{eq} = \frac{300}{37} mH = 8.1 mH$$

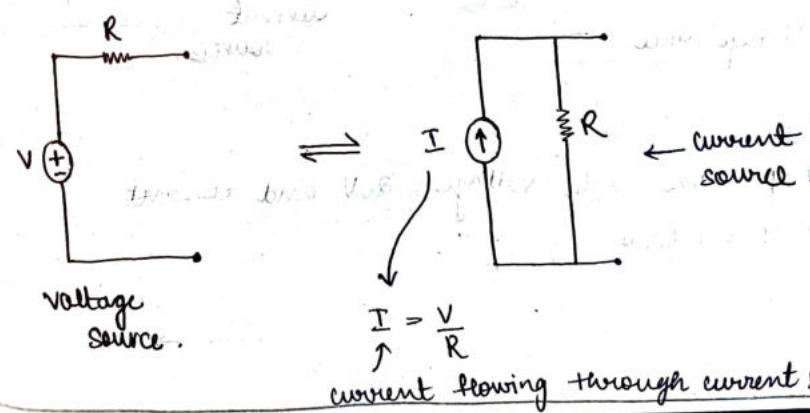
6) Reduce current source from voltage source using source transformation.

source transformation for deducing current source from voltage source is given below.



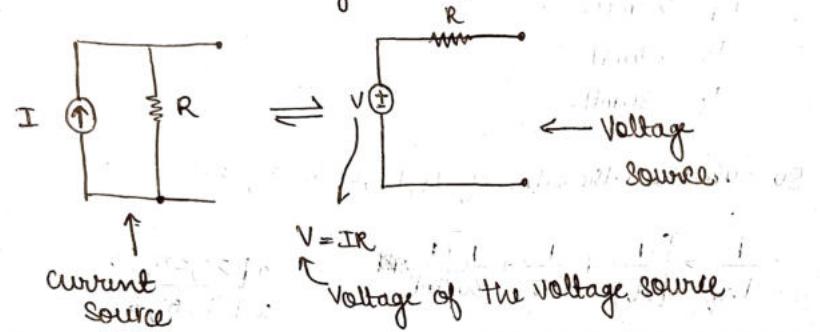7). Deduce voltage source from current source using source transformation.


Source transformation for deducing current voltage source from current source can be given as follows.



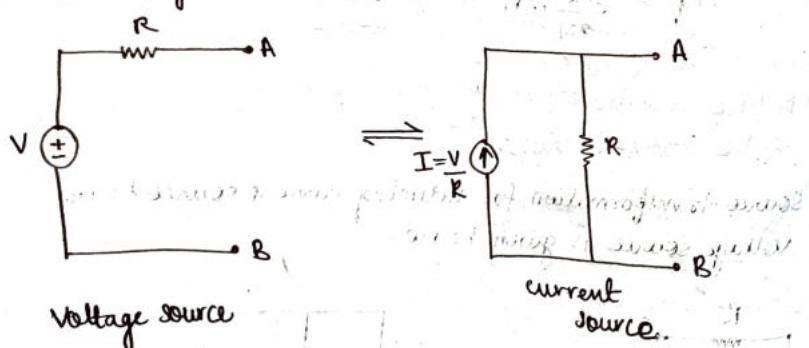8) Across AB terminal, a voltage source of 25V is in series with resistance of 150 ohm resistor, apply source transformation and redraw the circuit diagram across AB terminal.


Ans:-

To convert voltage source to current source, the following source transformation should be done.



Given,

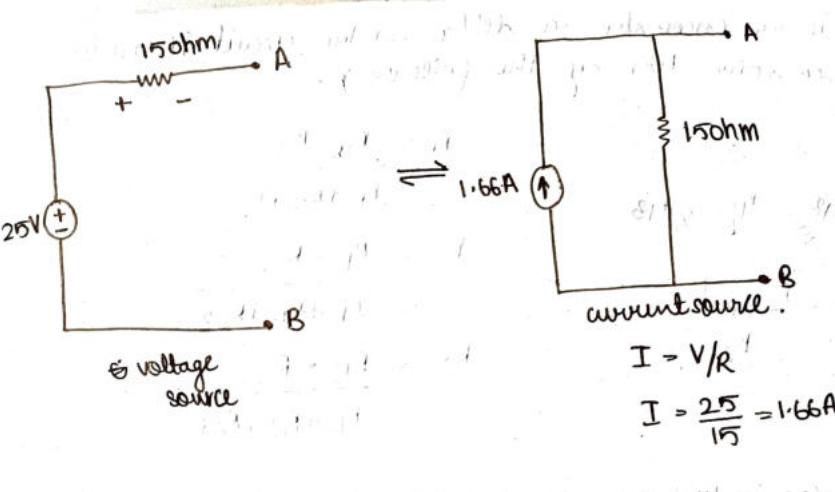Voltage source with voltage = 25V and current resistor = 150ohm





9) Write expression for star delta formation.

Ans:- Whenever we encounter a star formation in the circuit we can do the following transformation

$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

$$R_{13} = R_1 + R_3 + \frac{R_1 R_3}{R_2}$$
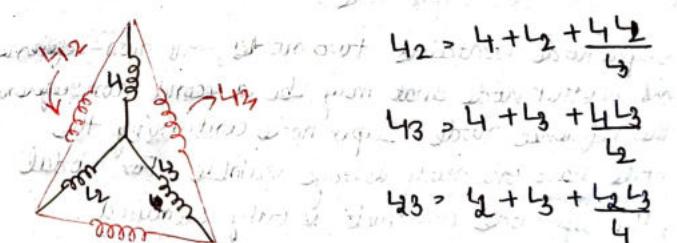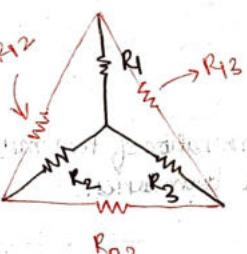
$$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$




$$\frac{1}{L_{12}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_1 L_2}$$

$$\frac{1}{L_{13}} = \frac{1}{L_1} + \frac{1}{L_3} + \frac{1}{L_1 L_3}$$

$$\frac{1}{L_{23}} = \frac{1}{L_2} + \frac{1}{L_3} + \frac{1}{L_2 L_3}$$

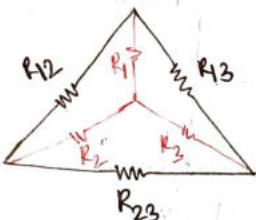(Q9) If we encounter a delta in the circuit it can be solved like by the following-



$$R_1 = \frac{R_{12} \cdot R_{13}}{R_{12} + R_{13} + R_{23}}$$

$$R_2 = \frac{R_{12} \cdot R_{23}}{R_{12} + R_{13} + R_{23}}$$

$$R_3 = \frac{R_{13} \cdot R_{23}}{R_{12} + R_{13} + R_{23}}$$

(Q10) For inductance also its similar to resistor

for conductance in place of R_1, R_2, R_3 we should write

$$\frac{1}{R_1}, \frac{1}{R_2}, \frac{1}{R_3}$$


Please write down the expression for inductor & conductor also in the exam!

(Q11) Define super mesh:

Ans:- Supermesh is defined as the combination of two meshes which have current source on their boundaries.

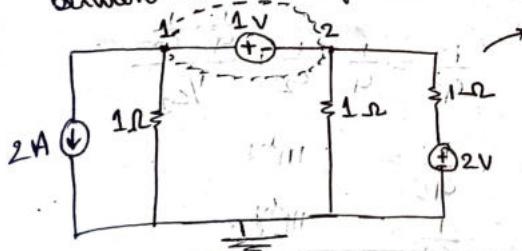(Q12) Give the condition for supernode.

Ans:- Each supernode contains two nodes, one non-reference node and another node that may be a second non-reference node or the reference node. Super node containing the reference node have one node voltage variable. For nodal analysis, the supernode construct is only required between two non-reference nodes.



In the fig as there is a voltage source present between the two non-reference nodes it becomes a SUPERNODE.

(Q13) Limitation of Mesh Analysis:

- We can use this method only when the circuit is planar, otherwise the method is not fully useful.
- If network is large then no. of meshes will be large, hence the no. of equations will be more & it will be inconvenient to use in that case.

(Q14) Limitation of Nodal analysis.

- Only used for analysis of linear elements such as resistors, capacitors and inductors.
- The other limitation is that they assume reference 0Volt that is constantly zero. However, constant zero volt does not always occur especially in long distance transmission line.

(Q15) If three equivalent values of resistors are in delta determine their equivalent values in star connection (Delta to Star).

$$R_{12} = \frac{R_{12} \cdot R_{13}}{R_{12} + R_{13} + R_{23}}$$


$$R_2 = \frac{R_{12} \cdot R_{23}}{R_{12} + R_{13} + R_{23}}$$

$$R_3 = \frac{R_{13} \cdot R_{23}}{R_{12} + R_{13} + R_{23}}$$

$$\text{Since } R_{12} = R_{13} = R_{23} = R$$

$$\text{So, } R_1 = R_2 = R_3 = \frac{R^2}{3R} ; R_2 = \frac{R^2}{3R} ; R_3 = \frac{R^2}{3R}.$$
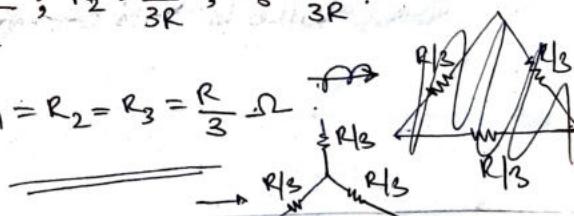
$$\text{So, } R_1 = R_2 = R_3 = \frac{R}{3} \Omega$$



Q16) Define reference node.

Ans:- A reference node is a node created that is also called as the ground node and helps in defining other node voltages with respect to this point. The reference node has a potential of zero. The following symbol indicates the reference node.



Reference node symbol.

Q17) Give difference between nodal analysis & mesh analysis.

Mesh Analysis:- Technique used to solve the complex networks of more no. of meshes. Mesh analysis is nothing but apply KVL to each on every loop in the circuit & solving for mesh currents. By finding the mesh current we can solve any required data of networks.

(with diagram)

Nodal Analysis:- Nodal analysis is a technique used for solving complex networks consisting of more number of nodes. Node analysis is nothing but applying KCL to each and every node in circuit & solving for node voltages. By find node voltage we can solve any required data of the network.

Q18) If three equivalent resistors are in star, then calculate their equivalent values in Delta connection.

PTO.

(star to delta)



$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3} \rightarrow ①$$

$$R_{13} = R_1 + R_3 + \frac{R_1 R_3}{R_2} \rightarrow ②$$

$$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1} \rightarrow ③$$

$$\text{But we know that } R_1 = R_2 = R_3 = R \rightarrow ④$$

Sub ④ in eq ①.


$$R_{12} = R + R + \frac{R^2}{R} = 3R$$

$$R_{13} = R + R + \frac{R^2}{R} = 3R$$

$$R_{23} = R + R + \frac{R^2}{R} = 3R$$

therefore,


$$R_{12} = R_{13} = R_{23} = 3R$$

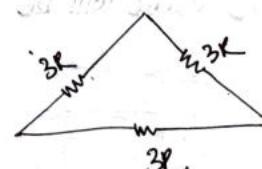

19) If three equal value resistors with $R = 3\Omega$ are in delta ; Determine their eqv equivalent value in star connection.


Ans:- First write 15th question solution i.e., the proof to of delta to star then write the answer below:-

Given

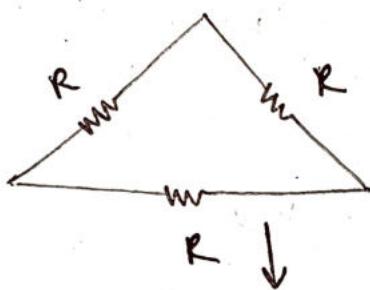


$$R = 3\Omega$$


then,

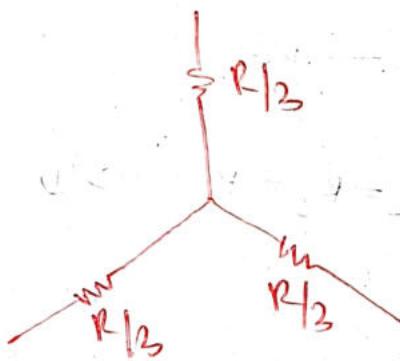

so

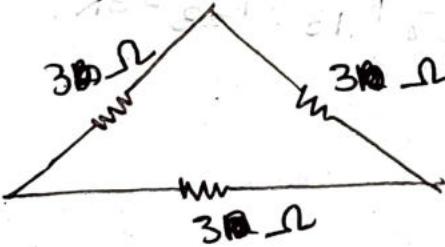


\Rightarrow

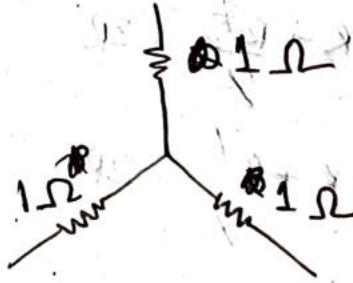

so the equivalence value will be 1 Ω each.

2) Predict in detail the equivalence of resistance of series & parallel circuits respectively & explain with neat example.

Inductors in Parallel :-

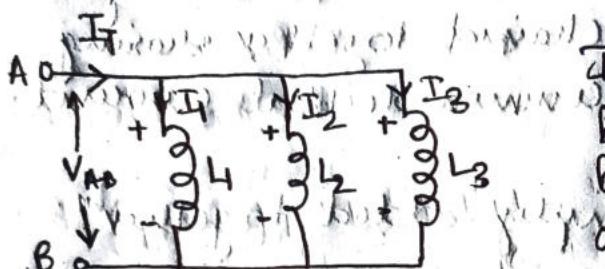

Inductors are said to be in parallel when both of their terminals are respectively connected to reach other terminal of another inductor or inductors.

The voltage drop across all the inductors in parallel will be the same. Then, inductors in parallel have a common voltage across them, V_{AB} , in the example below.

$$V_{L1} = V_{L2} = V_{L3} = V_{AB} \dots \text{etc.}$$

The sum of individual current flowing through each inductor can be found using KCL where $i_T = i_1 + i_2 + i_3$ and self induced emf across an inductor is given as

$$\mathcal{E} = L \frac{di}{dt}$$

Substituting the current $i_1 + i_2 + i_3$ the voltage across the parallel combination is given as -


$$V_{AB} = L_T \frac{d}{dt} (i_1 + i_2 + i_3) = L_T \left[\frac{di_1}{dt} + \frac{di_2}{dt} + \frac{di_3}{dt} \right]$$

Sub $\frac{di}{dt} = \frac{V}{L}$ we get,

$$V_{AB} = L_T \left[\frac{V}{L_1} + \frac{V}{L_2} + \frac{V}{L_3} \right]$$

So the parallel inductor eq' can be given as

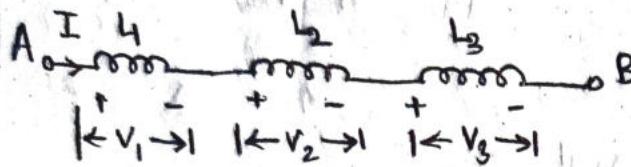
$$\frac{1}{L} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots + \frac{1}{L_n}$$



Inductors can be connected together in series when they are

chained together sharing common electrical current.

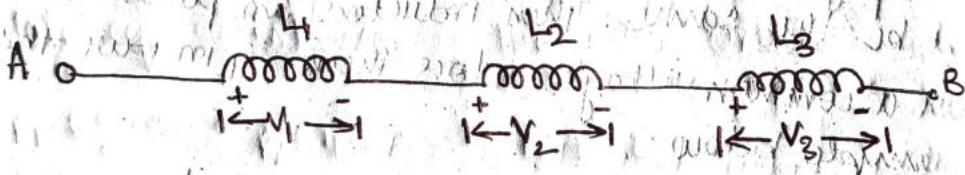Inductors in series are simply "added together" because the no of coil turns is effectively increased, with total current inductance L_T being equal to the sum all individual inductances added together.



Series inductor have common current flowing through them

$$I_{L1} = I_{L2} = I_{L3} = I_{AB} \text{ etc.}$$

The sum of individual voltage drop across each inductor is given as $V_T = V_1 + V_2 + V_3$ by the use of KVL.

The self inductance emf across an inductor is given by $\frac{V}{dt} = L \frac{di}{dt}$.

$$L_T \frac{di}{dt} = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + L_3 \frac{di}{dt} + \dots + L_n \frac{di}{dt}$$

The eq' for series connection can be given as

$$L_T = L_1 + L_2 + L_3 + \dots + L_n$$

3) Estimate the equivalent capacitance of series and parallel connection of capacitors element.


→ SERIES CONNECTION:

The capacitance of a capacitor is given by the relationship of charge and voltage i.e., $Q = CV$ or $C = \frac{Q}{V}$.

for calculation of V we can write $V = \frac{Q}{C}$.

The voltage across individual capacitors will be
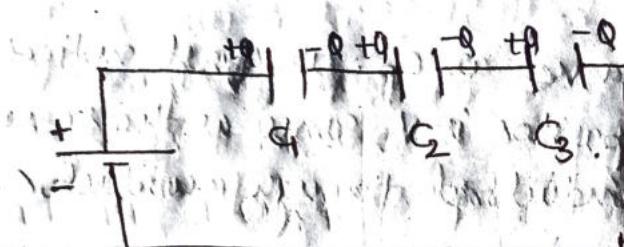
$$V_1 = \frac{Q}{C_1}, V_2 = \frac{Q}{C_2}, V_3 = \frac{Q}{C_3}, \dots \text{so on.}$$



Thus the total is the sum of individual voltages

$$V = V_1 + V_2 + V_3,$$

Taking total capacitance as C_s for series capacitance

consider $V = \frac{Q}{C_s} = V_1 + V_2 + V_3.$

$$V = V_1 + V_2 + V_3. \quad [\because V = \frac{Q}{C_s} \text{ and } V_1 = \frac{Q}{C_1}, V_2 = \frac{Q}{C_2}, V_3 = \frac{Q}{C_3}]$$

$$\frac{Q}{C_s} = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3}$$


taking Q as common on both sides.

$$\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}. \quad \left. \begin{array}{l} \text{Formula for calculating} \\ \text{eq. capacitance for} \\ \text{Capacitors connected in} \\ \text{series.} \end{array} \right\}$$

For n capacitors the total capacitance will be:-

$$\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_n}$$

Parallel Combination:

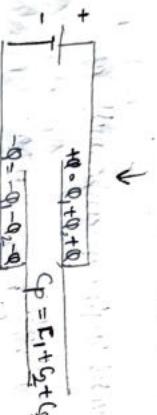

Taking equivalent capacitance as C_p . We first notice that the voltage across each capacitor is same as the source since they are directly connected through a conductor.

Thus capacitors have same effect on them as they would be connected individually to voltage source.

The total charge Q is the sum of individual charges

$$Q = Q_1 + Q_2 + Q_3 \dots$$

Using the ~~for~~ relationship $Q = CV$, we use total charge

$$Q = C_p V, \text{ where } Q_1 = C_1 V; Q_2 = C_2 V; Q_3 = C_3 V.$$

$$Q = C_p V = C_1 V + C_2 V + C_3 V.$$

taking V common \cancel{V} cancelling on both sides



Formula for capacitance for ~~parallel~~ combination of capacitors connected in parallel combination

$$C_p = C_1 + C_2 + C_3 + \dots + C_n$$

For n no. of capacitors connected in series the formula is given but:-

$$C_p = C_1 + C_2 + C_3 + \dots + C_n$$

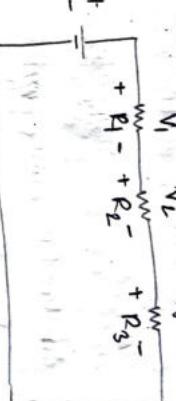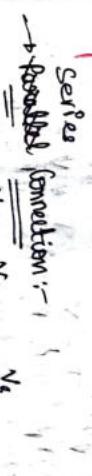- 1) Estimate the equivalent capacitance of resistors in parallel combination.



According to ohm's law, $V = IR$, since energy is conserved the voltage is equal to the potential energy per charge. The sum of voltage applied to the circuit by the source and potential drops across individual resistor across the loop should be equal to zero.

We get $V = IR_1 + IR_2 + IR_3$.

$$IR_p = IR_1 + IR_2 + IR_3$$

$$IR_p = I(R_1 + R_2 + R_3)$$

$$R_p = R_1 + R_2 + R_3 \quad \left\{ \begin{array}{l} \text{Formula for eq resistance} \\ \text{of resistors connected} \\ \text{in parallel combination} \end{array} \right.$$

for n no. of resistors connected in series.

For each resistor there is the same voltage supply. According to Ohm's law, $V = IR$.

For each resistor

$$I_1 = \frac{V}{R_1}, I_2 = \frac{V}{R_2}, I_3 = \frac{V}{R_3}$$

So,

$$I = I_1 + I_2 + I_3.$$

$$\frac{V}{R_{eq}} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

Taking V common on both sides

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Formula for R_{eq} resistance of resistor connected in parallel combination.

For n no. of resistors the formula will be

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$$

Q) Distinguish the method used to determine loop current for multiple loop networks with neat diagram.

Loop current method :-


The loop current method is a small variation on the Mesh current method. The changes are highlighted in the text below.

• Identify the meshes (open windings of the circuit) and loops (other closed paths).

• Assign current variable to each mesh or loop, using a consistent direction (clockwise or anticlockwise).

• Write Kirchhoff's voltage law equation around each mesh and loop.

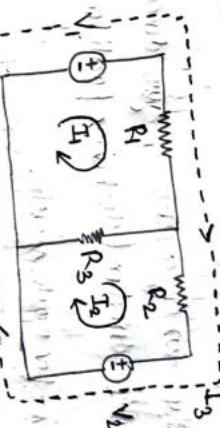- Solve the resulting system of equations for all unknown currents.
- Solve for any element currents and voltages you want using Ohm's law.



Q) Summarise the procedure to calculate the voltages of electrical network using nodal analysis.

Nodal voltage can be calculated by using Nodal Analysis. This type of analysis can be used for both Planar & Non-Planar networks.

→ Firstly identify the no. of nodes and take one node as the reference node (grounded).


→ Assign voltages (V_1, V_2, \dots, V_{n-1}) [no. of nodes] including the reference node.

→ Assign KCL equations at each node except to that of the reference node.

→ Use ohm's law to calculate the value of current or resistance.

b) To find equivalent resistors when $R = 3\Omega$ in question
Star determine their equivalent resistances by using
delta connection

Star to Delta conversion :-

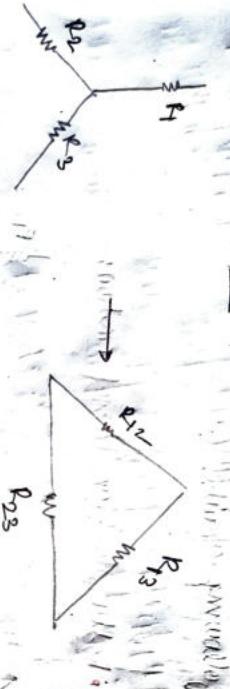


$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

$$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$

$$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$

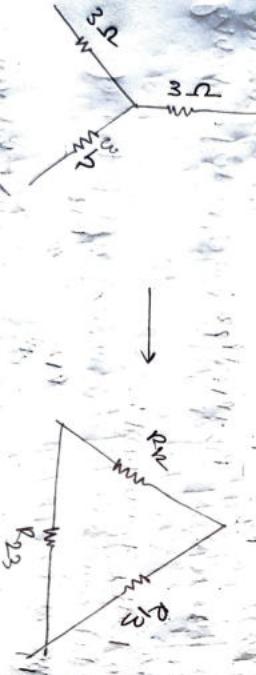Here in the given it is ~~not~~ given ~~eqn~~ resistance of
3 ohm each.



$$\frac{1}{C_{eq}} = \frac{1}{10} + \frac{1}{12} + \frac{1}{5}$$

$$\frac{1}{C_{eq}} = \frac{27}{600}$$

$$C_{eq} = \frac{600}{27} = 22.22F.$$

Parallel connection of capacitors :-
The formula is given by —

$$C_{eq} = C_1 + C_2 + \dots + C_n$$

$$n \rightarrow n=3$$

$$C_1 = 10F$$

$$C_2 = 12F$$

$$C_3 = 5F$$

$$C_{eq} = 10 + 12 + 5$$

$$C_{eq} = 27F.$$

- 11) Consider in coil following a current of $i(t) = 4t^2$ for 1ms.
Derive net voltage across induced power absorbed &
energy stored by 4 inductors if the inductance is 5H

$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3} = 3 + 3 + \frac{3 \cdot 3}{3} = 3R = 3(3) = 9\Omega$$

$$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1} = 3 + 3 + \frac{3 \cdot 3}{3} = 3R = 3(3) = 9\Omega$$

$$R_{31} = R_1 + R_3 + \frac{R_1 R_3}{R_2} = 3 + 3 + \frac{3 \cdot 3}{3} = 3R = 3(3) = 9\Omega$$

Series connection of Capacitors :-
The formula is given by —

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$$

$$n \rightarrow n=3$$

$$C_1 = 10F$$

$$C_2 = 12F$$

$$C_3 = 5F$$

$$C_{eq} = 5(8t)$$

$$= 40t.$$

12) Three capacitors are 10F, 10F & 5F calculate the
capacitance in series & parallel connection.

Power absorbed:

$$P = V^2 = \left[L \frac{di}{dt} \right]^2 + i^2 = \frac{1}{2} L \frac{di^2}{dt} + \frac{1}{2} i^2 = \frac{d}{dt} \left[\frac{1}{2} L i^2 \right].$$

$$P = \frac{d}{dt} \left[\frac{1}{2} L i^2 \right] = \frac{d}{dt} \left[\frac{1}{2} (5)(4t^2) \right] = \frac{d}{dt} \left[\frac{1}{2} i^2 \right].$$

$$P = \frac{d}{dt} \left[\frac{5}{2} \times 16t^4 \right] = \frac{d}{dt} \left[40t^4 \right].$$

$$P = 160t^3.$$

Energy stored:

$$E = \frac{1}{2} L i^2 = \frac{1}{2}(5)(4t^2) = 10t^2.$$

Q) Consider a capacitor absorbing a current of $i(t) = 4t^2$ A. It absorbs 100J of energy. Find the power absorbed and energy stored by capacitor if capacitor is $10\mu F$.

Current flow:

$$i = C \frac{dv}{dt}. \quad i = 5 \left[\frac{d}{dt} [4t^2 + 2t + 4] \right]$$

$$i = 5 [8t + 2].$$

$$i = 40t + 10.$$

power absorbed:

Energy stored:

$P = \frac{d}{dt} \left[\frac{1}{2} C v^2 \right] = \frac{1}{2} C [4t^2 + 2t + 4].$

$i = \frac{1}{2} C v(t).$

- Q) If three inductors are placed in parallel having $100mH$, $25mH$ and $35mH$ inductances respectively. Then calculate equivalent inductance.

For inductors connected in parallel combination the formula is given by:-

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$

$$n_1 = 100mH$$

$$n_2 = 25mH$$

$$n_3 = 35mH$$


$$\frac{1}{L_{eq}} = \frac{1}{100} + \frac{1}{25} + \frac{1}{35} = \frac{100 + 25 + 35}{87500} = \frac{160}{87500} = 5.46 \cdot 87 \text{ mH} = 5.46 \cdot 87 \times 10^{-3} \text{ H} = 0.54 \text{ H}.$$

$$\frac{1}{L_{eq}} = \frac{100 + 25 + 35}{87500} = \frac{160}{87500} = 5.46 \cdot 87 \text{ mH} = 5.46 \cdot 87 \times 10^{-3} \text{ H} = 0.54 \text{ H}.$$

- Q) Explain superposition method to write mesh equations for one port network.

The mesh equations for general planar network can be written by inspection without going through detailed steps.

The loop eqn are:-

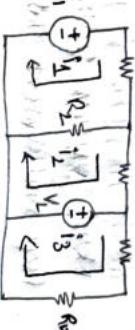

$$IR_1 + R_2(I_1 + I_2) = V_1 \\ R_2(I_2 - I_1) + R_3R_4 = -V_2 \\ R_4I_3 + R_3I_2 = V_2.$$

Reduce the eqn

$$(R_1 + R_2)I_1 - R_2 I_2 = V_1$$

$$-R_2 I_1 + (R_2 + R_3)I_2 = -V_2$$

$$(R_4 + R_5)I_3 = V_2$$

This is how we write eqn of mesh in general.

Take a circuit

$$= \frac{1}{\text{loop}} \times \text{loop}$$

There is 10V

$$10\Omega$$

$$2\Omega$$

$$3\Omega$$

$$I_1$$

$$I_2$$

$$5\Omega$$

$$4\Omega$$

$$6\Omega$$

$$I_3$$

$$0.01$$

$$20V$$

$$I_4$$

$$I_5$$

$$I_6$$

$$I_7$$

$$I_8$$

$$I_9$$

$$I_{10}$$

$$I_{11}$$

$$I_{12}$$

$$I_{244}$$
</

→ The X matrix is a 2×1 matrix where the respective voltages are written.

Here its $\begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$

→ The B matrix is also a 2×1 matrix when the current source value is written.

I_1 is incoming & I_2 outgoing so $I_1 = I_1 - I_2$

$$I_{21} = I_2$$

[Here incoming current is taken positive]

$$\text{so } B = \begin{bmatrix} I_1 - I_2 \\ I_2 \end{bmatrix}$$

Take the whole eqn of matrix we get

$$\begin{bmatrix} G_1 + G_2, G_1 + G_2 \\ -G_2, G_2 + G_3 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_1 - I_2 \\ I_2 \end{bmatrix}$$


$$(G_1 + G_2)(G_2 + G_3)V_1 - G_2V_2 = I_1 - I_2 \quad \text{--- (1)}$$

$$-G_2V_1 + (G_2 + G_3)V_2 = I_2 \quad \text{--- (2)}$$


Solve for required values.

PART-C

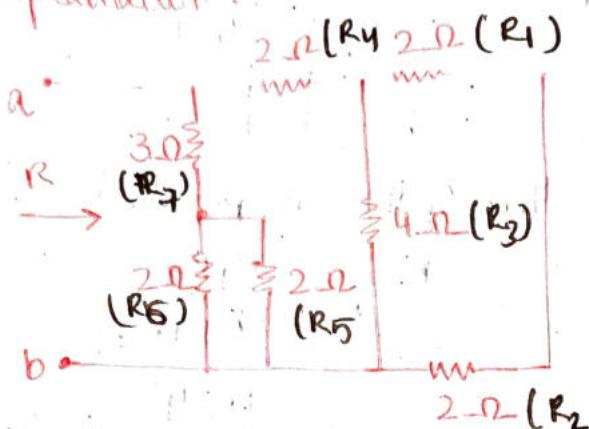1) Calculate eq. resistance showing step by step explanation.



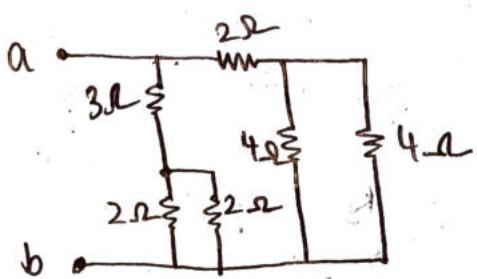
Step 1 :- The last two resistors (R_1) & (R_2) are in series so they can be written as $R_1 + R_2$ i.e., $2 + 2 = 4 \Omega$




Step 2 :-

Now 4Ω & 4Ω are in parallel so the eq. resistance will be $\frac{R_1 R_2}{R_1 + R_2}$ ie.

$$\frac{4 \times 4}{4+4} = 2\Omega$$

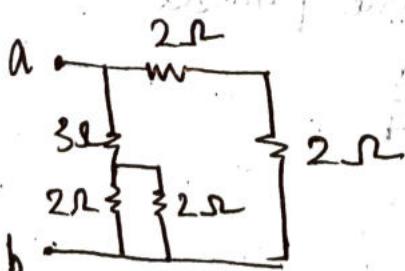

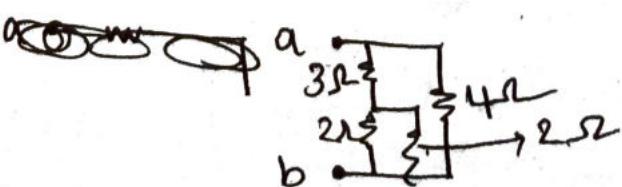
Step 3 :- 2Ω & 2Ω are in series so $R_1 + R_2$ i.e., $2 + 2 = 4\Omega$



Step 4 :- 2Ω & 2Ω in parallel so $\frac{R_1 R_2}{R_1 + R_2} = 1\Omega$

a) Step 5 3Ω & 1Ω in series so

$$R_1 + R_2, 3+1 = 4\Omega$$

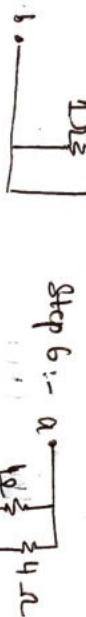

1Ω

3Ω

4Ω

3)



6Ω

$12V$

3Ω

I_1

I_2

6Ω

3Ω

$12V$


I_1

I_2

6Ω

$$\begin{array}{l} \text{eqn } ① \\ \text{eqn } ② \\ \text{eqn } ③ \end{array} \rightarrow V_1 - V_3 = 36V$$

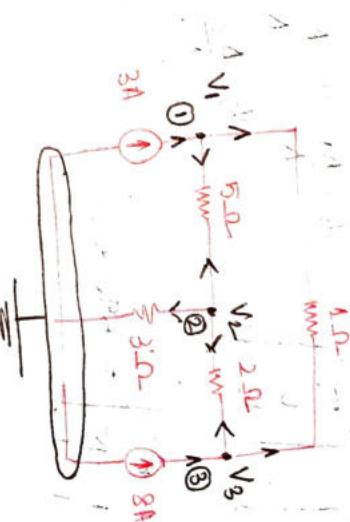The crammer's rule to find out the value of v_1, v_2, v_3 .



$$\frac{276 + V_2 - V_3}{2} = 36V$$

$$\begin{bmatrix} 10-1 \\ 1-10 \\ 4-40 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 36 \\ 276 \\ 290 \end{bmatrix}$$

$$A \geq \sqrt{2} \sqrt{\frac{1}{\lambda_1} + \frac{1}{\lambda_2}} = \sqrt{2} \sqrt{\frac{1}{\lambda_1} + \frac{1}{\lambda_2}}$$

$$\Delta = 8$$

卷之三

~~440.92~~

四庫全書

V. IK

out through

$$\frac{72.5}{12.0} = 6.04 \text{ Am}$$

125

卷之三

$$\Delta \rightarrow \frac{174.25}{1} = 174$$

۲

$$\Delta \rightarrow \frac{138.25}{\gamma} = 2$$

274

⑤ Determine node voltage and power absorbed by nodes 8 and 9 for the network shown.

Nodal analysis (a) 1

$$\frac{V_1 - V_3}{1} + \frac{V_1 - V_2}{5} = 3 .$$

$$5V_1 - 5V_3 + V_1 - V_2 = 15$$

$$6V_1 - V_2 + 5V_3 = 15 \rightarrow 0$$

word count at $\sqrt{2}$

$$\frac{r}{5} + \frac{\sqrt{2}-\sqrt{3}}{2} + \frac{\sqrt{2}}{3} = 0$$

$$6V_2 - 8V_1 + 15V_2 - 15V_3 + 10V_2 = 0$$

$$-6V_1 + 31V_2 - 15V_3 = 0 \quad \text{---} \quad ②$$

Neural amnesia @ V

卷之三

$$G_8 = \frac{e}{\tau_0 \cdot g} + \frac{c}{\tau_0 \cdot g}$$

$$= \frac{1}{\lambda} \left(\frac{\partial}{\partial \lambda} \ln \det \left(\lambda I + A \right) \right)$$

$$\textcircled{3} \rightarrow 91 = 3\sqrt{1 + \sqrt{1 + \sqrt{1 + \dots}}}$$

For calculation of node voltage.
we should apply cramer's rule.

- 6) Using superposition method, calculate the current in each branch for network shown in figure.

shown in figure?

$$\begin{bmatrix} 6 & -1 & 5 \\ -6 & 31 & -15 \\ -2 & -1 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 15 \\ 0 \\ 16 \end{bmatrix}$$

$$V_1 = \frac{\Delta_1}{\Delta}, V_2 = \frac{\Delta_2}{\Delta}, V_3 = \frac{\Delta_3}{\Delta}$$

$$\Delta = \begin{bmatrix} 6 & -1 & 5 \\ -6 & 31 & -15 \\ -2 & -1 & 1 \end{bmatrix} = 1600$$

$$\Delta_1 = \begin{bmatrix} 15 & -1 & 5 \\ 0 & 31 & -15 \\ 16 & -1 & 1 \end{bmatrix} = -2000$$

$$\Delta_2 = \begin{bmatrix} 6 & 15 & 5 \\ -6 & 0 & -15 \\ -2 & 16 & 1 \end{bmatrix} = 1800$$

$$\Delta_3 = \begin{bmatrix} 6 & -1 & 15 \\ -6 & 31 & 0 \\ -2 & -1 & 16 \end{bmatrix} = 3900$$

$$i_1 = \frac{1}{2}V + \frac{1}{3}V - \frac{1}{2}V$$

$$i_2 = \frac{1}{3}V - \frac{1}{2}V + \frac{1}{2}V$$

$$i_3 = \frac{1}{2}V - \frac{1}{3}V + \frac{1}{2}V$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{-2000}{1600} = -1.25V$$


$$V_2 = \frac{\Delta_2}{\Delta} = \frac{1800}{1600} = 1.125V$$

$$V_3 = \frac{\Delta_3}{\Delta} = \frac{3900}{1600} = 2.4375V$$

$$\text{Power} = \frac{V^2}{R} = \frac{V_1^2}{R_1} = \frac{(-1.25)^2}{5} = 0.75W$$

$$= \frac{V_2^2}{R_2} = \frac{(1.125)^2}{5} = 0.25W$$
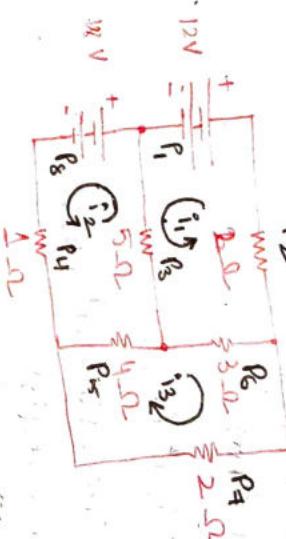
$$= \frac{V_3^2}{R_3} = \frac{(2.4375)^2}{5} = 1.175W$$



Mesh analysis by inspection
can only be applied
if there is a
circuit with only
resistor & independent
voltage sources.

$$\begin{bmatrix} 10 & -5 & -3 \\ -5 & 10 & -4 \\ -3 & -4 & 9 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 12 \\ -18 \\ 0 \end{bmatrix}$$

$$\begin{aligned} 10i_1 - 5i_2 - 3i_3 &= 12 \\ -5i_1 + 10i_2 - 4i_3 &= -18 \\ -3i_1 - 4i_2 + 9i_3 &= 0 \end{aligned}$$

After applying cramer's rule,

$$i_1 = \frac{\Delta_1}{\Delta}, i_2 = \frac{\Delta_2}{\Delta}, i_3 = \frac{\Delta_3}{\Delta}$$

$$\Delta_1 = \begin{bmatrix} -12 & -5 & -3 \\ -18 & 10 & -4 \\ 0 & -4 & 9 \end{bmatrix} = -1914$$

$$\Delta_2 = \begin{bmatrix} 10 & -12 & -3 \\ -15 & 10 & -4 \\ -3 & 0 & 9 \end{bmatrix} = -2242$$

$$\Delta_3 = \begin{bmatrix} 10 & -5 & -12 \\ -5 & 10 & -4 \\ -3 & -4 & 0 \end{bmatrix} = -1590$$

$$\Delta = 305$$

$$i_1 = -6.27A$$

$$i_2 = 17.02A$$

$$i_3 = -5.21A$$

Power Loss :-

Power loss is given by I^2R .

$$\text{Power loss at } P_2 = (-6.27)^2 \times 2 = 39.31 \text{ W}$$

$$\text{Power loss at } P_2 = (\overline{i_2})^2 \times 5 = 0.5025 \text{ W}$$

$$= (-7.02 + 6.27)^2 \times 5 = 19.21 \text{ W}$$

$$= 0.5025 \text{ W}$$

$$\text{Power loss at } P_4 = (\overline{i_2})^2 \times 1 = 49.28 \text{ W}$$

$$\text{Power loss at } P_5 = (\overline{i_2} + \overline{i_3})^2 \times 4 = (-7.02 - 5.21)^2 \times 4 = 598.29 \text{ W}$$

$$\text{Power loss at } P_6 = (\overline{i_3})^2 \times 3 = (-5.21)^2 \times 3 = 395.37 \text{ W}$$



$$= (-11.48)^2 \times 3 = 395.37 \text{ W}$$

$$R_1 = \frac{R_{12} \cdot R_{23}}{R_{12} + R_{13} + R_{23}} = \frac{2 \times 3}{10} = \frac{6}{10} = \frac{3}{5} \Omega$$


$$R_2 = \frac{R_{13} \cdot R_{23}}{R_{12} + R_{13} + R_{23}} = \frac{2 \times 5}{10} = 1 \Omega$$

$$\text{Power loss at } P_7 = (\overline{i_3})^2 \times 2$$

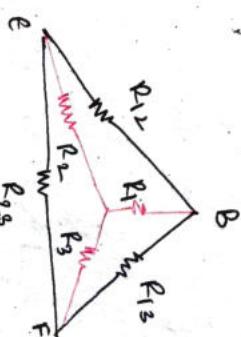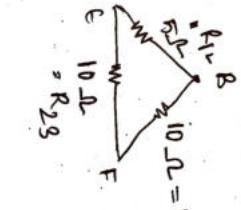
$$= (-5.21)^2 \times 2 = 54.28 \text{ W}$$


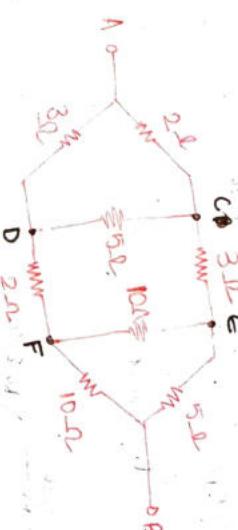
$$R_1 = \frac{R_{12} \cdot R_{13}}{R_{12} + R_{13} + R_{23}} = \frac{10 \times 5}{25} = 2 \Omega$$



Convert Δ Delta to star:-


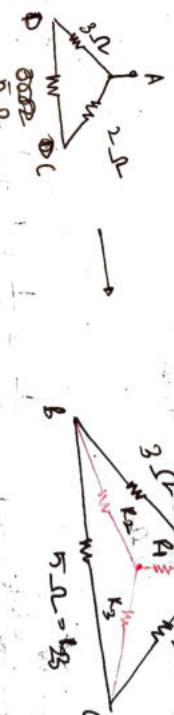


- ④ Calculate the voltage to be applied across the resistors to drive current of 1 A . In the circuit using star-delta transformation for the network shown in fig?

$$R_2 = \frac{R_{12} \cdot R_{23}}{R_{12} + R_{23} + R_{13}} = \frac{15 \times 10}{25} = 2\Omega$$

$$R_3 = \frac{R_{13} \cdot R_{23}}{R_{12} + R_{23} + R_{13}} = \frac{10 \times 10}{25} = 4\Omega$$

The circuit can be redrawn as:-

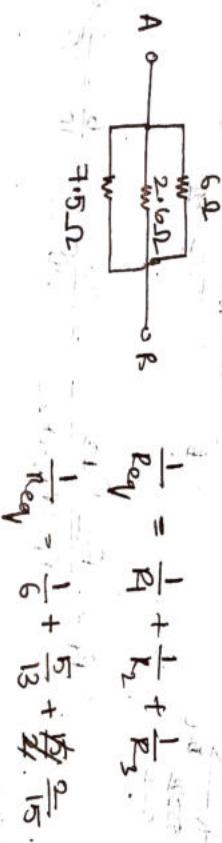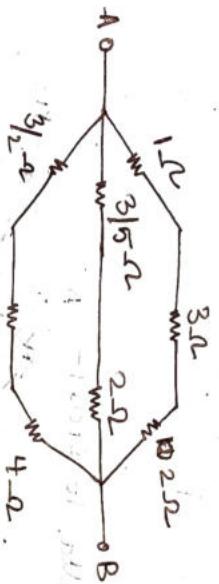

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_{eq}} = \frac{1}{6} + \frac{1}{13} + \frac{2.6}{15}$$

$$\frac{1}{R_{eq}} = \frac{450}{195 + 20 + 156}$$

$$R_{eq} = \frac{1170}{450} = 1.46\Omega$$

Nodal analysis @ C.

$$\frac{V_A - V_C}{2} = \frac{V_B - V_C}{5} + 4 + \frac{V_B}{1} \rightarrow \textcircled{2}$$

~~$$\text{Nodal Analysis @ A.}$$~~

$$\bar{\sigma} = \frac{V_A}{3} + \frac{V_B - V_C}{2} \rightarrow \textcircled{1}$$

Nodal Analysis @ B.

$$\frac{V_A - V_B}{5} + 4 = \frac{V_C + 29}{1} \rightarrow \textcircled{3}$$


Simplifying $\textcircled{1}, \textcircled{2}$ & $\textcircled{3}$

$\therefore \text{eqn } \textcircled{1} :- 30 = 5V_A - 3V_B$.

$\text{eqn } \textcircled{2} :- 40 = 5V_A - 17V_B + 2V_C$.

$\text{eqn } \textcircled{3} :- V_B - V_C + 20 = 5V_C + 145$

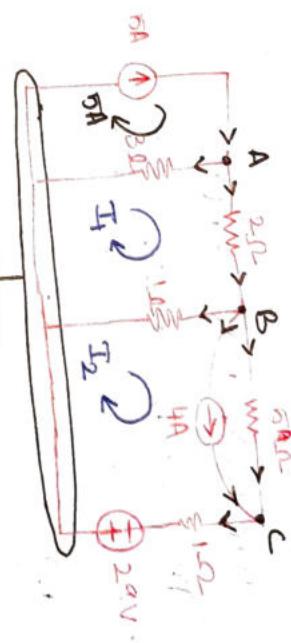a) Determine the node voltage using nodal analysis for given circuit.



use eq ① ② ③ to find V_A, V_B, V_C .

$$eq \textcircled{1} \rightarrow (5V_A - 3V_B) - 14V_B + 2V_C = 40$$

~~$$30 - 14V_B + 2V_C = 10 \rightarrow \textcircled{2}$$~~

~~$$14V_B - 2V_C = -10.$$~~

$$\Delta_1 = \begin{bmatrix} 90 & -3 & 0 \\ 40 & -17 & 2 \\ 125 & 1 & -6 \end{bmatrix} = 1530$$

eq ③

~~$$V_B - 6V_C = 125.$$~~

$$V_B - 6V_C - 135 = -10 \rightarrow \textcircled{3}$$

eq ② & eq ③ to be equated.

~~$$14V_B - 2V_C = V_B - 6V_C - 135.$$~~

~~$$13V_B + 4V_C = -135.$$~~

so the equations are:-

~~$$5V_A - 3V_B + 0V_C = 30$$~~

~~$$5V_A - 14V_B + 2V_C = 40$$~~

~~$$0V_A + V_B - 6V_C = 125.$$~~

Apply cramer's rule.

$$V_A = \frac{\Delta_1}{\Delta}, \quad V_B = \frac{\Delta_2}{\Delta}, \quad V_C = \frac{\Delta_3}{\Delta}$$

$$\begin{bmatrix} 5 & -3 & 0 \\ 5 & -17 & 2 \\ 0 & 1 & -6 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} 30 \\ 40 \\ 125 \end{bmatrix}$$

$$\Delta = \begin{bmatrix} 5 & -3 & 0 \\ 5 & -17 & 2 \\ 0 & 1 & -6 \end{bmatrix}.$$


$$V_A = \frac{\Delta_1}{\Delta} = \frac{1530}{410} = 3.73V$$

$$V_B = \frac{\Delta_2}{\Delta} = \frac{-1550}{410} = -3.78V$$

$$V_B = \frac{\Delta_3}{\Delta} = \frac{-8800}{410} = -21.4V$$

= 10)

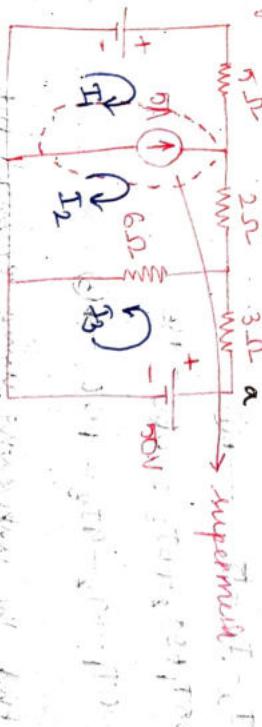Determine the current through branch $a-b$ using mesh analysis shown in the figure.




There is independent current source in between 2 meshes so it is a supermesh.

The eq of supermesh is $I_2 - I_1 = 5 \rightarrow \textcircled{1}$

Write the eq's of mesh ④ & ② simultaneously excluding the supernode.

$$I_1 = \frac{\Delta_1}{\Delta}, \quad I_2 = \frac{\Delta_2}{\Delta}, \quad I_3 = \frac{\Delta_3}{\Delta}$$
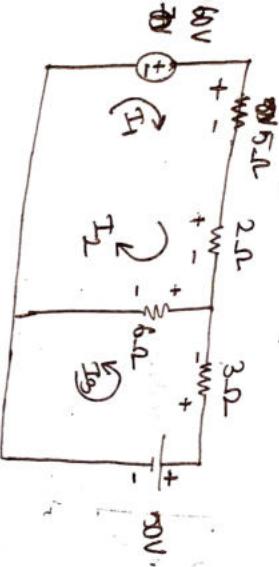
$$I_1 = 8.14A, \quad I_2 = 13.14A, \quad I_3 = -14.32A$$



$$60 - 5I_1 - 2I_2 - 6(I_2 + I_3) = 0 \rightarrow ②$$

$$60 - 5I_1 - 2I_2 - 6I_3 = 0 \rightarrow ③$$

$$60 - 5I_1 - 8I_2 - 6I_3 = 0 \rightarrow ②$$

Mesh analysis at ③ mesh 3.

$$-50 - 3I_3 - 6(I_3 + 0I_2) = 0$$

$$-50 - 3I_3 - 6I_3 - 6I_2 = 0$$

$$-50 - 6I_2 - 9I_3 = 0 \rightarrow ③$$

$$I_2 - I_1 = 5 \rightarrow ①$$

$$5I_1 + 8I_2 + 6I_3 = 60 \rightarrow ②$$

$$0I_1 - 6I_2 - 9I_3 = 50 \rightarrow ③$$

Find the unknowns using cramer's rule.


$$\begin{bmatrix} 5 & 8 & 6 \\ 0 & -6 & -9 \\ 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 50 \\ 0 \end{bmatrix}$$

$$4I_1 - 200I_2 - 800I_3 = 0 \rightarrow ④$$

$$4I_1 - 800I_2 = 50 \rightarrow I_1 = \frac{50}{400} = 0.005A$$

$$400I_2 + 1600I_3 = -4 \rightarrow ⑤$$

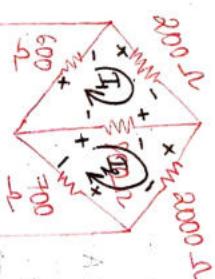(ii) Determine current through 800Ωm resistor in the network shown.



Apply mesh analysis at ③ mesh ①.

$$4I_1 - 200I_2 - 800I_3 = 0 \rightarrow ④$$

$$4I_1 - 800I_2 = 50 \rightarrow I_1 = \frac{50}{400} = 0.005A$$

$$400I_2 + 1600I_3 = -4 \rightarrow ⑤$$

Apply mesh analysis @ mesh ①

$$+4 - 2000\text{I}_2 - 700\text{I}_1 - 800\text{I}_2 + 800\text{I}_1 = 0$$

$$800\text{I}_1 - 3500\text{I}_2 = -4 \rightarrow ②$$

Solve eq ① & eq ② for current values.

$$800\text{I}_2 - 1600\text{I}_1 = -4$$

$$800\text{I}_1 - 3500\text{I}_2 = -4 \quad \times 2$$

$$800\text{I}_2 - 1600\text{I}_1 = -4$$

$$1600\text{I}_1 - 7000\text{I}_2 = -8$$

$$\cancel{+6200\text{I}_2 = 12}$$

$$\begin{cases} \text{I}_1 = 0.0019 \text{ A.} \\ \text{I}_2 = 1.9 \text{ mA.} \end{cases}$$

$$\text{NOTE: } 800(1.9 \text{ mA}) - 1600(\text{I}_1) = -4$$

$$800(0.0019) - 1600\text{I}_1 = -4$$

$$-1600\text{I}_1 = -4 - 1.52$$

$$1600\text{I}_1 = 4.52$$

$$\text{I}_1 = \frac{4.52}{1600} = 0.0034 \text{ A.}$$

$$\boxed{\text{I}_1 = 0.34 \text{ mA}}$$

current through 800Ω $\cancel{\text{I}_1 - \text{I}_2} = 3.4 \text{ mA} - 1.9 \text{ mA} = 1.5 \text{ mA}$

$$\text{Super node eq} \rightarrow \boxed{V_2 - V_1 = 6} \rightarrow ①$$

$$\text{Node analysis @ } V_2 \rightarrow \boxed{4 = \frac{V_3 - V_2}{0.5} + 2} \rightarrow ②$$

$$4 = 2V_3 - 2V_2 + 2$$

$$2 = 2(V_2 - V_3) \quad V_3 - V_2 = 1 \rightarrow ③$$

Simultaneous eq ① & eq ② excluding super node.

$$\frac{V_2}{0.5} + \frac{V_2 - V_3}{0.5} + \frac{V_1}{0.5} - 2 = 0 \rightarrow ②$$

$$2V_2 + 2V_2 - 2V_3 + 2V_1 - 2 = 0$$

$$4V_2 + 2V_1 - 2V_3 - 2 = 0$$

$$2V_2 + V_1 - V_3 - 1 = 0 \rightarrow ④$$

Sub ④ in ②

$$2V_2 + V_1 - 6 + V_3 + 1 = 0$$

$$3V_2 + V_3 + 5 = 0 \rightarrow ④$$

Solve ③ & ④.

$$\begin{cases} 3V_3 - 3V_2 = 3 \\ 3V_2 + V_3 = 5 \end{cases}$$

$$4V_3 = 8 \quad V_3 = 2 \text{ V}$$

$$2V_2 = 5 \quad V_2 = 2.5 \text{ V}$$

$$V_1 = 1 \text{ V}$$

$$V_2 = 2.5 \text{ V}$$

$$V_3 = 2 \text{ V}$$

$$V_1 = 1 \text{ V}$$

$$V_2 = 2.5 \text{ V}$$

$$V_3 = 2 \text{ V}$$

$$V_1 = 1 \text{ V}$$

$$V_2 = 2.5 \text{ V}$$

$$V_3 = 2 \text{ V}$$

$$V_1 = 1 \text{ V}$$

$$V_2 = 2.5 \text{ V}$$

$$V_3 = 2 \text{ V}$$

$$V_1 = 1 \text{ V}$$

<


13) Determine value of node voltage V_A & V_B .



supernode eq². explain later

$$\boxed{V_b - V_A = 12} \rightarrow ①$$

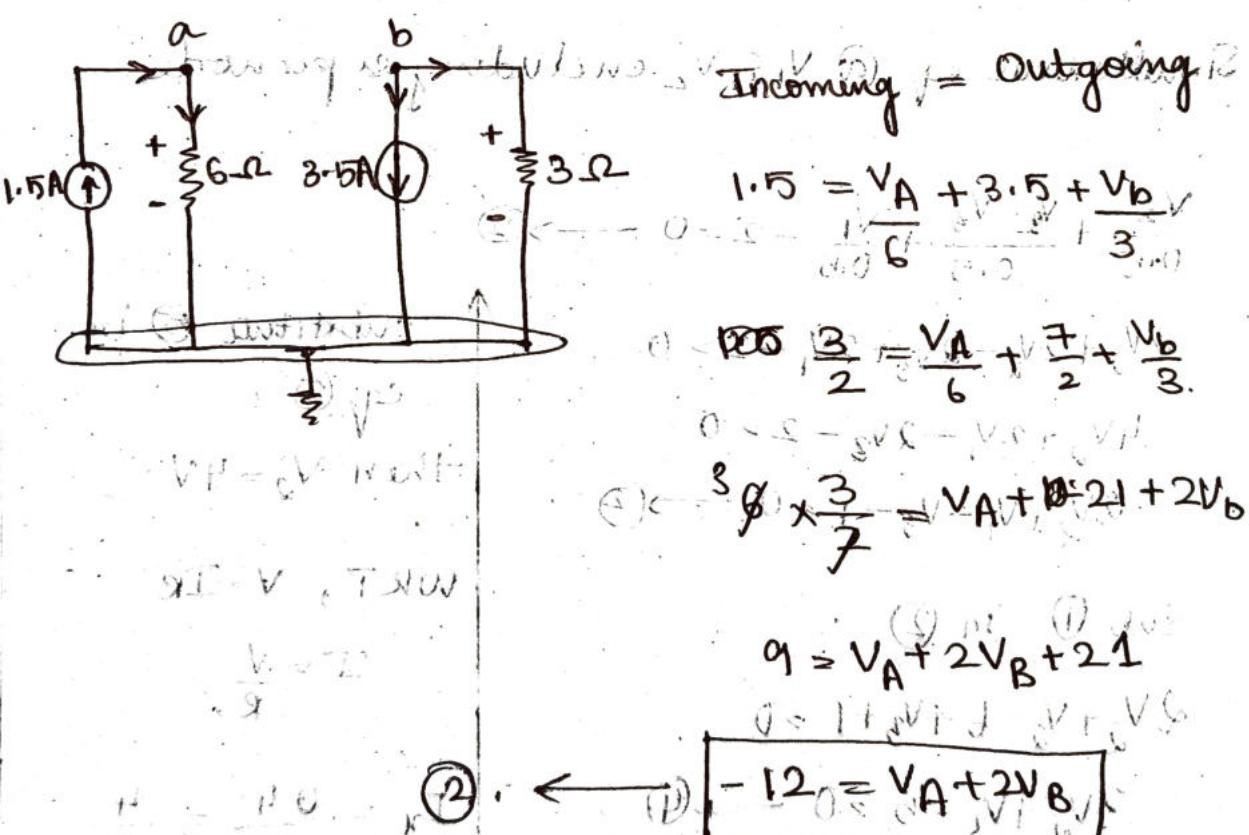Write 2nd eq i.e., simultaneously between node a & b excluding the supernode.



Node analysis @ node 3.

~~$$V_b - V_A = 12$$~~

~~$$V_A + 2V_B = -12$$~~

$$3V_B > 0 \rightarrow V_B > 0$$

$$\boxed{\begin{aligned} V_B &= 0 \\ V_A &= -12V \end{aligned}}$$