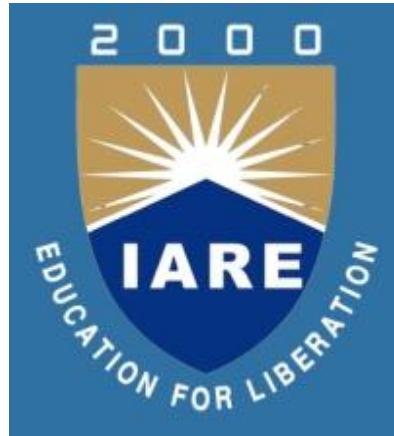


# BASIC ELECTRICAL AND ELECTRONICS ENGINEERING



PPT ON  
**BASIC ELECTRICAL AND ELECTRONICS  
ENGINEERING**



**Network Theorems:** Superposition, Reciprocity, Thevenin's, Norton's, Maximum power transfer for DC excitations circuits.


**Network Topology:** Definitions, Graph, Tree, Incidence matrix, Basic Cut Set and Basic Tie Set Matrices for planar networks.

- **Superposition theorem** states that in any linear, active, bilateral network having more than one source, the response across any element is the sum of the responses obtained from each source considered separately and all other sources are replaced by their internal resistance.
- The superposition theorem is used to solve the network where two or more sources are present and connected.

- **Superposition theorem** states that in any linear, active, bilateral network having more than one source, the response across any element is the sum of the responses obtained from each source considered separately and all other sources are replaced by their internal resistance.
- The superposition theorem is used to solve the network where two or more sources are present and connected.



# Superposition Theorem

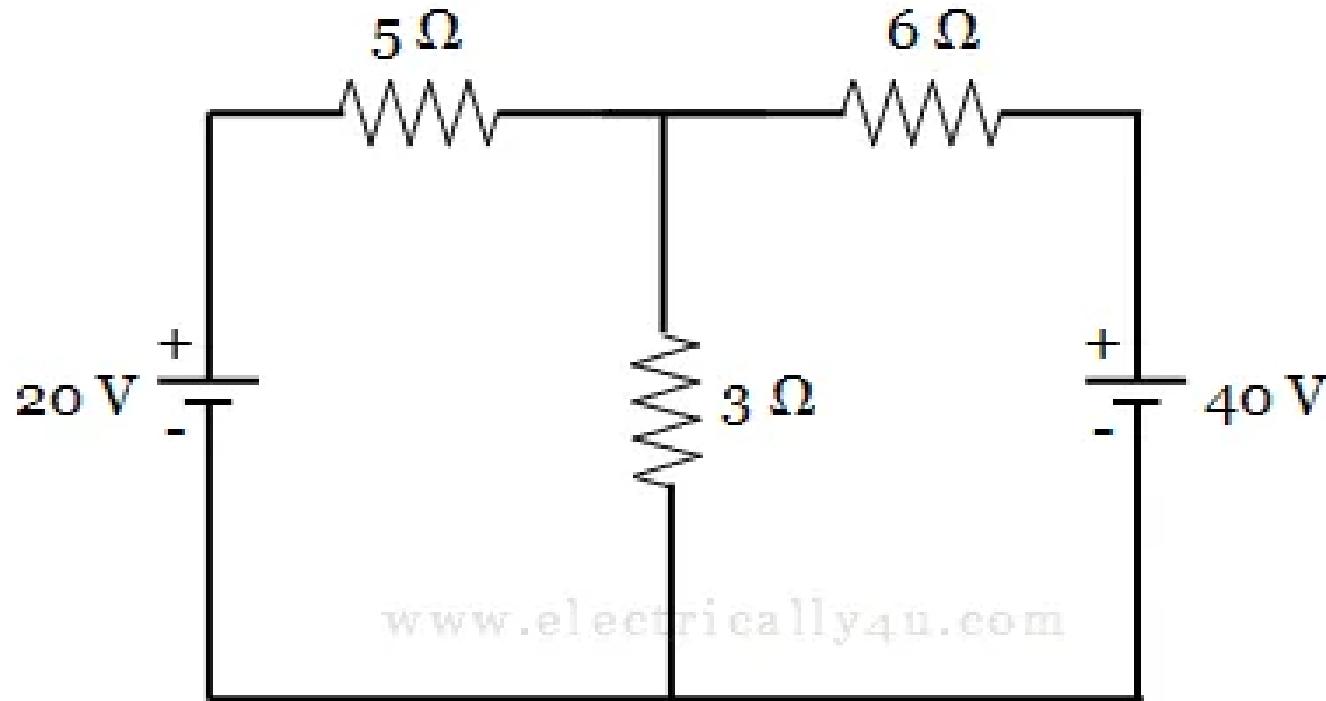***Find the current through  $3\ \Omega$  resistor using superposition theorem.***


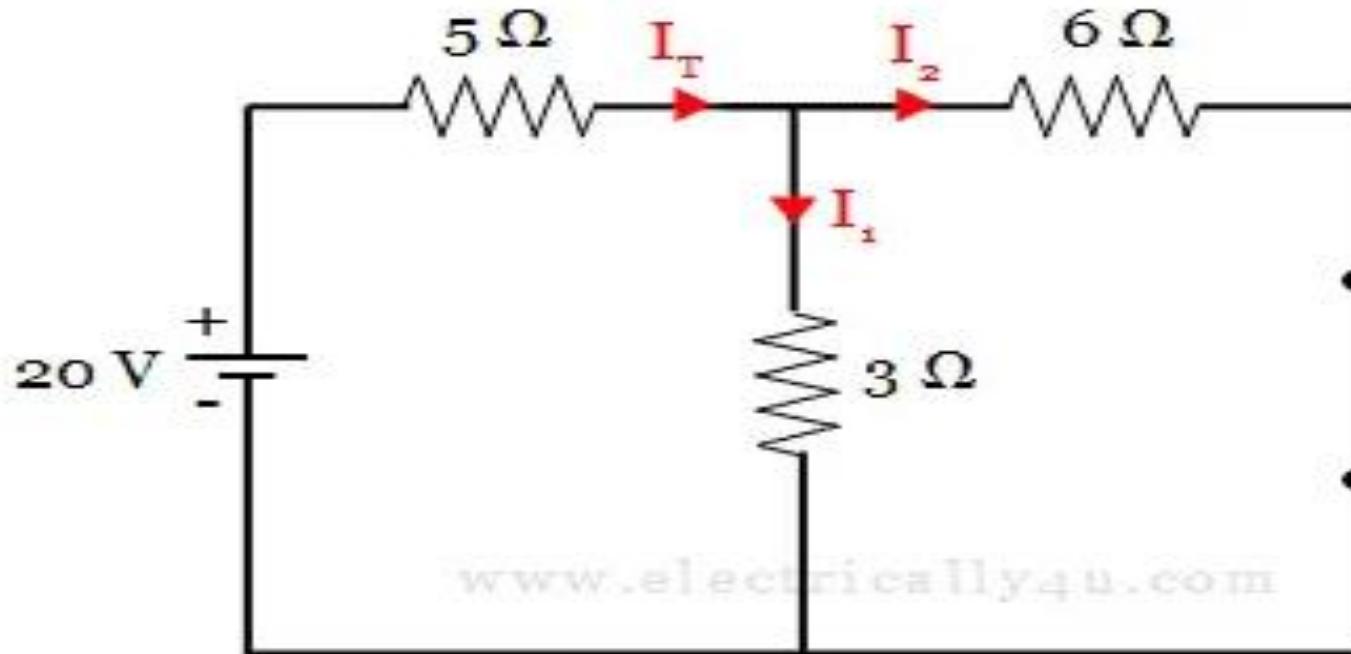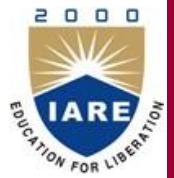
## Superposition Theorem

Consider **20 v voltage source alone**. Hence, Short circuit the other voltage source and the circuit is redrawn as below,



# Superposition Theorem




$$R_T = 5 + \frac{3 * 6}{3 + 6} = 7\Omega \cancel{\Omega}$$

$$I_T = \frac{V}{R_T} = \frac{20}{7} = 2.857A$$

$$I_1 = I_T * \frac{6}{6 + 3} = 2.857 * 0.667 = 1.904A$$
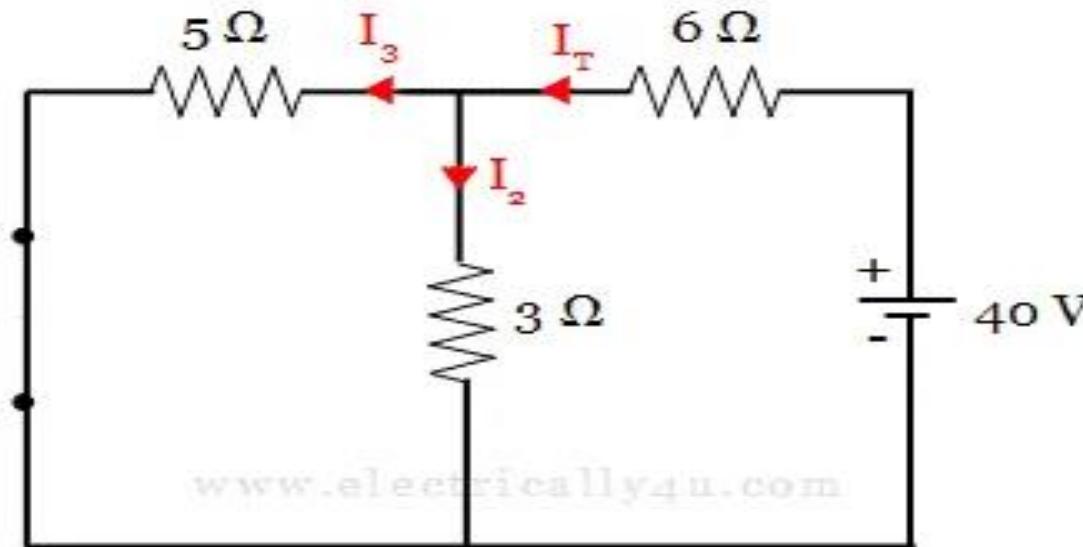
## Superposition Theorem

Consider **40 v voltage source alone**. Hence, Short circuit the other voltage source and the circuit is redrawn as below,



# Superposition Theorem




$$R_T = 6 + \frac{3 * 5}{3 + 5} = 7.875\Omega$$

$$I_T = \frac{V}{R_T} = \frac{40}{7.875} = 5.079A$$

$$I_2 = I_T * \frac{5}{5 + 3} = 5.079 * 0.625 = 3.174A$$


## Superposition Theorem

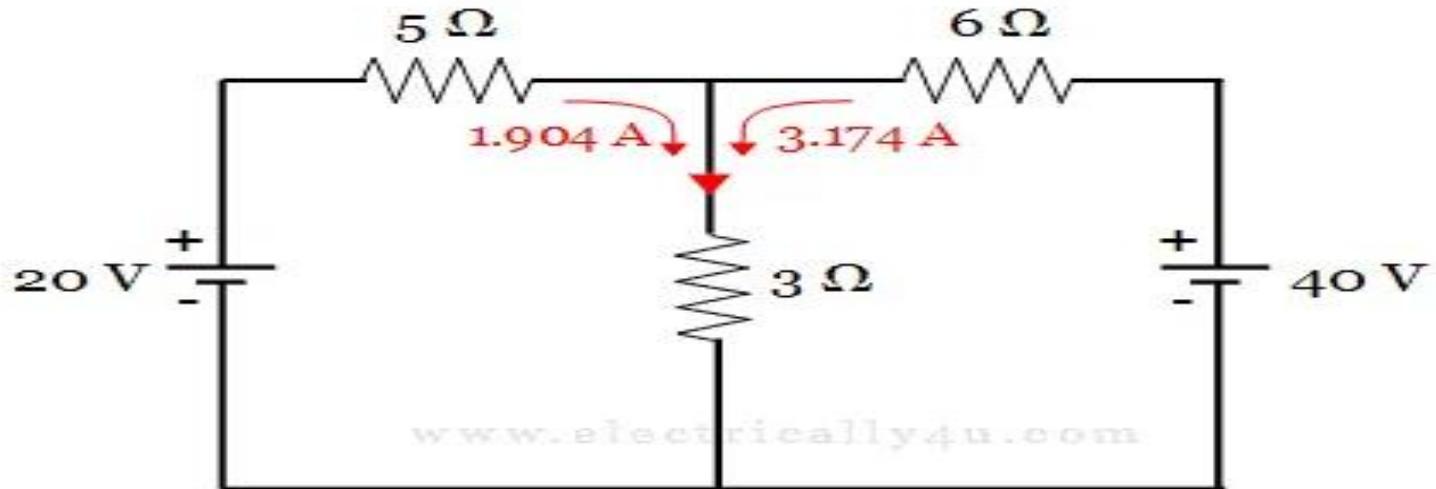


By superposition theorem, the total current is determined by adding the individual currents produced by 20 v and 40 v.

*Thus the current through  $3 \Omega$  resistor is  $= I_1 + I_2 = 1.904 + 3.174 = 5.078 A$*

# Superposition Theorem

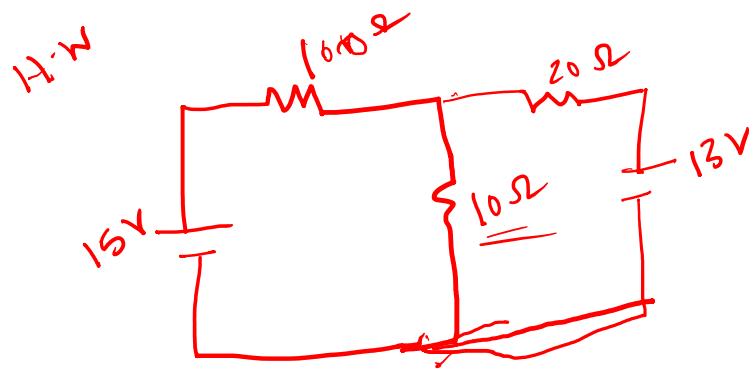

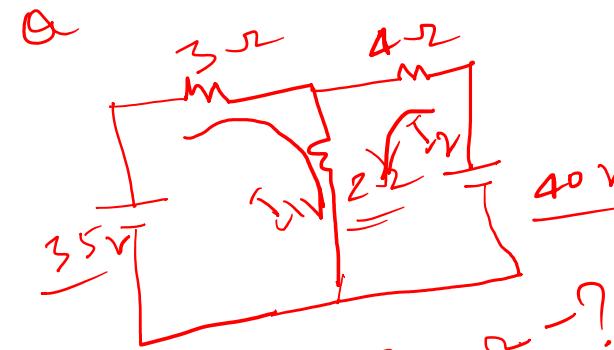find current through  $10\Omega$   
resistor  
using superposition theorem



$$35V - I_1 + I_2 = ?$$


$$R_{eq} = \frac{3}{4} \Omega, I_1 = \frac{V}{R} = \frac{35}{4.33} = 8.08A$$

$$40V - I_2 =$$

$$R_{eq} = 5.2\Omega, I_2 = \frac{40}{5.2} = 7.69A$$

$$I_{25V} = I_1 + I_2$$

# Superposition Theorem

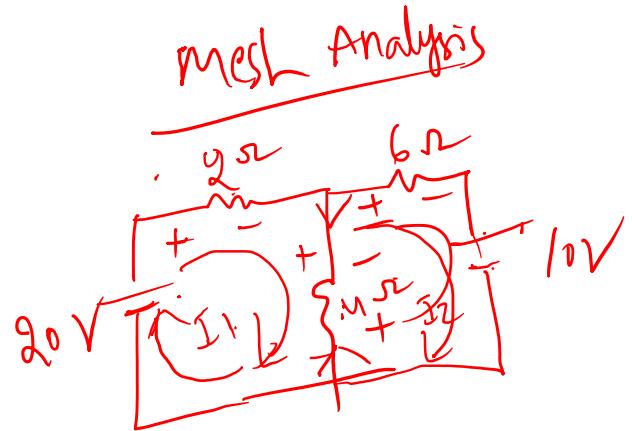

mesh 1

$$2I_1 + 4(I_1 - I_2) - 20 = 0$$

$$(2I_1 + UI_1) - 4I_2 = 20 \quad (1)$$

$$6I_1 - UI_2 = 20 \quad (2)$$

$$6I_1 = 20 + UI_2 \quad (3)$$

$$I_1 = \frac{20 + UI_2}{6} \quad (4)$$

Mesh 2)


$$6I_2 + 10 + u(I_2 - I_1) = 0$$

$$6I_2 + UI_2 - UI_1 + 10 = 0$$

$$-UI_1 + 10I_2 = -10 \quad (5)$$

Solve eq ① & ②

$I_1$  &  $I_2$

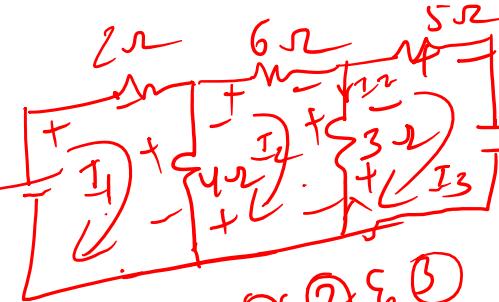

solve eq ① & ② & ⑤

$I_1$ ,  $I_2$  &  $I_3$

③

Cramer's rule

=

mesh 1

$$2I_1 + 4(I_1 - I_2) - 30 = 0$$

$$(I_1 + UI_1) - UI_2 = 30$$

$$6I_1 - UI_2 = 30 \quad (1)$$

mesh II

$$6I_2 + 3(6I_2 + 3(I_2 - I_3) + 4(I_2 - I_1)) = 0$$

$$6I_2 + 3I_2 - 3I_3 + 4I_2 - 4I_1 = 0$$

$$-UI_1 + 13I_2 - 3I_3 = 0 \quad (2)$$



mesh III

$$5I_3 + 20 + 3(I_3 - I_2) = 0$$

$$\underline{5I_3 + 20 + 3I_3 - 3I_2 = 0}$$

$$-3I_2 + 8I_3 = -20 \quad (3)$$

# Superposition Theorem

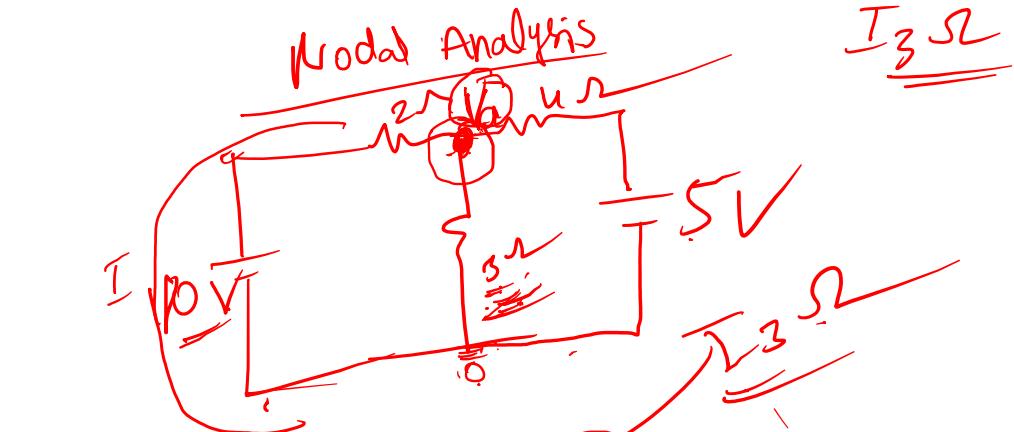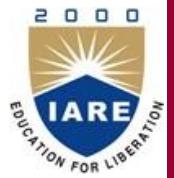

$$\rightarrow \frac{Va - 10}{2} + \frac{Va - 0}{3} + \frac{Va - 5}{4} = 0$$

$$0.5(Va - 10) + 0.33(Va) + 0.25(Va - 5) = 0$$

$$0.5Va - (0.5 \times 10) + 0.33Va + 0.25Va - (0.25 \times 5) = 0$$

$$\underline{0.5Va - 5 + 0.33Va + 0.25Va - 1.25 = 0}$$

$$1.08Va - 6.25 = 0$$

$$\underline{\underline{Va}} = \frac{6.25}{1.08} = 5.787V$$


$$\underline{\underline{I_{3SL}}} = \frac{Va}{3} = \frac{5.787}{3}$$

$$\underline{\underline{= 1.929A}}$$

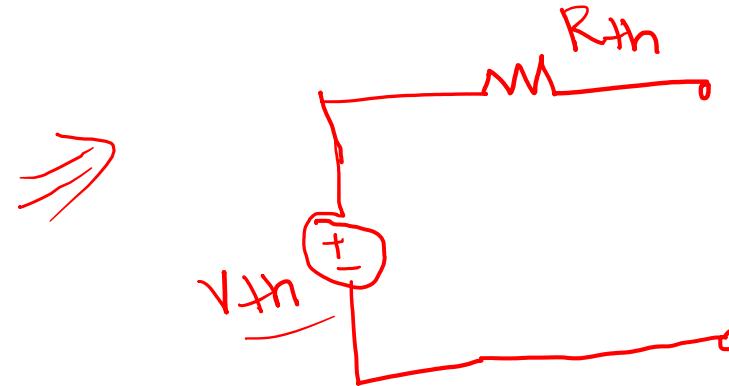
## Thevenin's theorem



Any **linear electric network** or a complex circuit with current and voltage sources can be replaced by an equivalent circuit containing of a single independent voltage source  $V_{TH}$  and a Series Resistance  $R_{TH}$ .






# Thevenin's theorem

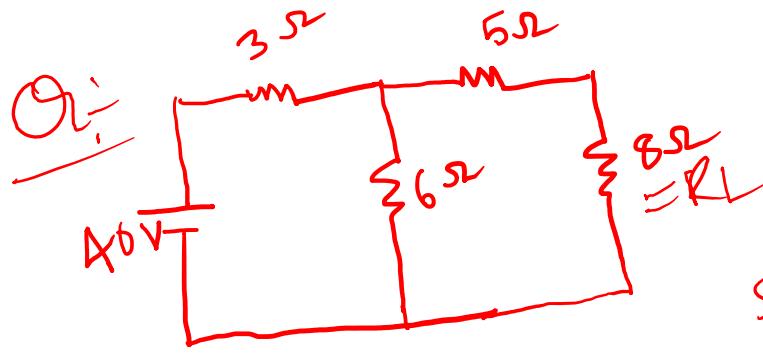

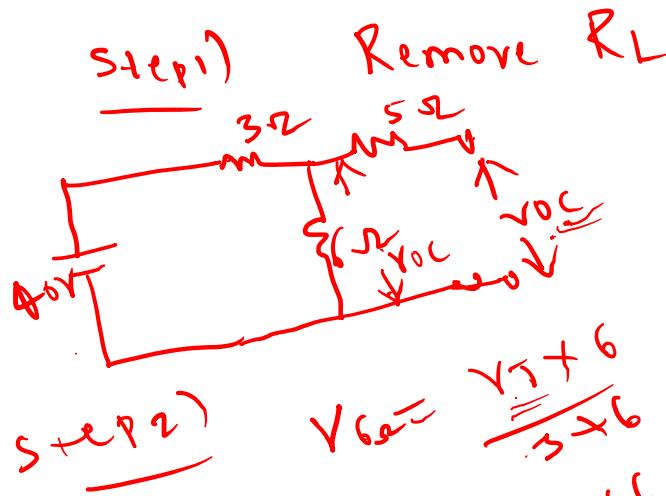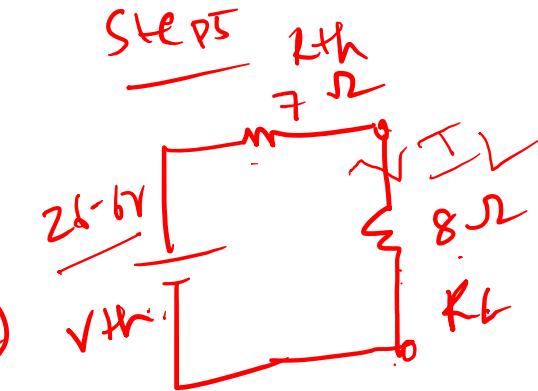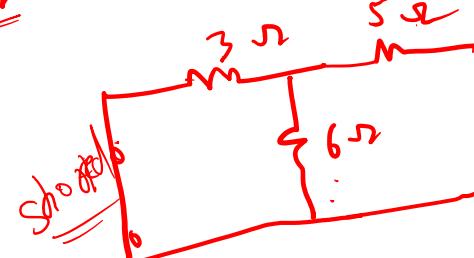
Q1: Calculate current flowing through 8Ω Resistor using Thevenin's theorem

Step 1) Req =  $\rightarrow$  shorted T-open



$$V_{oc} = \frac{40 + 6}{3 + 6} = 6.6V$$
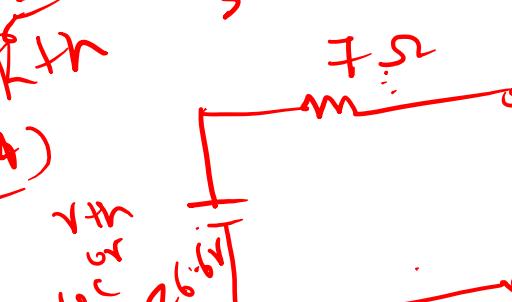
$$R_{eq} = \frac{3 + 6}{3 + 6} + 5 = 7\Omega$$




$$I_L = \frac{V_{th}}{R_{th} + R_L}$$


$$I_L = \frac{26.6V}{7 + 8}$$

$$I_{8\Omega} = 1.77A$$

# Thevenin's theorem

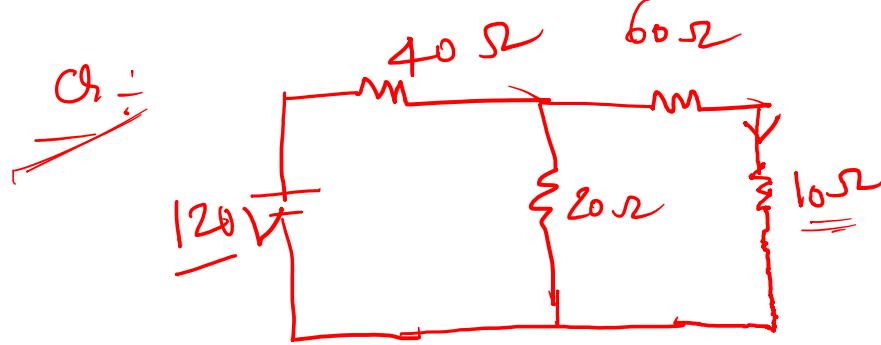

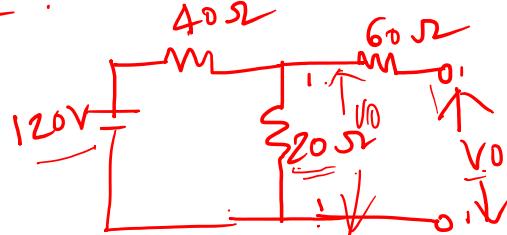Step 1: Remove Load Resistance ( $10\text{ }\Omega - R_L$ )



Step 2:  $V_0$  or  $V_{th}$  Voltage division Rule

$$V_0 = \frac{V_t \times 20}{40 + 20} = 40\text{ V}$$


$$= \frac{120 \times 20}{40 + 20} = 40\text{ V}$$

Calculate current flowing through  $10\text{ }\Omega$  Resistor using  
Thevenin's theorem.

$$I_{10\Omega} = 0.481\text{ A}$$

Step 3:  $R_{eq}$  or  $R_{th}$

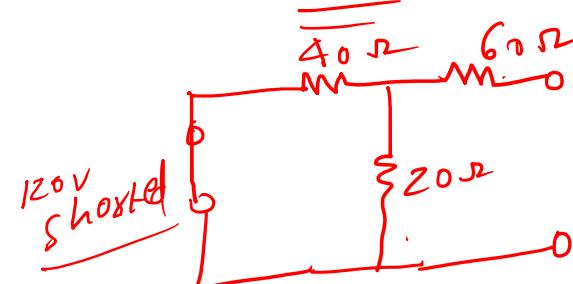$V \rightarrow$  shorted or  $I \rightarrow$  open




$$R_{eq} = \frac{40 \times 20}{40 + 20} + 60 = 73.33\text{ }\Omega$$


$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

$$= \frac{40}{73.33 + 10}$$

$$I_L = 0.481\text{ A}$$

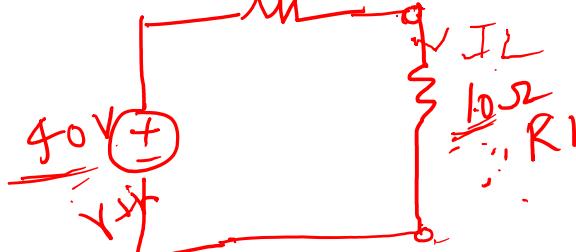

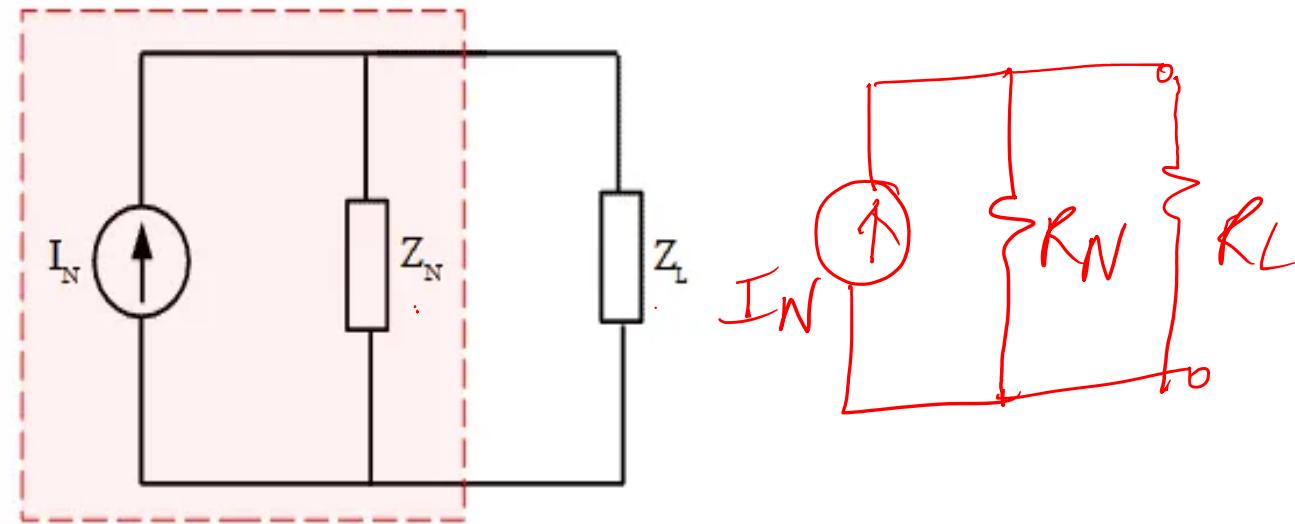**Statement:** Norton's theorem is used to solve the complex circuits consisting of several sources and impedances by converting them into a simple equivalent circuit called Norton's equivalent circuit. Now let's look at the statement.




# Norton's theorem

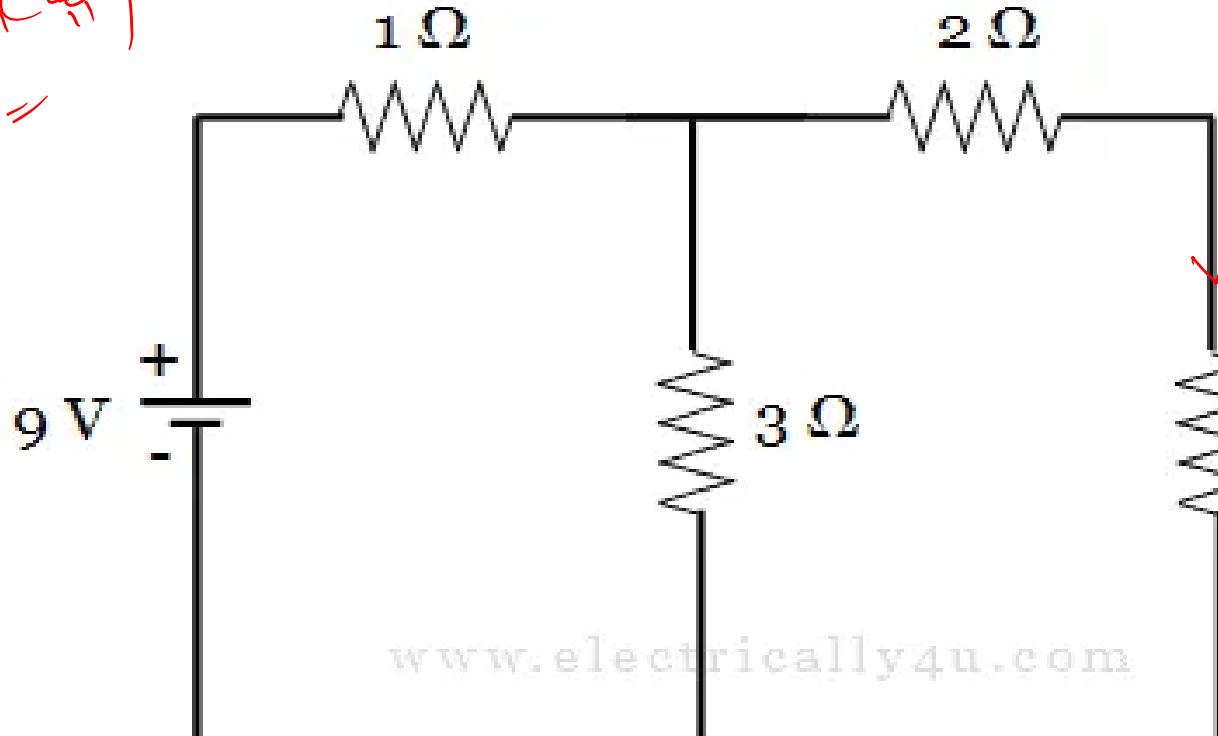
**For the given circuit, determine the current flowing through  $10\ \Omega$  resistor using Norton's theorem.**

$$R_{eq} = \frac{3+2}{3+2} + 1 = \frac{6}{5} + 1 = \frac{6+5}{5} = 11/5 = 2.2\ \Omega$$

$$\begin{aligned} I_T &= \frac{V}{R_{eq}} = \frac{9V}{2.2\ \Omega} \\ R_{eq} &= \frac{V}{I_T} = \frac{9V}{4.09A} = 2.2\ \Omega \end{aligned}$$



Step 1)  $R_L = 10\ \Omega$   
shorted

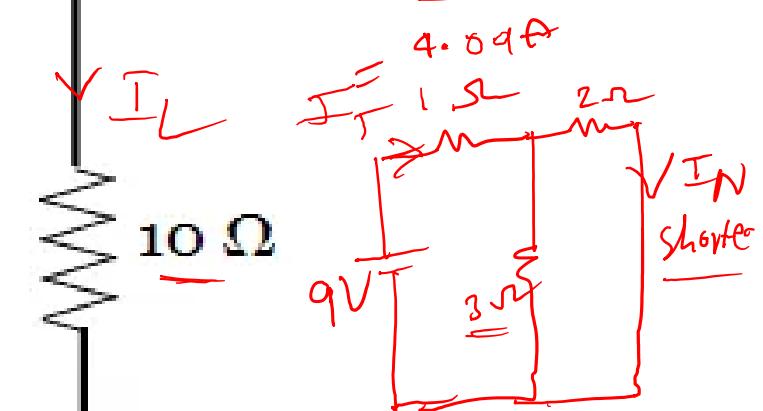

$$I_N = \frac{4.09 \times 3}{3+2} = 2.454A$$

# Norton's theorem





(a) To find Norton's current, Remove the load resistor( $10\ \Omega$ ), short it with a wire and the circuit is redrawn as below.

Step 1 - short Load terminals

Step 2 -  $R_{eq}$ ,  $V_{shorted\ I_{open}}$

Step 3 -  $I_T$

Step 4) -  $I_N$

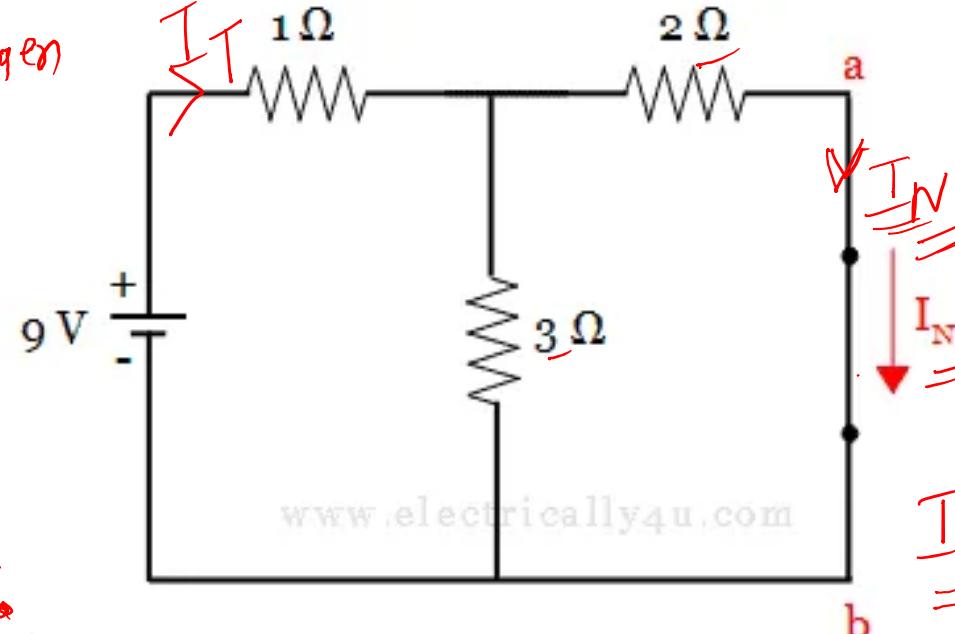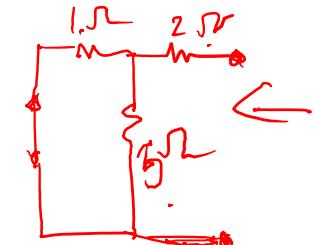

$$R_{eq} = \frac{1 \times 3}{1+3} + 2 = \frac{3}{4} + 2 = \frac{3+8}{4} = \frac{11}{4} = 2.75\ \Omega$$

Step 1  $I_N$

$$I_T = \frac{V}{R_{eq}} = \frac{9}{2.75} = 4.09\ A$$


$$I_L = \frac{2.75}{2.75+10} = \frac{2.75}{12.75} = 0.2145\ A$$

$$R_{eq} = \frac{3 \times 2}{3+2} + 1\ \Omega = 2.2\ \Omega$$

$$I_N = \frac{I_T \times 3}{3+2} = \frac{4.09 \times 3}{3+2} = 2.454\ A$$

$$I_N = \frac{4.09 \times 3}{3+2} = 2.454\ A$$

## Norton's theorem

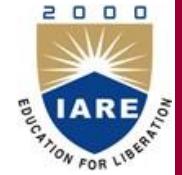

$$R_{eq} = 1 + \frac{3 * 2}{3 + 2} = 2.2\Omega$$

$$I_T = \frac{V_s}{R_{eq}} = \frac{9}{2.2} = 4.09A$$

# Norton's theorem



The current through the  $2\ \Omega$  resistor (or **Norton's current  $I_N$** ) is obtained by applying current division rule,



$$I_N = I_T * \frac{3}{3+2} = 4.09 * \frac{3}{5} = 2.454A$$

**(b) To find Norton's resistance**, Remove the load resistor, short the voltage source and circuit is redrawn as below.

open the current source

step 6)  $R_{eq}$  v-shorted  
 $I - 0.3A$   
open circuit
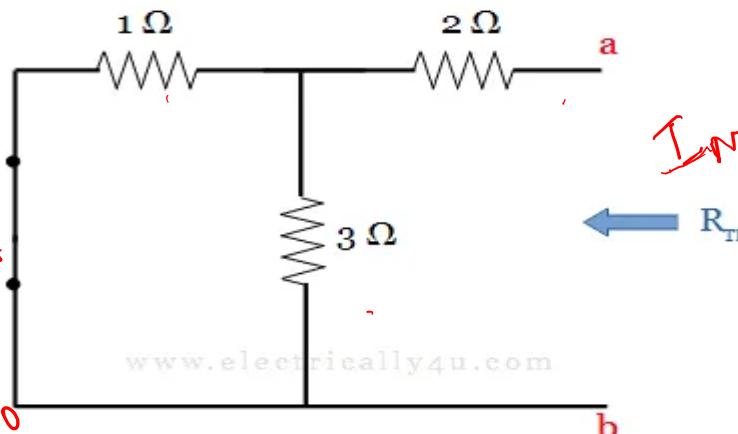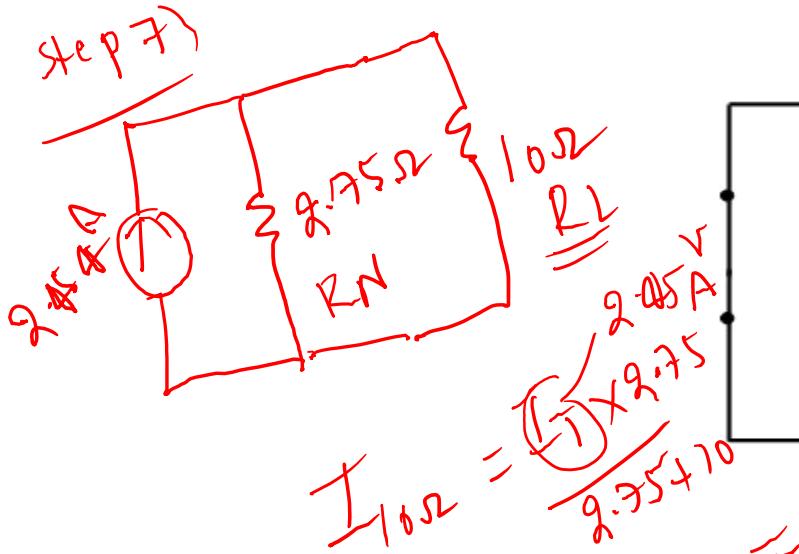
$$R_N = \frac{1 \times 3}{1+3} + 2 = 2.75\ \Omega$$



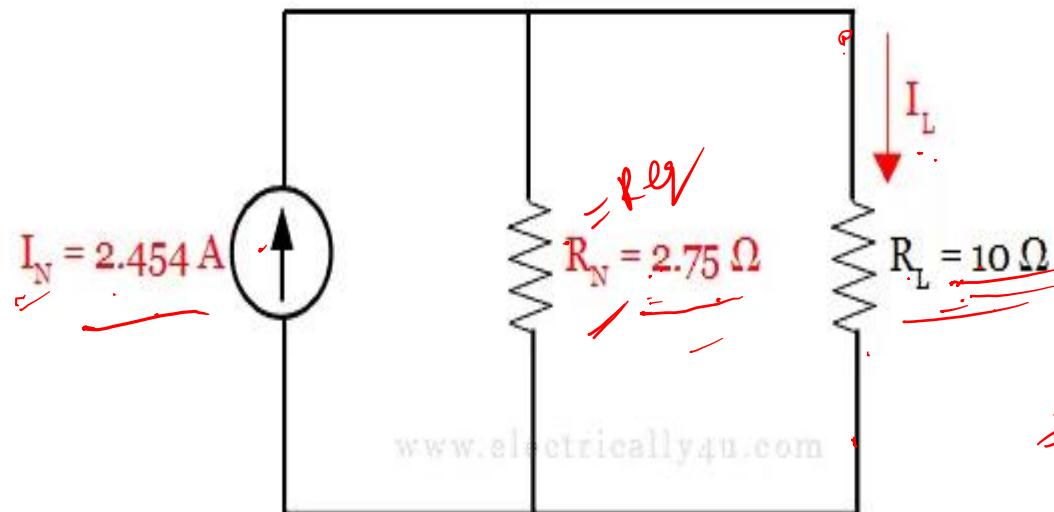
# Norton's theorem




$$R_N = 2 + \frac{1 * 3}{1 + 3} = 2.75\Omega$$

$$I_L = \frac{2.454 \times 2.75}{2.75 + 10} = \underline{\underline{0.529A}}$$



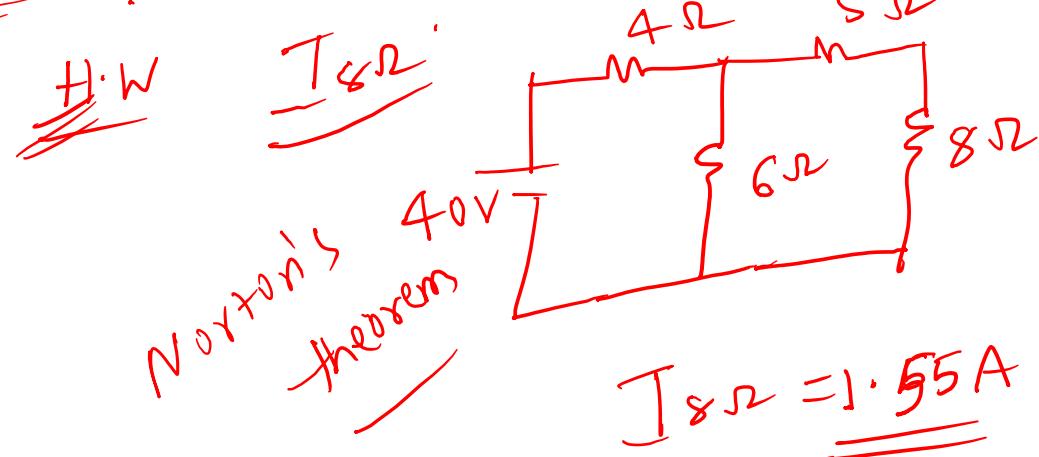
$$I_L = I_N * \frac{R_N}{R_N + R_L} = 2.454 * \frac{2.75}{2.75 + 10} = \underline{\underline{0.529A}}$$



# Norton's theorem



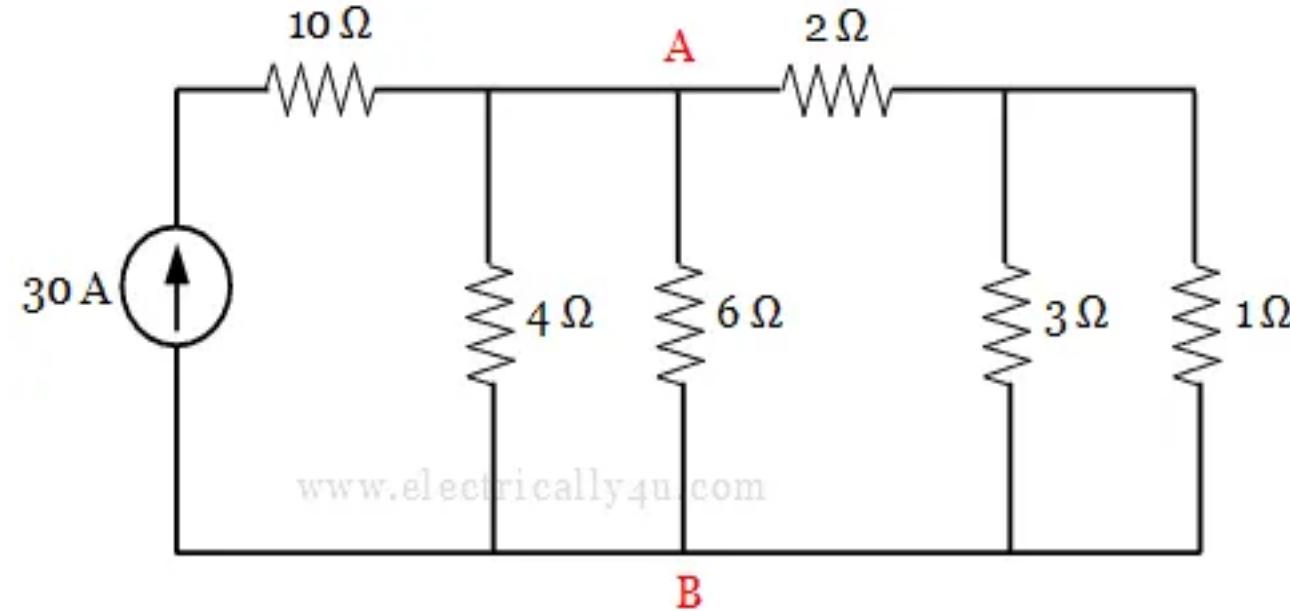
**Determine the current through AB in the given circuit using Norton's theorem.**




# Norton's theorem



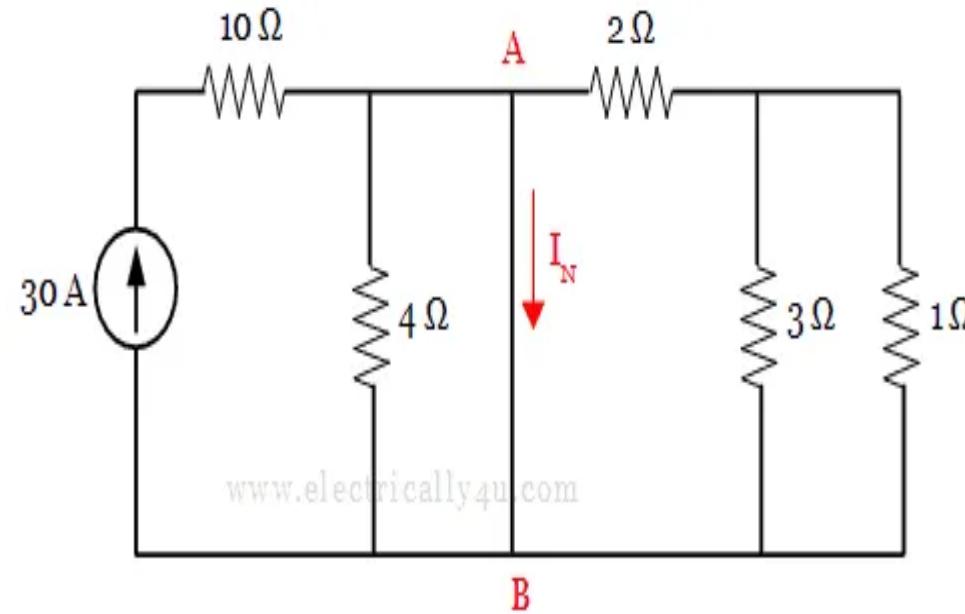**(a) To find Norton's current,** Remove the load resistor( $6\ \Omega$ ), short it with a wire and the circuit is redrawn as below.




# Norton's theorem

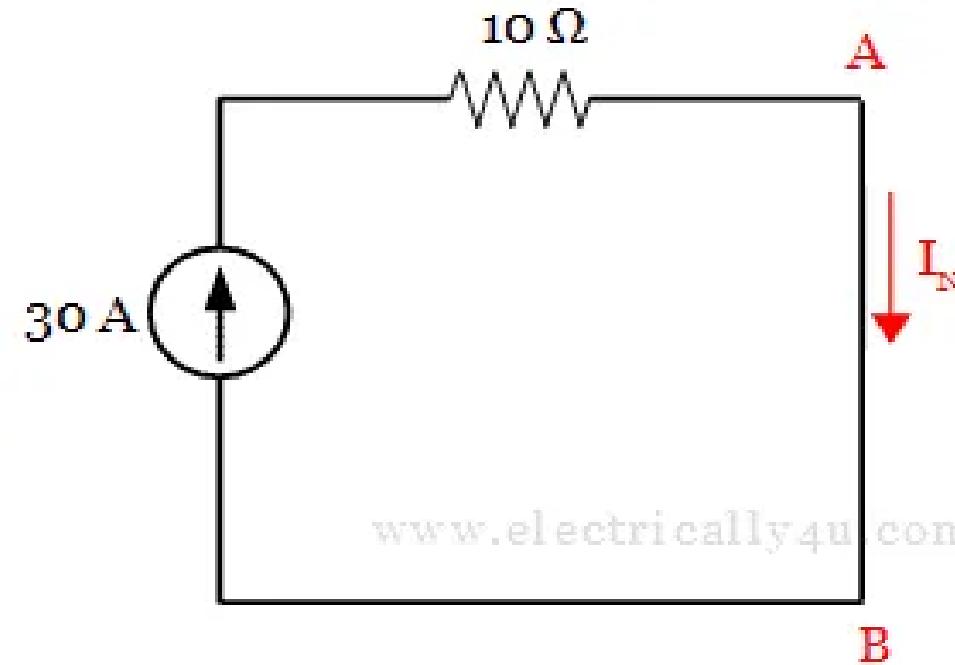



## Norton's theorem



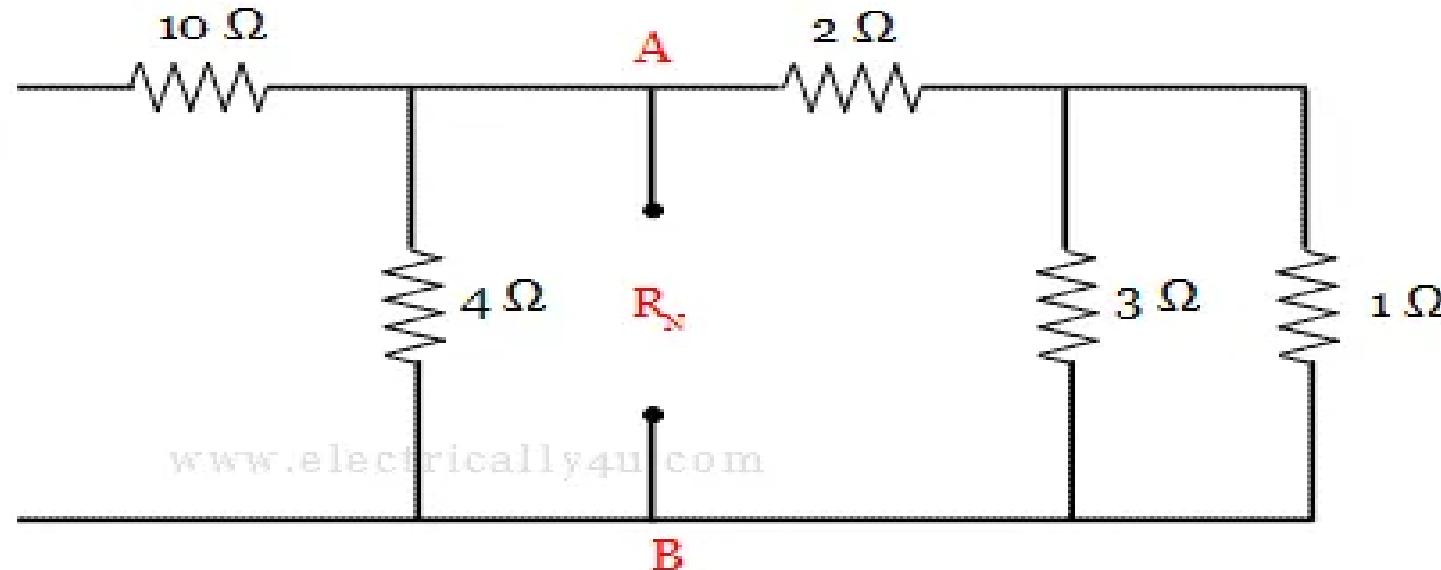**(b) To find Norton's resistance,** Remove the load resistor, open the current source and the resulting circuit is redrawn as below.



# Norton's theorem

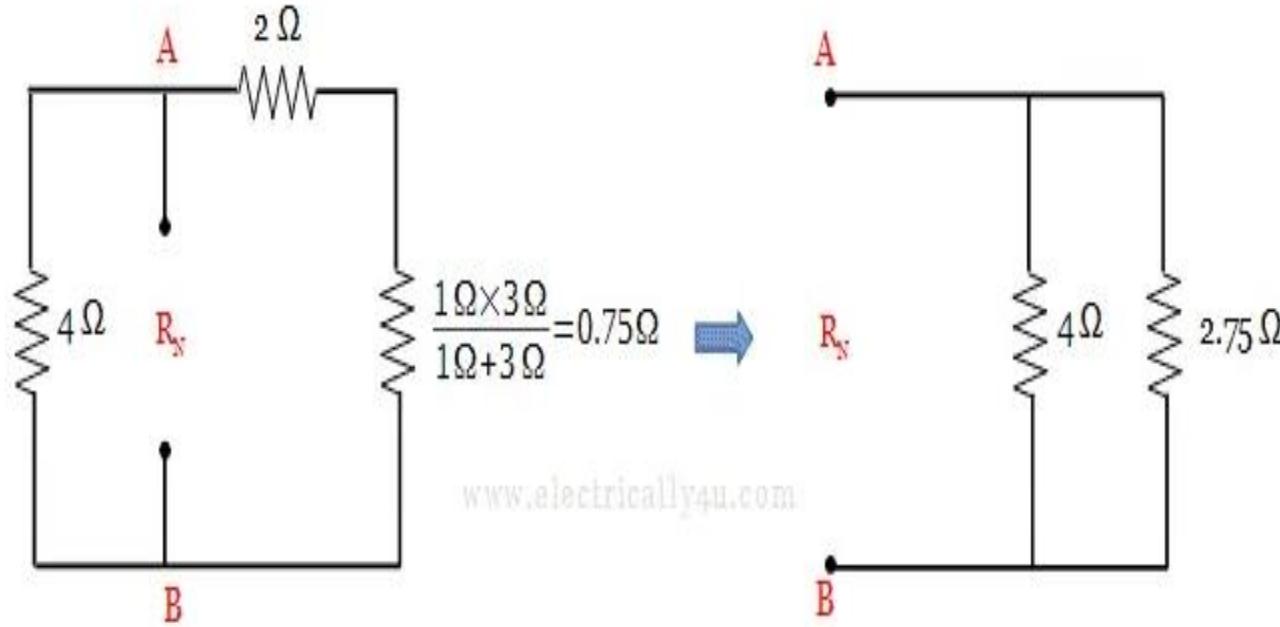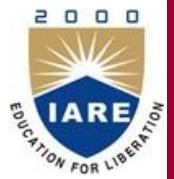


# Norton's theorem



$$R_N = \frac{4 * 2.75}{4 + 2.75} = 1.63\Omega$$

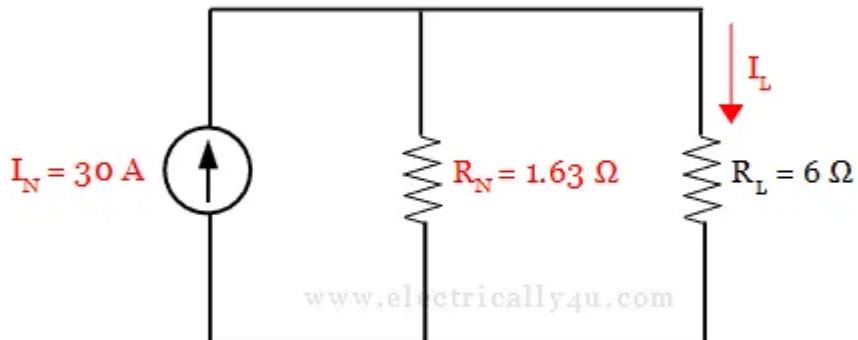**(c) Norton's Equivalent Circuit.** It is drawn by connecting Norton's voltage  $I_N$ , Norton's resistance  $R_N$  and load resistor in series, as shown below



$$I_L = I_N * \frac{R_N}{R_N + R_L} = 30 * \frac{1.63}{1.63 + 6} = 6.409\text{ A}$$


# Norton's theorem



# Norton's theorem



# Norton's theorem

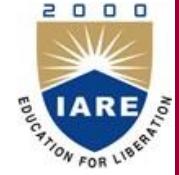


# Maximum Power Transfer Theorem




The maximum power transfer theorem is applicable to both AC and DC circuits. In any circuit, the maximum power drawn from the supply depends on the load.
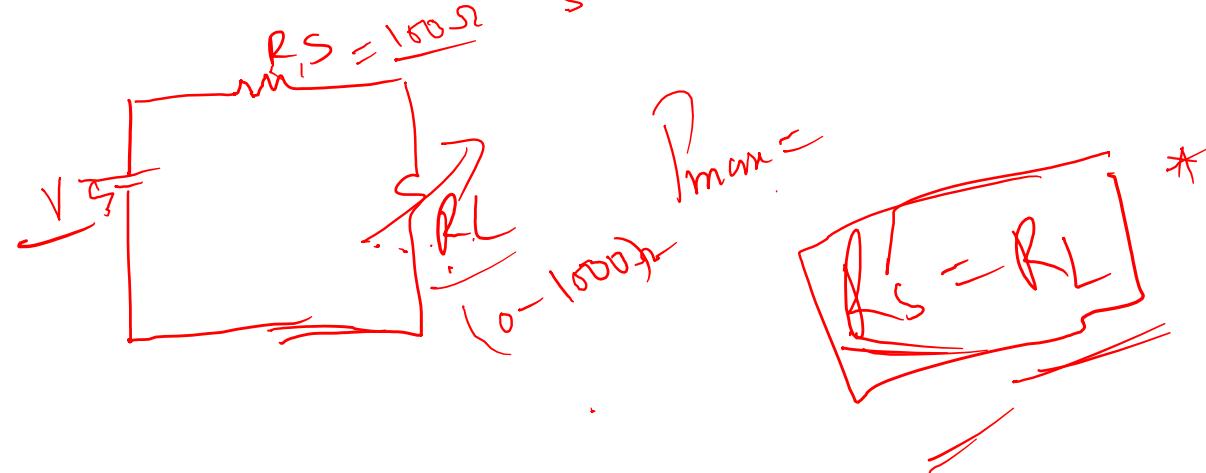
## Statement:

“In a linear, bilateral DC network, Maximum Power will be transferred to the load, when the load resistance is equal to the internal resistance of the source.”



# Maximum Power Transfer Theorem

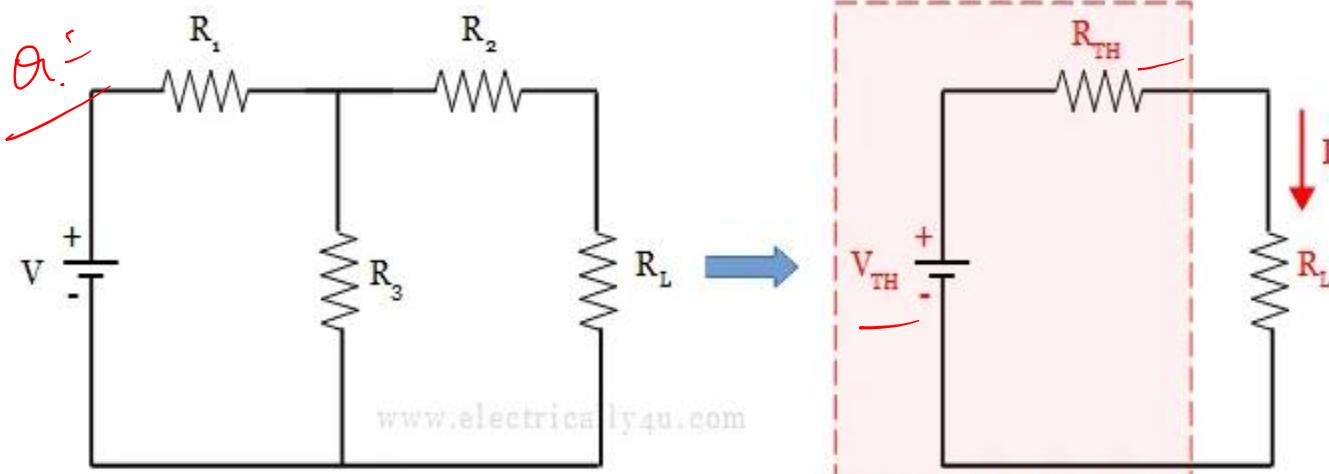

The power dissipated across the load resistor is given by,

$$P_L = I_L^2 \cdot R_L \dots \dots \dots (1)$$

The current through the load is given by,

$$I_L = \frac{V_{TH}}{R_{TH} + R_L}$$

Substitute the above expression in equation (1), we get,

$$P_L = \left( \frac{V_{TH}}{R_{TH} + R_L} \right)^2 \cdot R_L$$

## Maximum Power Transfer Theorem



$$P_L = V_{TH}^2 \cdot \left( \frac{R_L}{(R_{TH} + R_L)^2} \right) \quad \dots \dots \dots \quad (2)$$

the maximum power delivered depends on the value of load resistance  $R_L$ . Hence, to obtain the maximum power, the above expression is differentiated with respect to  $R_L$  and equate it to zero.

$$\frac{dP_L}{dR_L} = V_{TH}^2 \cdot \frac{d}{dR_L} \left[ \frac{R_L}{(R_{TH} + R_L)^2} \right] = 0$$

$$\Rightarrow V_{TH}^2 \cdot \left[ \frac{(R_{TH} + R_L)^2 * 1 - R_L * 2(R_{TH} + R_L)}{(R_{TH} + R_L)^4} \right] = 0$$

$$(R_{TH} + R_L)^2 - 2R_L(R_{TH} + R_L) = 0$$

$$(R_{TH} + R_L)[(R_{TH} + R_L) - 2R_L] = 0$$

$$(R_{TH} + R_L) - 2R_L = 0$$

$$R_{TH} = R_L$$

$$\begin{array}{l} R_S = R_L \\ \text{or} \\ R_{Th} = R_L \end{array}$$

## Maximum Power Transfer Theorem



Substitute  $R_{TH} = R_L$  in equation (2), we get,

$$P_{Max} = V_{TH}^2 \cdot \left[ \frac{R_{TH}}{(R_{TH} + R_{TH})^2} \right]$$

$\cancel{R_{TH}}$   $\cancel{R_{TH}}$   $\cancel{R_{TH}}$   $\cancel{R_{TH}}$


{  $R_{TH} = R_L$  }

$$P_{Max} = V_{TH}^2 \cdot \left[ \frac{R_{TH}}{4R_{TH}^2} \right]$$


$$P_{Max} = \frac{V_{TH}^2}{4R_{TH}}$$

✓ (87)  $P_{Max} = \frac{V_{TH}^2}{4R_L}$

# Maximum Power Transfer Theorem

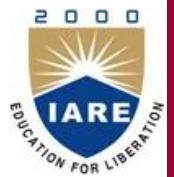


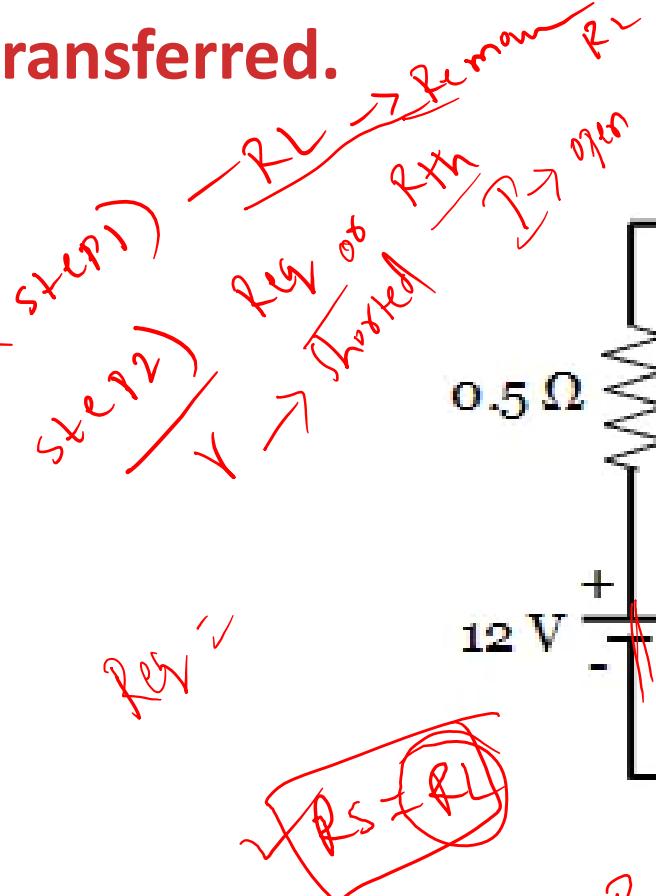Find the value of  $R_L$  at which maximum power is transferred to the load in the following circuit. Also, find the maximum power transferred.




[www.electrical4u.com](http://www.electrical4u.com)
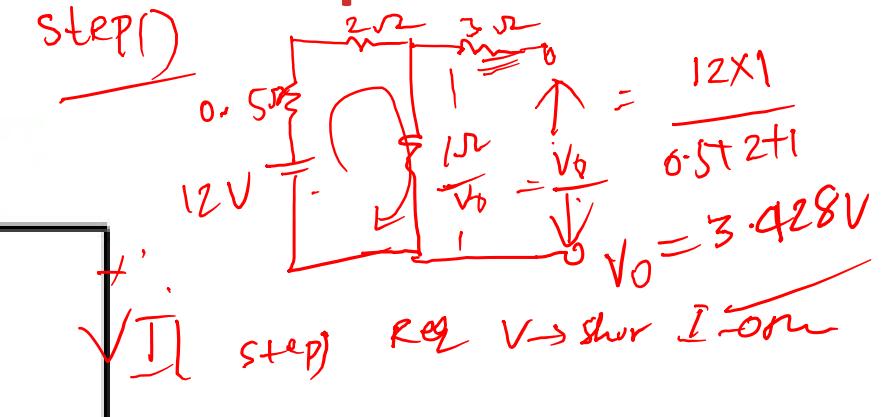
$$P_{max} = I_L^2 R_L = \frac{(0.46)^2 \times 3.714}{0.7912} = 3.428$$



$$\begin{aligned} V_o &= \frac{12}{0.5 + 2 + 1} \times 1 = 3.428V \\ I_L &= \frac{3.428}{3.714} \\ R_{th} &= 3.714 \\ P_{max} &= \frac{V_o^2}{4R_{th}} = \frac{3.428^2}{4 \times 3.714} = 0.461A \end{aligned}$$

# Maximum Power Transfer Theorem

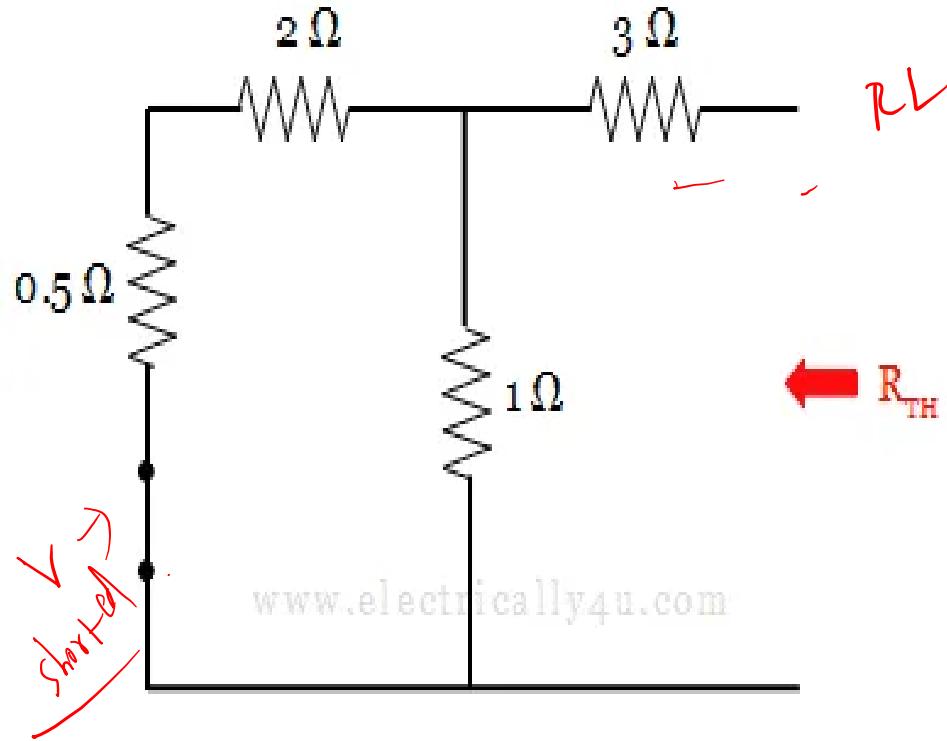

$$R_{TH} = \frac{1 * 2.5}{1 + 2.5} + 3 = 3.714\Omega$$


$$R_{TH} = R_L = 3.714\Omega$$

$$\frac{2.5+1}{2.5+1} \times 3 =$$

$$R_{eq} = R_{TH}$$


$$\text{Step 4) } V_{TH}$$

# Maximum Power Transfer Theorem

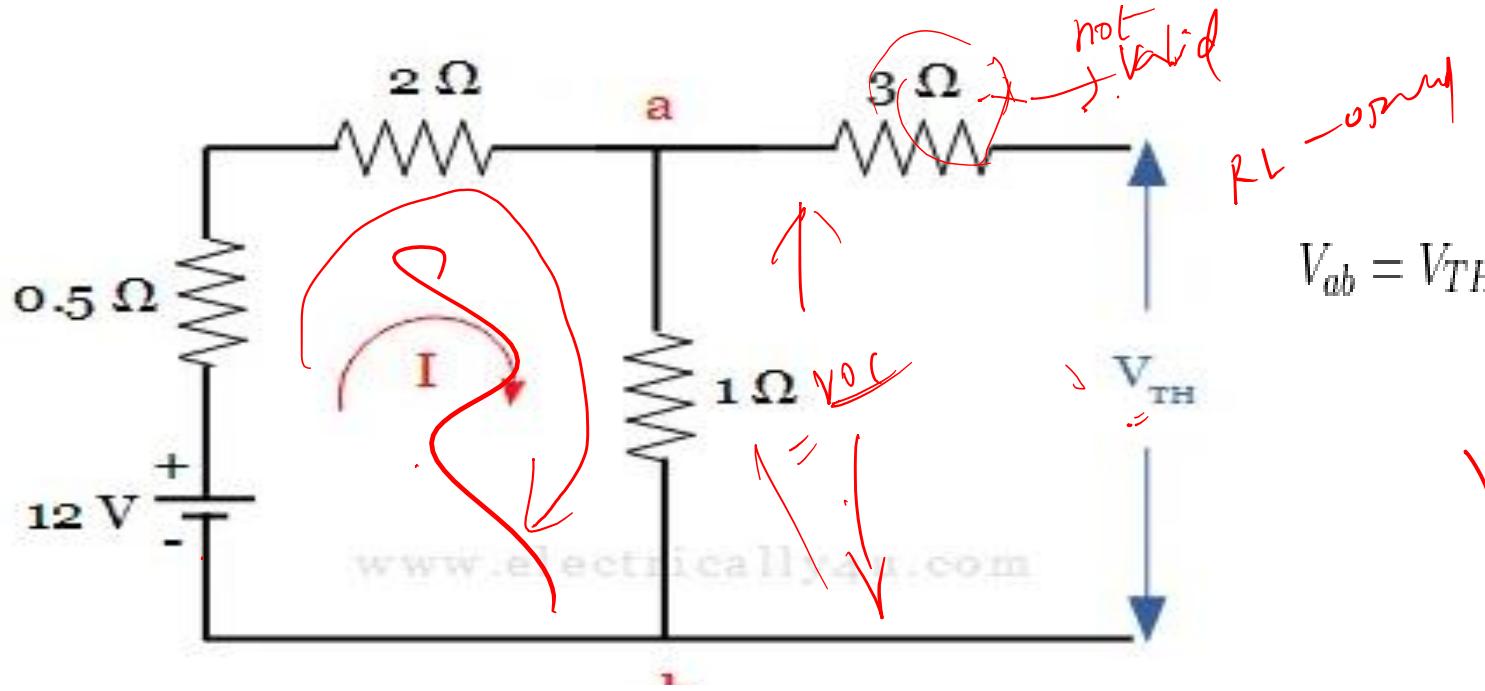

$$V_{ab} = V_{TH} = 3.428V$$
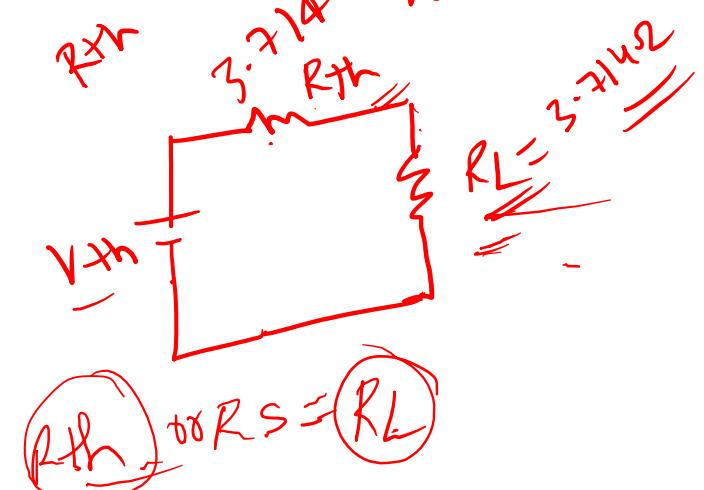
$$\text{or } V_{TH} = \frac{V_T \times 1}{0.5 + 2 + 1} = \frac{12 \times 1}{0.5 + 2 + 1} = 3.428V$$



Therefore, Maximum Power delivered to the load is given by,

$$P_{Max} = \frac{V_{TH}^2}{4R_{TH}} = \frac{3.428^2}{4 * 3.714} = 0.7912W$$


# Maximum Power Transfer Theorem



# Maximum Power Transfer Theorem



# Reciprocity Theorem

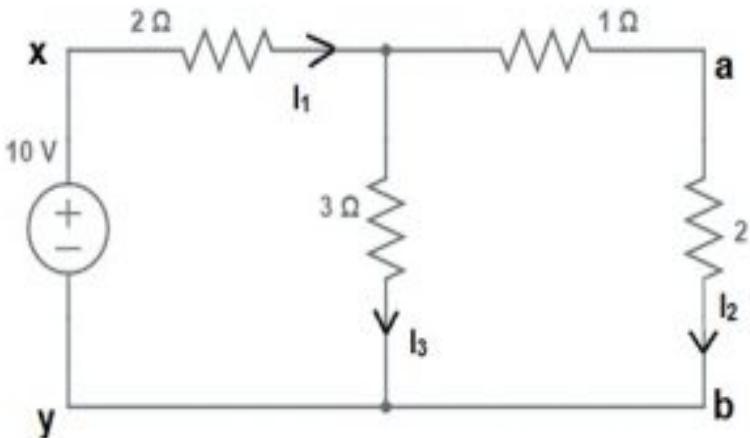

Equivalent resistance among x-y branch

$$R = [(2+1)||3] + 2$$

$$= (9/6) + 2 = ((12+9)/6) = 21/6 = 3.5 \text{ ohms}$$


So, current like 'I<sub>1</sub>'

$$10/3.5 \text{ A} \Rightarrow 2.86 \text{ A}$$

$$\text{Similarly, } I_2 = 2.86 \times (3/3+3) = 1.43 \text{ A}$$

$$I_3 = I_1 - I_2 = 2.86 - 1.43 = 1.43 \text{ A}$$

# Reciprocity Theorem

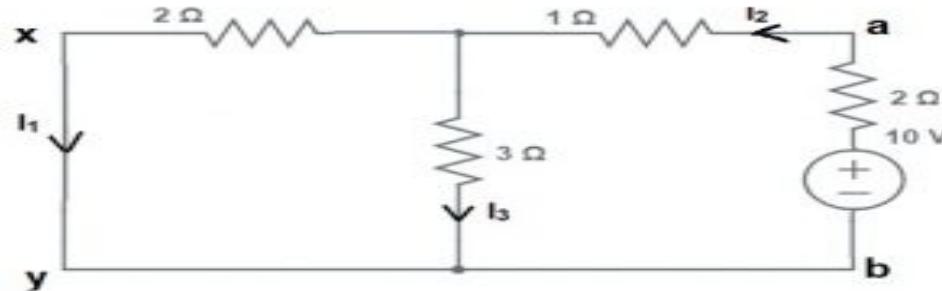

*Voltage Source is Changed*

Equivalent resistance across terminals x-y

$$R = (2||3/5) + 1+2$$


$$= (6/5) + 3 = 21/5 = 4.2 \text{ ohms}$$

$$I_2 = 10/4.2 \Rightarrow 2.34A$$

$$I_1 = I_2 \times (3/3+2)$$

$$= 2.384 \times (3/5) = 1.43A$$

## Reciprocity Theorem

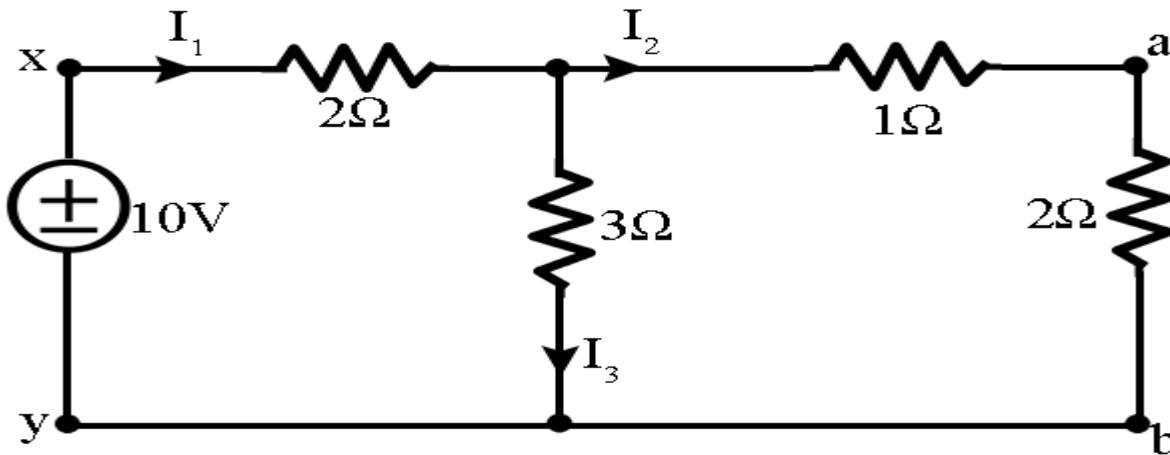

With the reference to figure 1,  
the equivalent resistance across  
x-y is given by


$$R_{eq} = [(2+1)||3] + 2 = 3.5\Omega$$

$$\therefore I_1 = \frac{10}{3.5} = 2.86A$$

$$I_2 = 2.86 \times \frac{3}{3+3} = 1.43A$$

$$I_3 = 2.86 - 1.43 = 1.43A$$

## Reciprocity Theorem

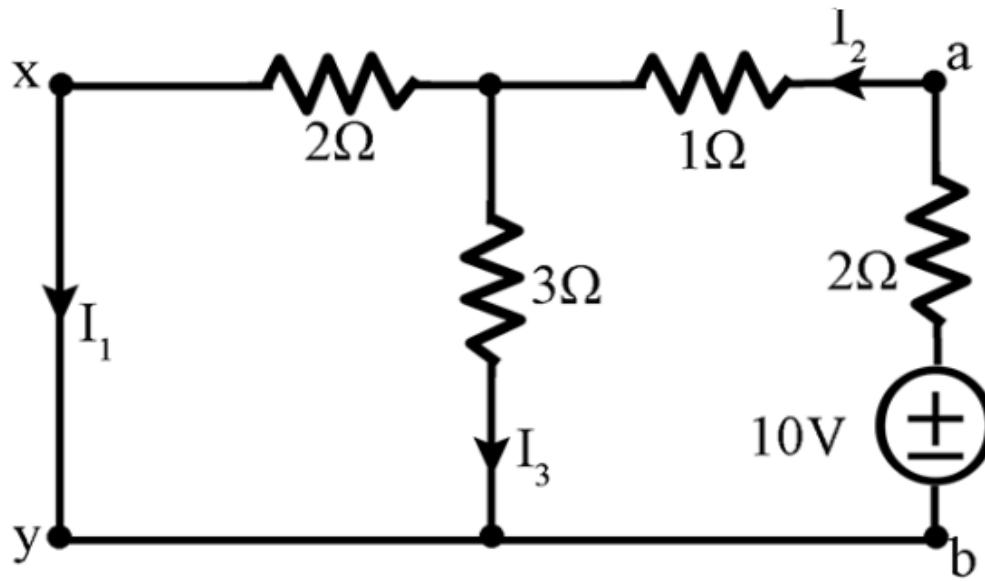


$$R_{eq} = (2\parallel 3) + 1 + 2 = \frac{6}{5} + 3 = \frac{21}{5} = 4.2\Omega$$

$$\therefore I_2 = \frac{10V}{4.2\Omega} = 2.381A$$

This gives

$$I_1 = I_2 \frac{3}{3+2} = 2.381 \times \frac{3}{5} = 1.43A$$

# Reciprocity Theorem

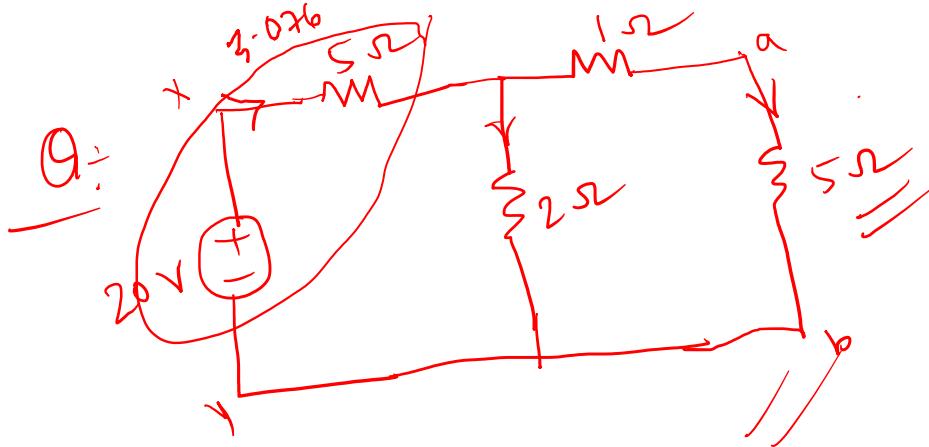


APPLY Reciprocity theorem find the

Response through  $5\Omega$

$$R_{eq} = 6.5\Omega$$

$$I = \frac{20}{6.5} = 3.076A$$

$$I_{5\Omega} =$$

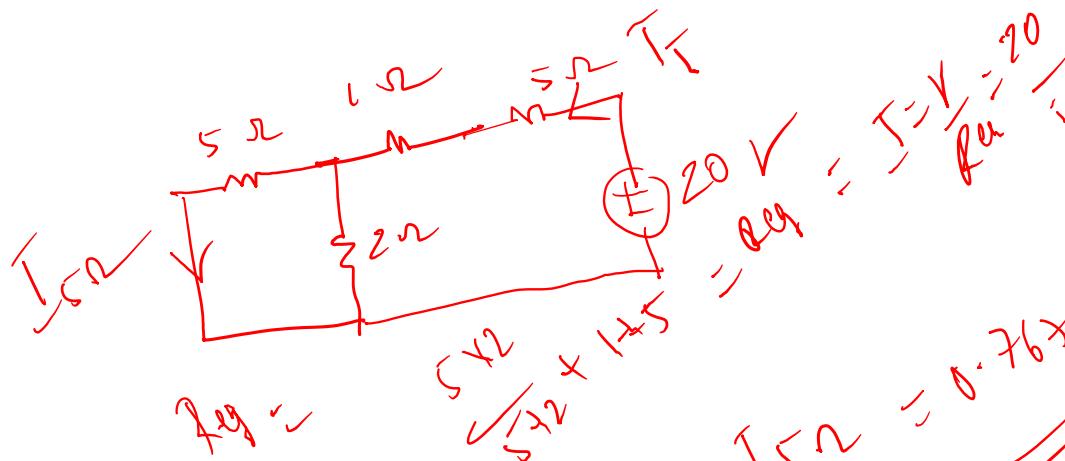

$$I_{5\Omega} = \frac{I(5+2)}{2+1+5} = 0.767A$$

$$I_{2\Omega} = I - I_{5\Omega}$$

$$= 3.076 - 0.767$$

$$I_{2\Omega} = \frac{2.31A}{2.3\Omega}$$

$$I_{2\Omega} = \frac{I(5+2)}{5+2} = 0.767A$$

## **What is Network Topology:**

Network topology is arrangement of various elements (links, nodes ,etc.) of a electrical network such that there is no distinction between different types of physical elements of network

**Why we need to learn Network Topology:** When a circuit is non planar or complicated with large number of nodes and closed paths, then conventional methods like KCL , KVL , Nodal analysis, Mesh analysis etc becomes highly difficult. Analysis of such networks can be done conveniently using network topology.


**Where do we apply Network Topology:** Network topology is used to analyze voltage and currents across various branches of an electrical circuit (more particularly complicated circuit)

## Basic Definitions



- **Node**
- **Essential Node**
- **Branch**
- **Loop**
- **Mesh**
- **Graph**



# Node

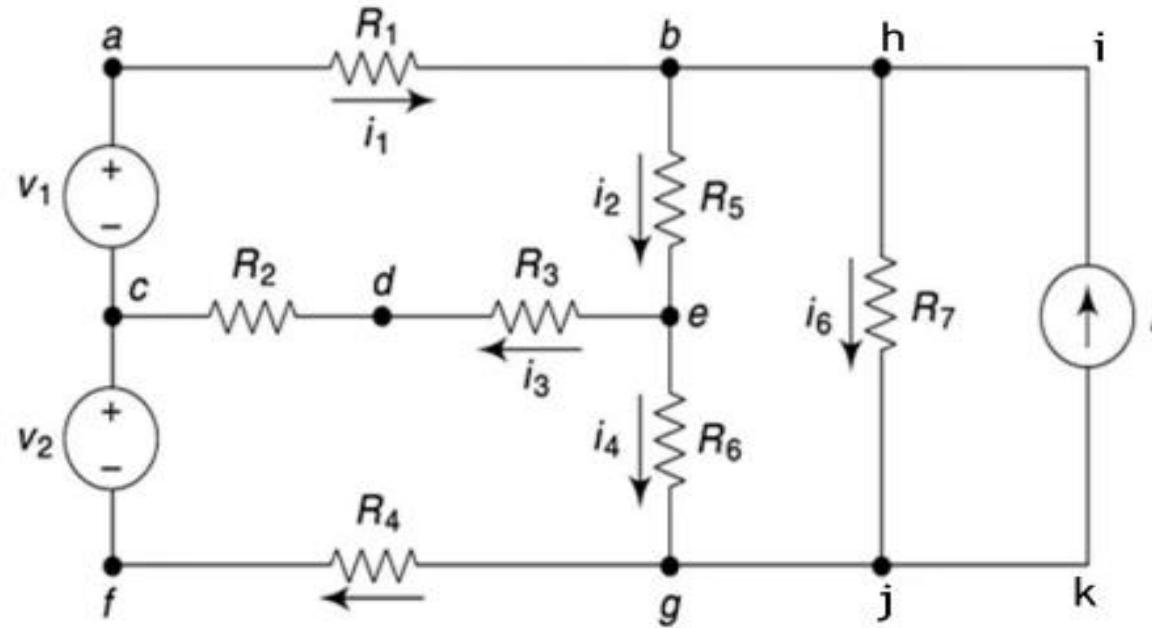

Circuit illustrating terminologies

- A node is a point in a circuit where two or more circuit elements join .
- The number of branches incident to that node is the degree of its node 07 a,b, c, d, e, f and g


## Essential Node

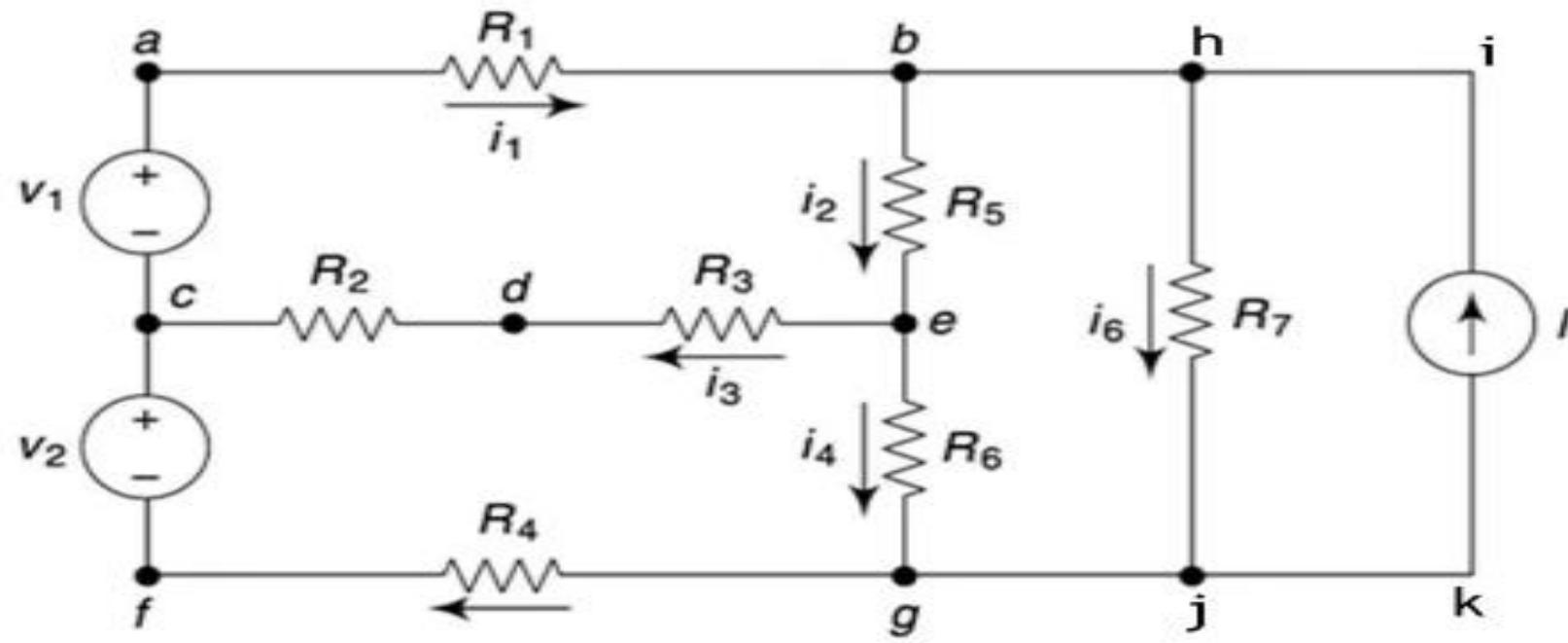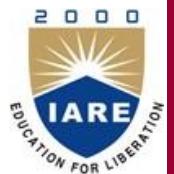

Circuit illustrating terminologies

A node that joins three or more elements. 04 b, c,e and g


# Branch

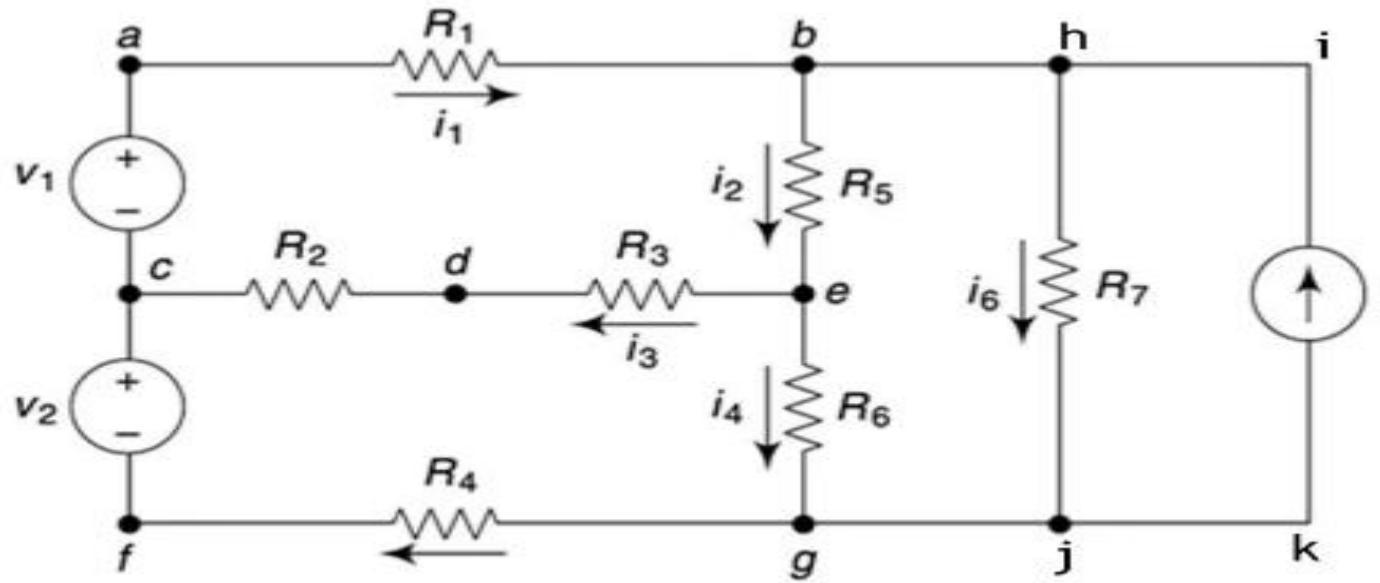

**Circuit illustrating terminologies**

Branch A single path containing one circuit element that connects one node to other and is represented by solid line  
10 V1,R1,R2,R3,V2,R4,R5,R6,R7and I

# Loop

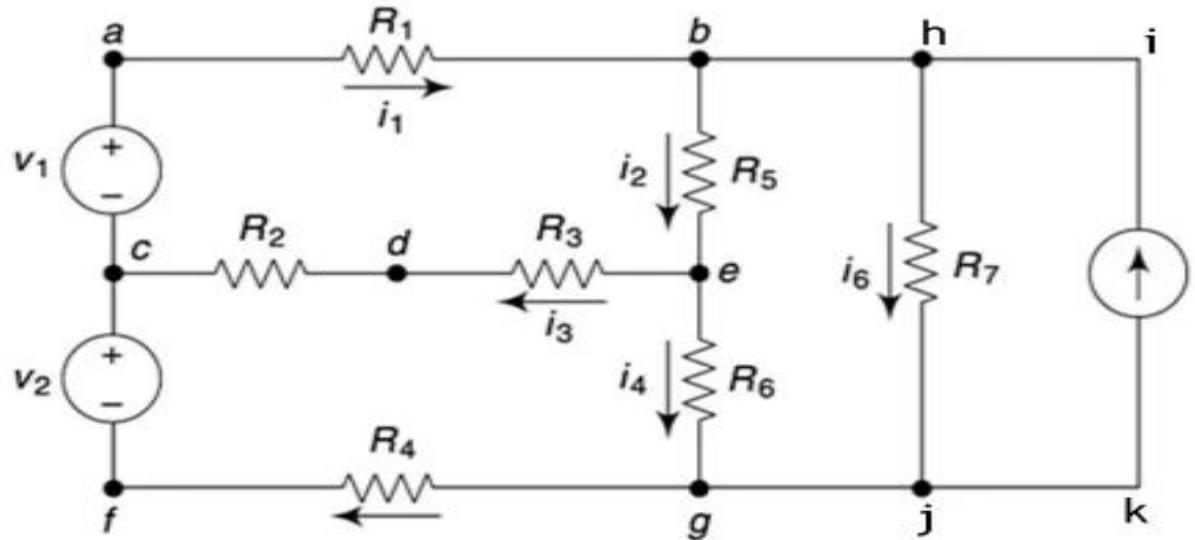


Circuit illustrating terminologies

Loop A loop is a closed path, i.e., it starts at a selected node, traces a set of connected basic circuit elements and returns to the original starting node without passing through any intermediate node more than once.

11 abhikjgfca ,abhjgfca,abegfca abedca,cdegfc cdebhikjgfc ,cdebhjgfc gebhjg ,jhik, abhjgedca, abhikjgedca

# Mesh

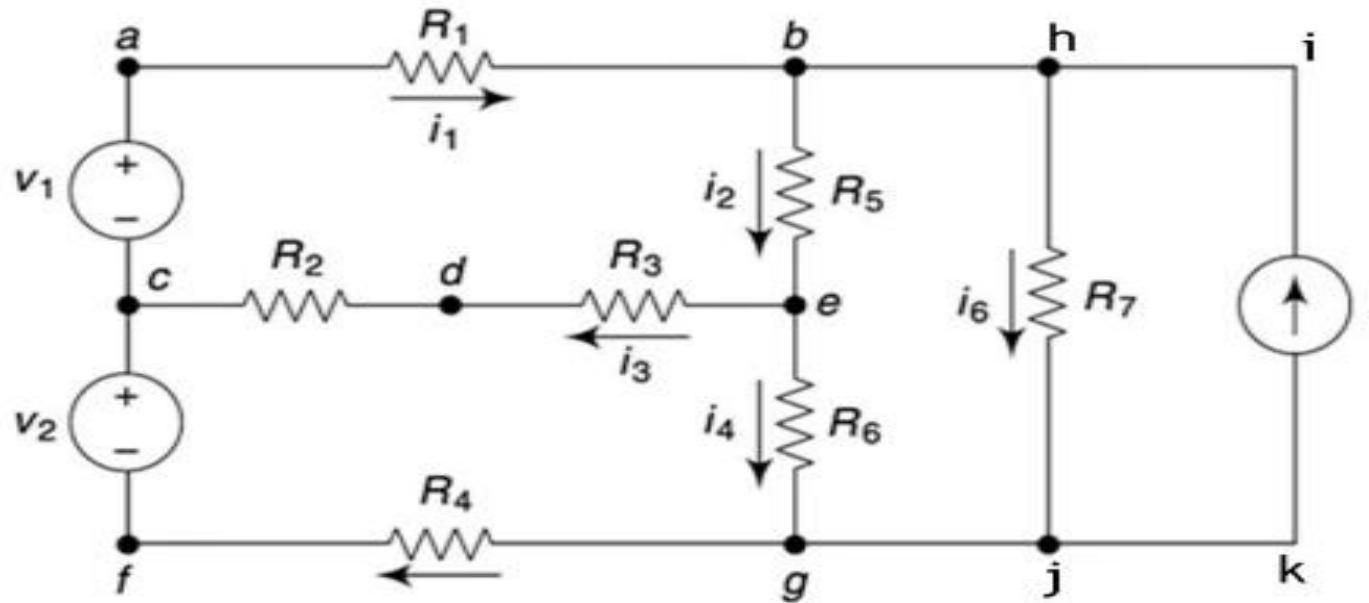

Circuit illustrating terminologies

Mesh A mesh is a special type of loop which does not contain any other loops within it. 04 abedca,cdegfc, gebhjg ,jhik

# Graph

Graph A graph corresponding to a given network is obtained by replacing all circuit elements with lines



# Network Topology



- Graph
- Oriented Graph
- Rank of a graph Graph
- Planar and non - planar graph Planar Graph
- Tree and twings
- Co tree and Links(Chords)



### Graph ,Oriented Graph & Rank of a graph Graph :

- A graph corresponding to a given network is obtained by replacing all circuit elements with lines.
- Rank of a Graph : If there are ‘n’ nodes in a graph then rank of the of the graph is  $(n-1)$
- Oriented Graph: If each of the line/branch of the graph has a reference direction [as indicated by an arrow mark],then the resulted graph is called oriented or directed graph


Steps for drawing oriented graph:

1. Replace all resistors , inductors and capacitors by line segments
2. Replace voltage source by short circuit and current sources by open circuit
3. Assume directions of branch currents
4. Name all the nodes and branches


# Network Topology

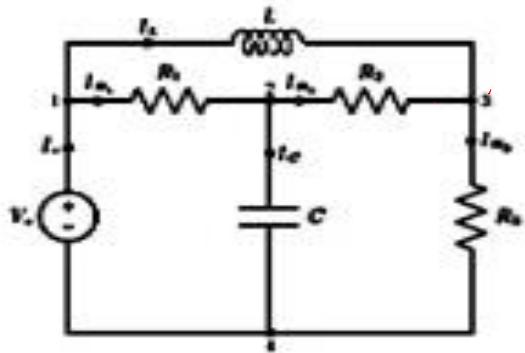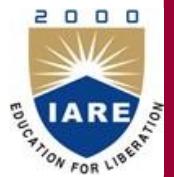




i) A Circuit

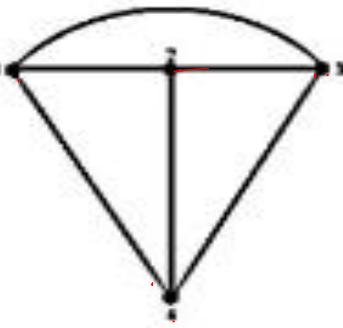

ii) its graph




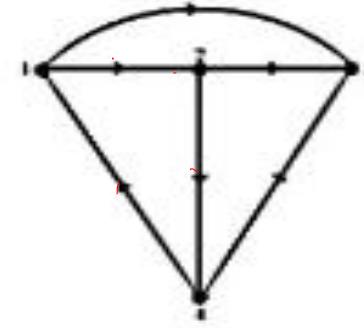


iii) directed graph

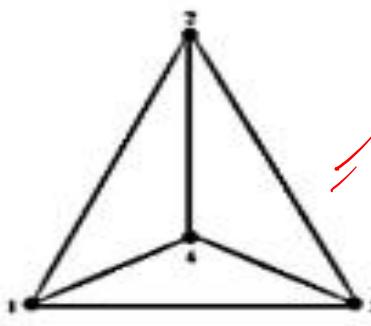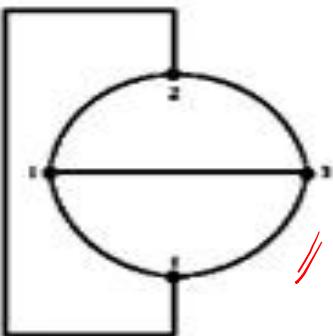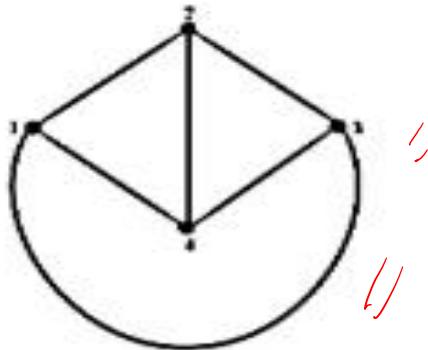

Three topologically equivalent graphs of figure ii).

# Network Topology

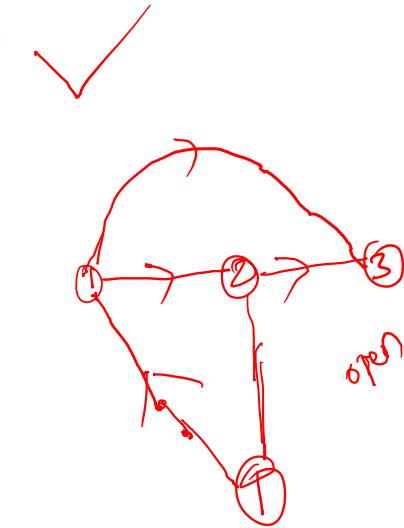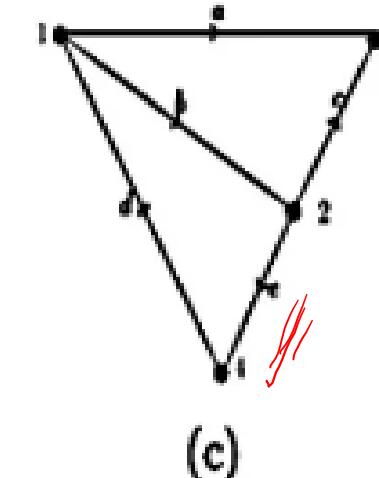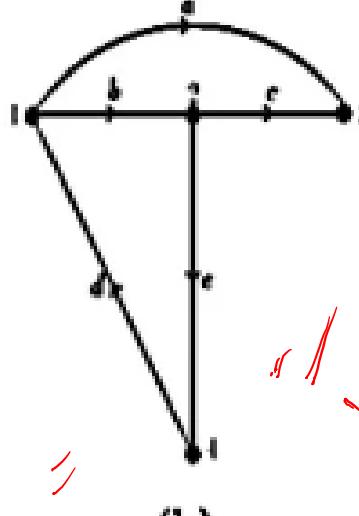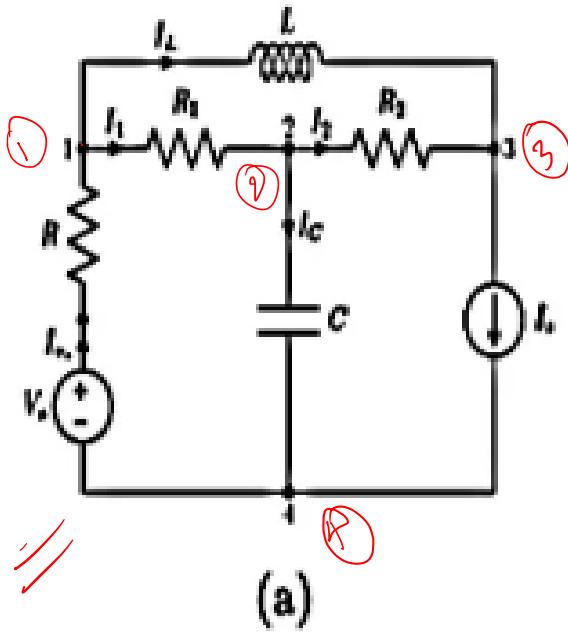


(a) A circuit, and (b),(c) its directed graphs.

Planar and non - planar graph Planar Graph :
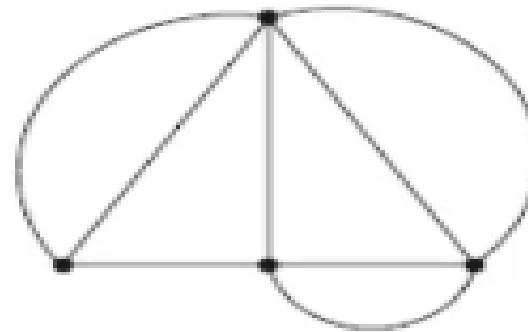
### Planar Graph:


A graph drawn on a 2 - dimensional plane is said to be planar if two branches do not intersect or cross at a point which is other than a node .



***Planar graph***
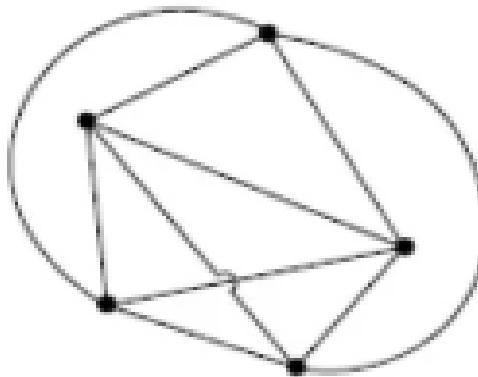
## Non Planar Graph :

A graph drawn on a 2 - dimensional plane is said to be planar if two branches intersect or cross at a point which is other than a node .




***Non-planar graph***

**Path** : A set of elements that may be traversed in order without passing through the same node twice.

**Sub Graph** : It is a sub set of branches and nodes of a graph.

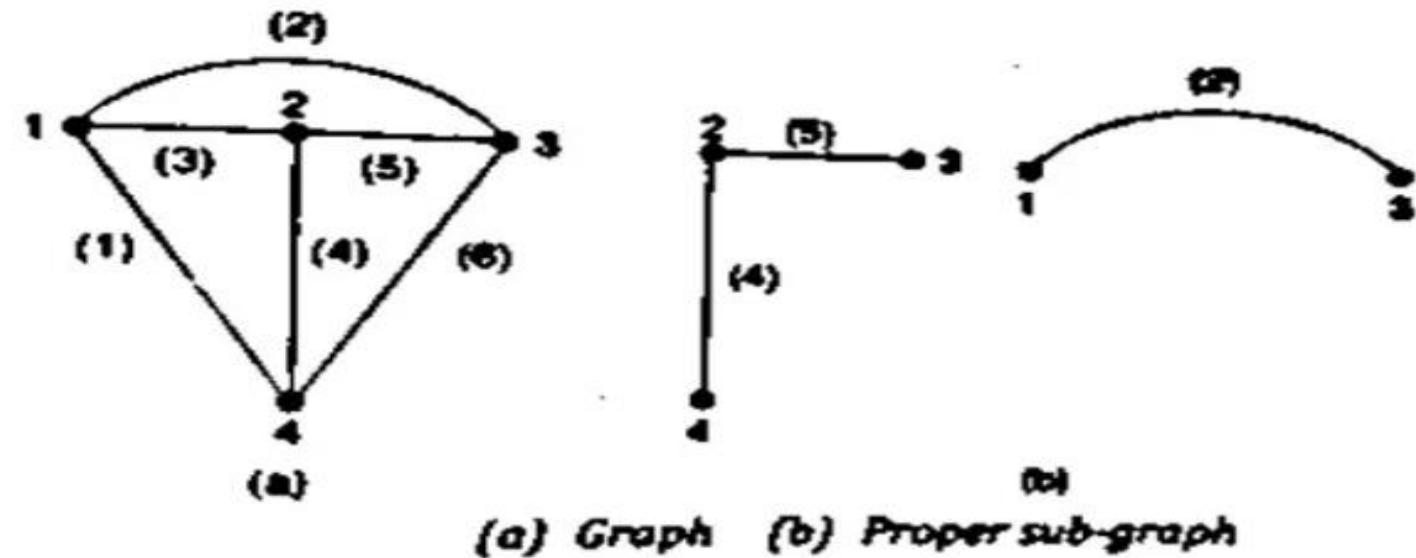It is a proper sub-graph if it contains branches and nodes less than those on a graph. A sub graph can be just a node or only one branch of the graph.



# Tree



A tree is a connected subgraph of a network which consists of all the nodes of the original graph but no closed paths.

The graph of a network may have a number of trees.


The number of nodes in a graph is equal to the number nodes in the tree.




# Tree

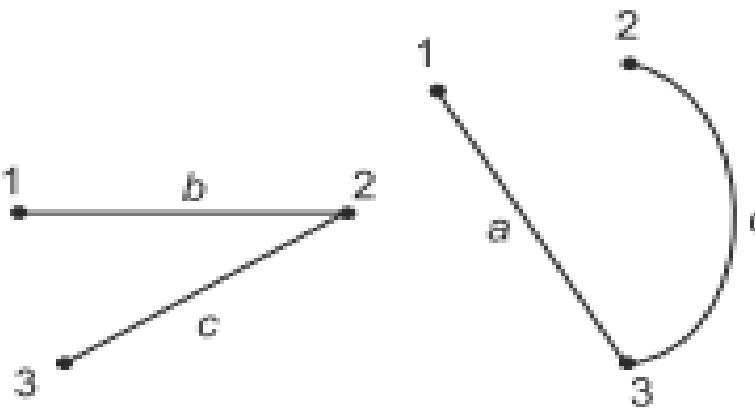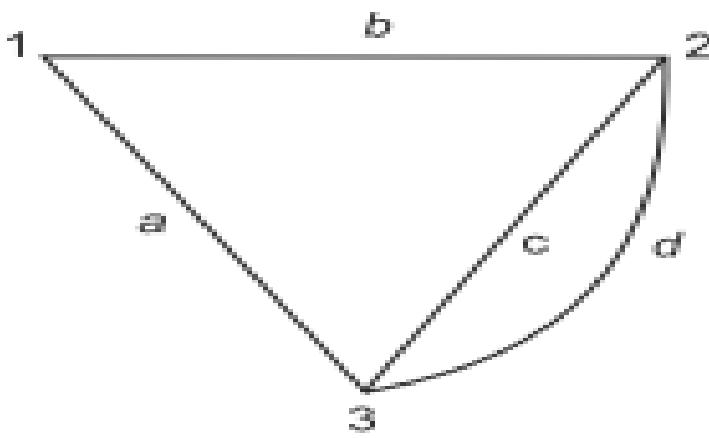


(a)

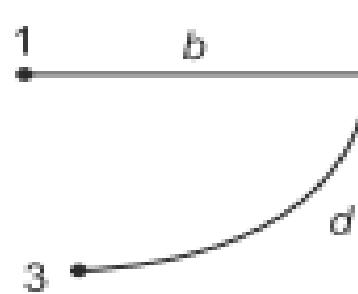


(b)

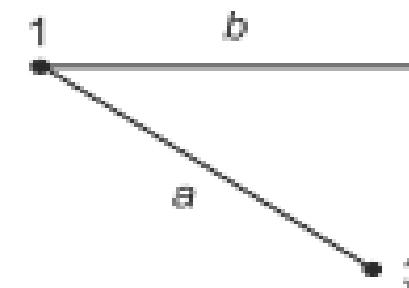

(c)

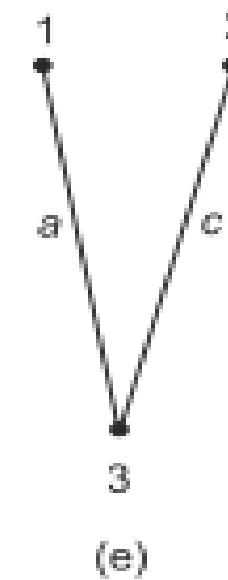

(d)

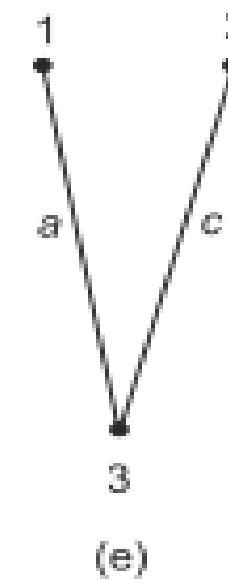

(e)

# Tree


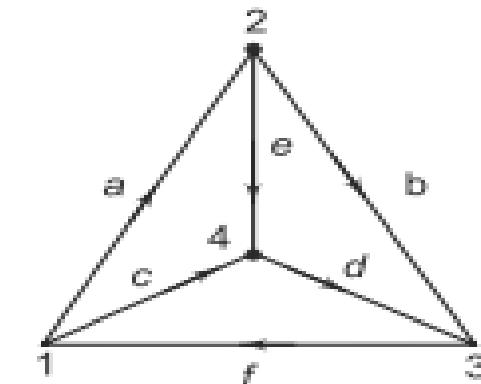


Fig. 2.7



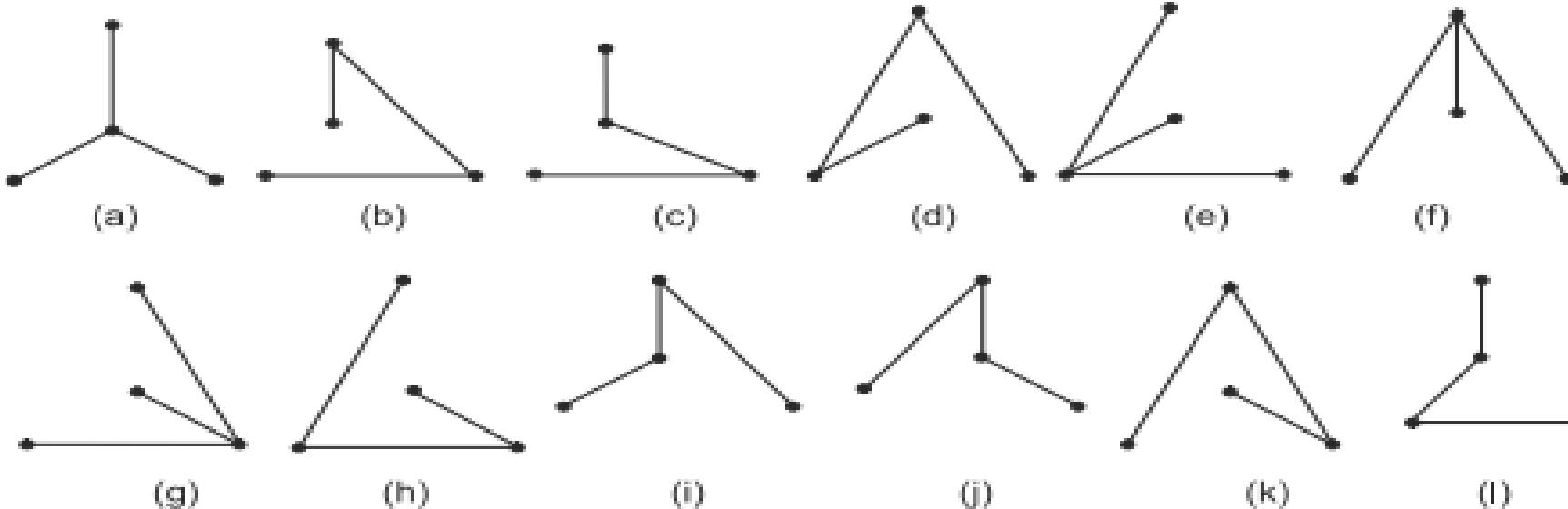


**Tree & Twigs :** A connected sub graph having all the nodes of a graph without any loop is called a tree and branches of a tree are called twigs.

## Properties of Tree .

- There exists only one path between any pair of nodes in a tree
- A tree contains all nodes of the graph
- If  $n$  is the number of nodes of the graph, there are  $(n-1)$  branches in the tree
- Tree do not contain any loops
- Every connected graph has at least one tree
- The minimum terminal nodes in a tree are two


## Tree

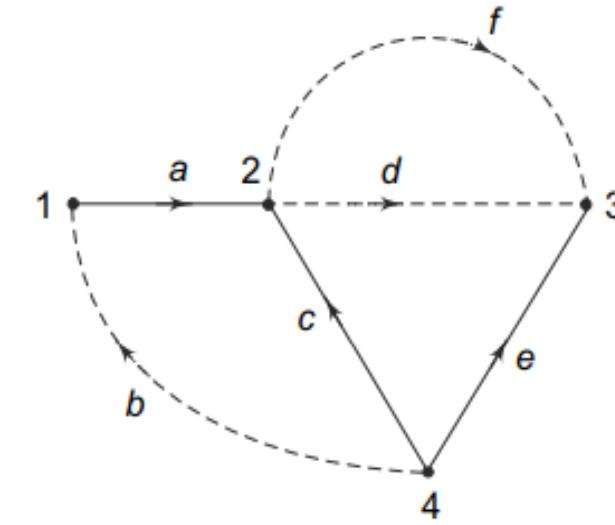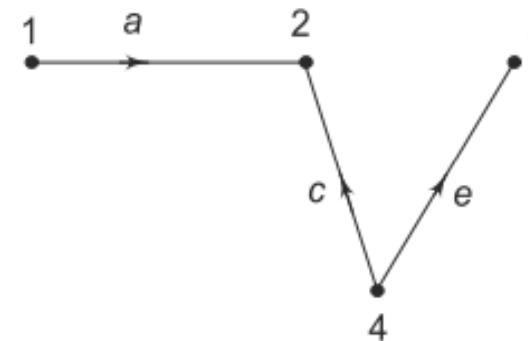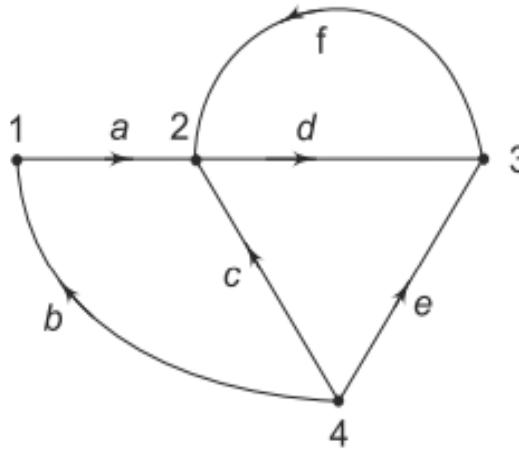


The branches a, c, and e are the twigs while the branches b, d, and f are the links of this tree. It can be seen that for a network with  $b$  branches and  $n$  nodes, the number of twigs for a selected tree is  $(n - 1)$  and the number of links  $l$  with respect to this tree is  $(b - n + 1)$ .

The number of twigs  $(n - 1)$  is known as the tree value of the graph. It is also called the rank of the tree.

# Tree and Twigs of graph

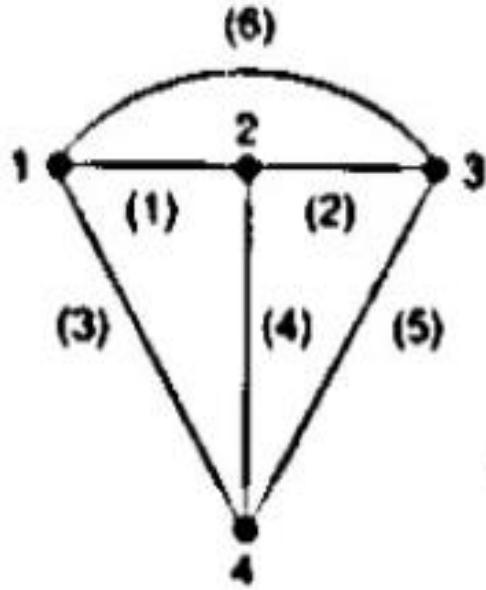


(a) Graph

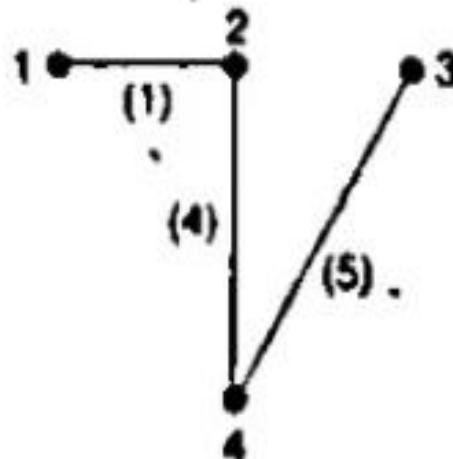

(b)


Twigs: {1, 4, 5}

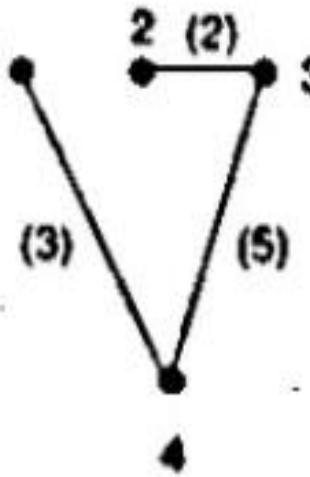










(c)

Twigs: {2, 3, 5}



# Tree and Twigs of graph

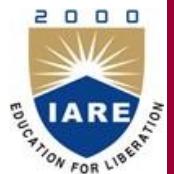

Identify Trees in the graph

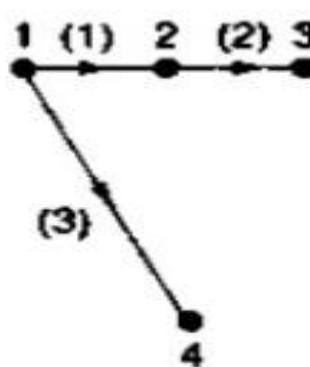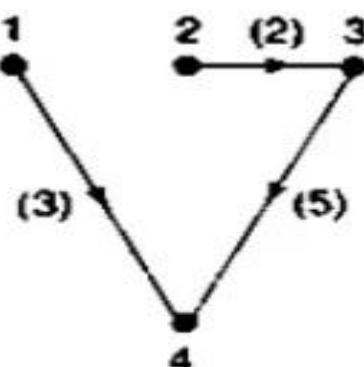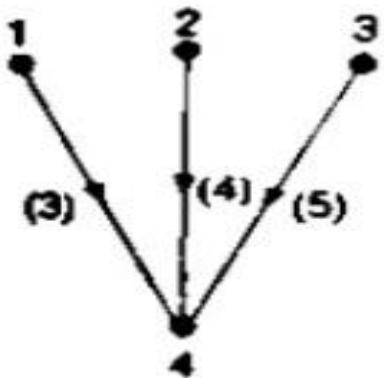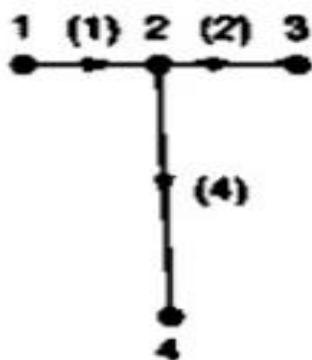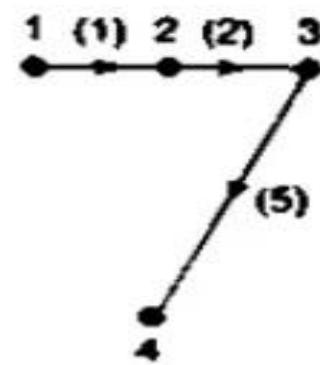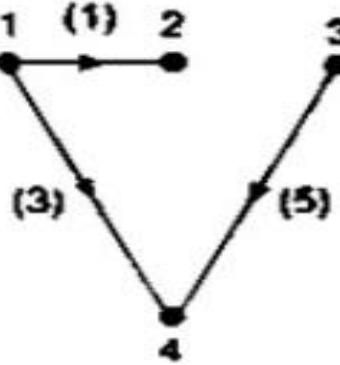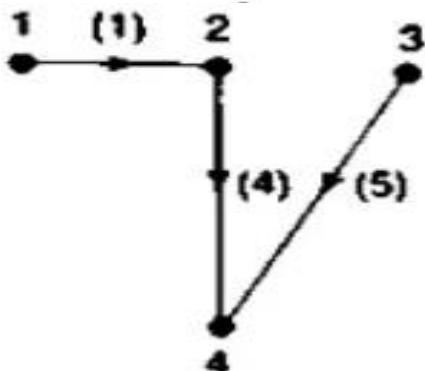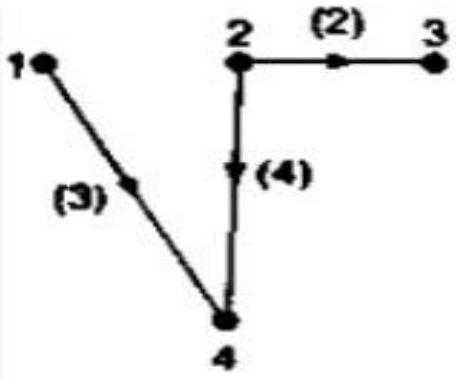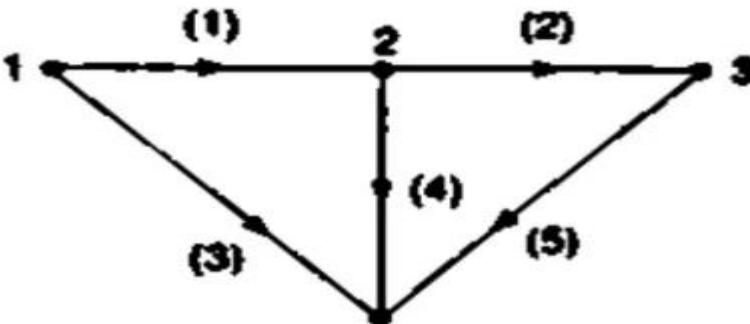

# Tree and Twigs of graph

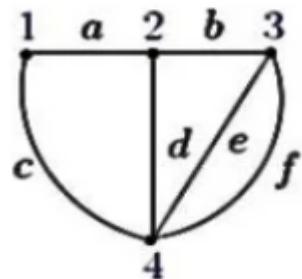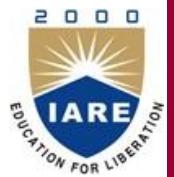

Tree	Twigs of tree	Links of cotree
	{a,b,d}	{c,e,f}
	{a,d,f}	{c,b,e}

## Incidence Matrix




In the matrix  $A$  with  $n$  rows and  $b$  columns, an entry  $a_{ij}$  in the  $i$ th row and  $j$ th column has the following values.

$a_{ij} = 1$ , if the  $j$ th branch is incident to and oriented away from the  $i$ th node.

$a_{ij} = -1$ , if the  $j$ th branch is incident to and oriented towards the  $i$ th node.

$a_{ij} = 0$ , if the  $j$ th branch is not incident to the  $i$ th node.

# Incidence Matrix

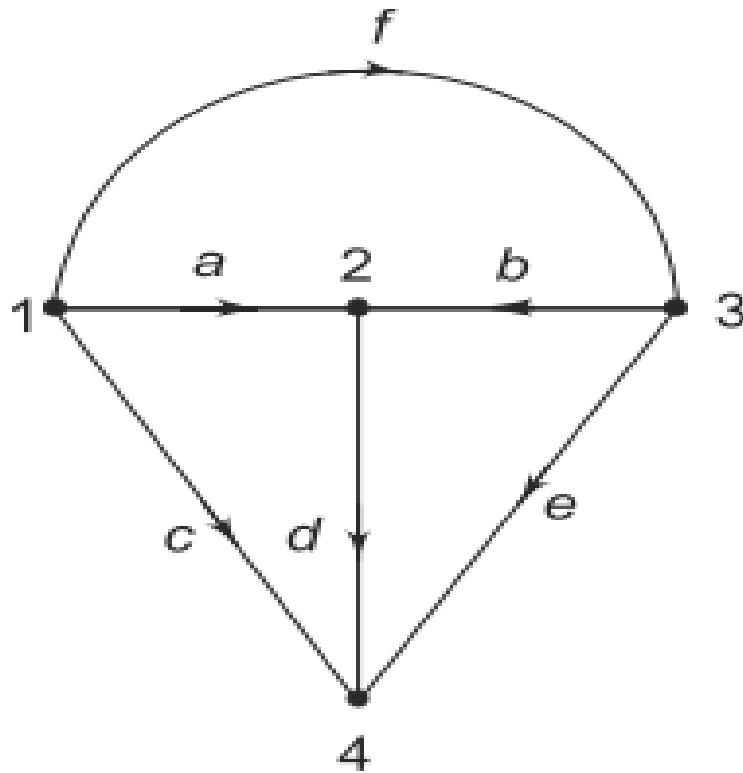


nodes  $\downarrow$       branches  $\rightarrow$

$$A = \begin{bmatrix} 1 & 1 & 0 & 1 & 0 & 0 & 1 \\ 2 & -1 & -1 & 0 & 1 & 0 & 0 \\ 3 & 0 & 1 & 0 & 0 & 1 & -1 \\ 4 & 0 & 0 & -1 & -1 & -1 & 0 \end{bmatrix}$$

## PROPERTIES OF INCIDENCE MATRIX A



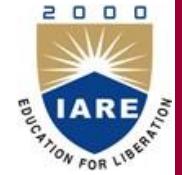1. Each column representing a branch contains two non-zero entries 1 and  $-1$ ; the rest being zero. The unit entries in a column identify the nodes of the branch between which it is connected.
2. The unit entries in a row identify the branches incident at a node. Their number is called the degree of the node.
3. A degree of 1 for a row means that there is one branch incident at the node. This is commonly possible in a tree.
4. If the degree of a node is two, then it indicates that two branches are incident at the node and these are in series.
5. Columns of A with unit entries in two identical rows correspond to two branches with same end nodes and hence they are in parallel.



6. Given the incidence matrix A, the corresponding graph can be easily constructed since A is a complete mathematical replica of the graph. 7. If one row of A is deleted the resulting  $(n - 1) \times b$  matrix is called the reduced incidence matrix.

## Incidence Matrix



In the matrix  $A$  with  $n$  rows and  $b$  columns, an entry  $a_{ij}$  in the  $i$ th row and  $j$ th column has the following values.

$a_{ij} = 1$ , if the  $j$ th branch is incident to and oriented away from the  $i$ th node.


$a_{ij} = -1$ , if the  $j$ th branch is incident to and oriented towards the  $i$ th node.

$a_{ij} = 0$ , if the  $j$ th branch is not incident to the  $i$ th node.

## Incidence Matrix



	$e_1$	$e_2$	$e_3$	$e_4$	$e_5$	$e_6$	$e_7$
$v_1$	1	0	0	0	0	1	-1
$v_2$	-1	1	0	0	0	0	0
$v_3$	0	-1	1	0	1	0	0
$v_4$	0	0	-1	-1	0	-1	0
$v_5$	0	0	0	1	-1	0	1

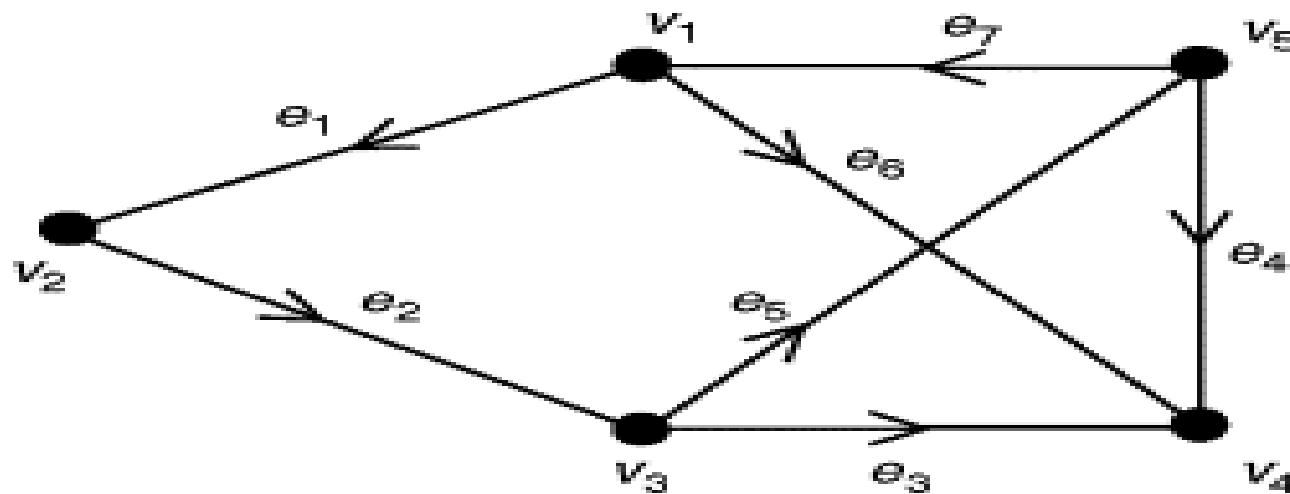

## Incidence Matrix





Draw the graph corresponding to the given incidence matrix

$$A = \begin{bmatrix} -1 & 0 & 0 & 0 & +1 & 0 & +1 & 0 \\ 0 & -1 & 0 & 0 & 0 & 0 & -1 & +1 \\ 0 & 0 & -1 & -1 & 0 & -1 & 0 & -1 \\ 0 & 0 & 0 & 0 & -1 & +1 & 0 & 0 \\ +1 & +1 & +1 & +1 & 0 & 0 & 0 & 0 \end{bmatrix}$$
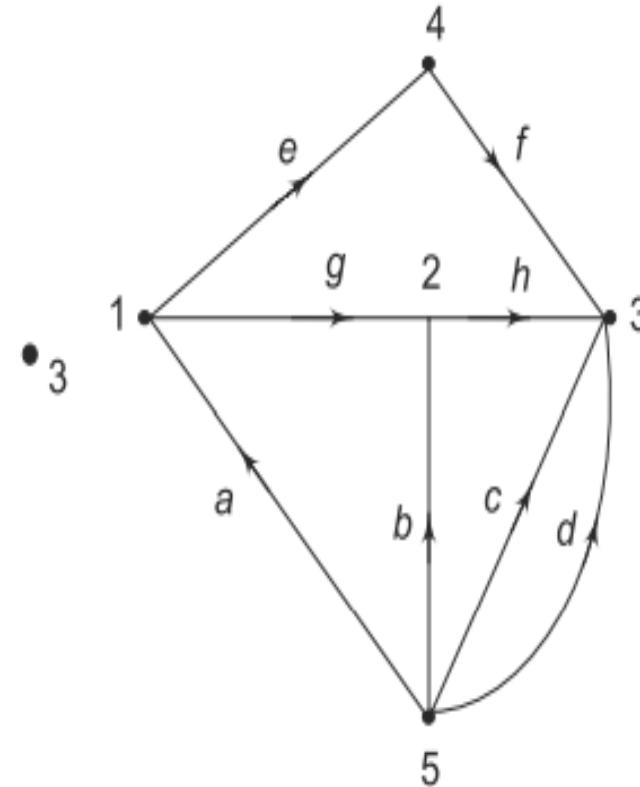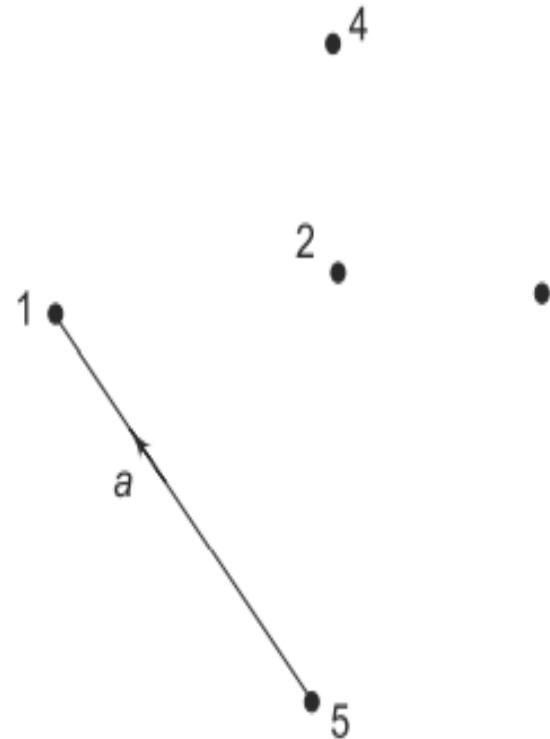
# Incidence Matrix



$$A = \begin{bmatrix} & a & b & c & d & e & f & g & h \\ 1 & -1 & 0 & 0 & 0 & 1 & 0 & 1 & 0 \\ 2 & 0 & -1 & 0 & 0 & 0 & 0 & -1 & 1 \\ 3 & 0 & 0 & -1 & -1 & 0 & -1 & 0 & -1 \\ 4 & 0 & 0 & 0 & 0 & -1 & 1 & 0 & 0 \\ 5 & 1 & 1 & 1 & 1 & 0 & 0 & 0 & 0 \end{bmatrix}$$



## Incidence Matrix





In the matrix  $A$  with  $n$  rows and  $b$  columns, an entry  $a_{ij}$  in the  $i$ th row and  $j$ th column has the following values.

$a_{ij} = 1$ , if the  $j$ th branch is incident to and oriented away from the  $i$ th node.

$a_{ij} = -1$ , if the  $j$ th branch is incident to and oriented towards the  $i$ th node.

$a_{ij} = 0$ , if the  $j$ th branch is not incident to the  $i$ th node.

# Incidence Matrix

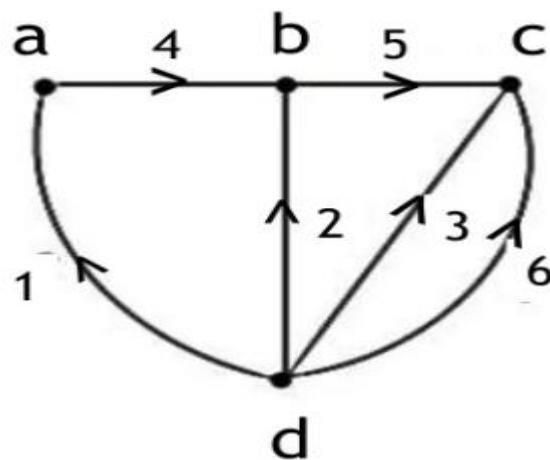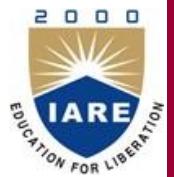

Complete Incident Matrix ( $A_a$ )


Nodes ↓	Branches →					
	1	2	3	4	5	6
a	-1	0	0	1	0	0
b	0	-1	0	-1	1	0
c	0	0	-1	0	-1	-1
d	1	1	1	0	0	1

Incident Matrix (A)

Nodes ↓	Branches →					
	1	2	3	4	5	6
a	1	-1	0	1	0	0
b	0	-1	0	-1	1	0
c	1	1	1	0	0	1

# Tie set Matrix

## Tie set Matrix (B)

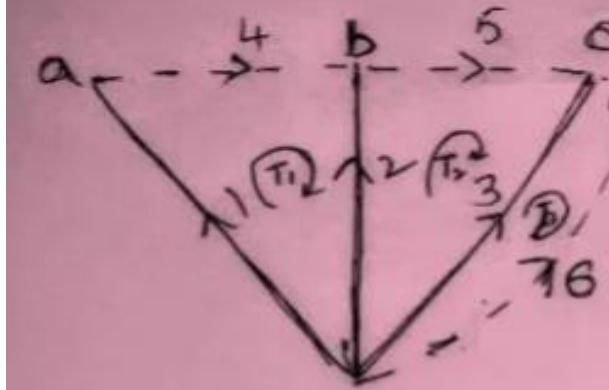


Tie set Matrix

$$B =$$

	Tie sets \ Branches $\rightarrow$					
	1	2	3	4	5	6
I	1	-1	0	1	0	0
II	0	+1	-1	0	1	0
III	0	0	-1	0	0	1

## Cut set Matrix (Q)

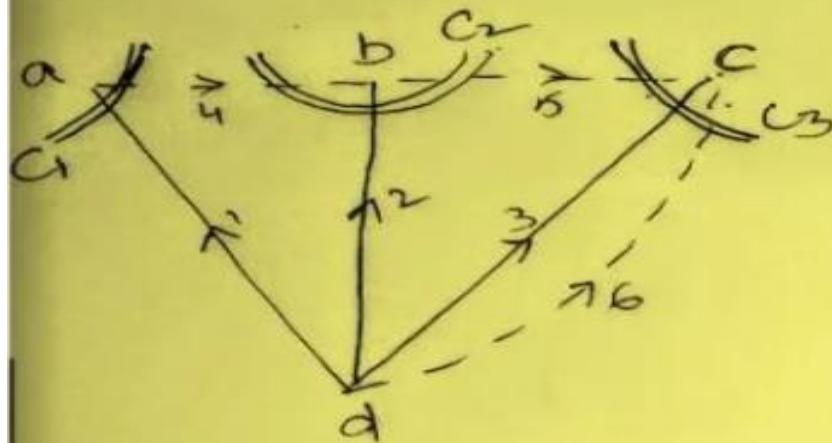

Cut Set Matrix




$$Q =$$

	Cut sets \ Branches $\rightarrow$					
	1	2	3	4	5	6
C1	1	0	0	-1	0	0
C2	0	1	0	+1	-1	0
C3	0	0	1	0	1	1


# Tree and Twigs of graph

Electrical Network


(Q.)

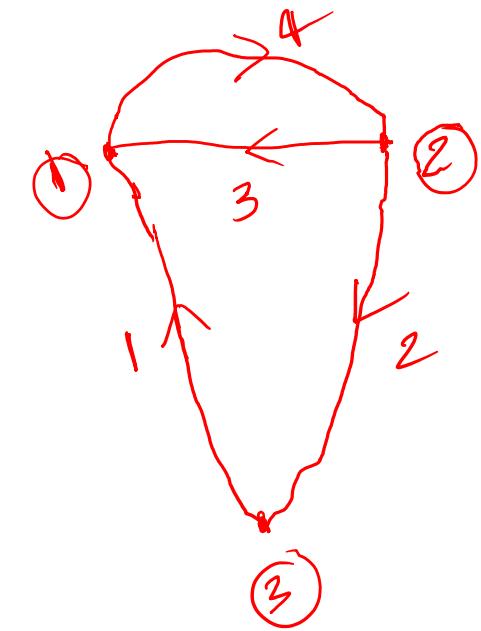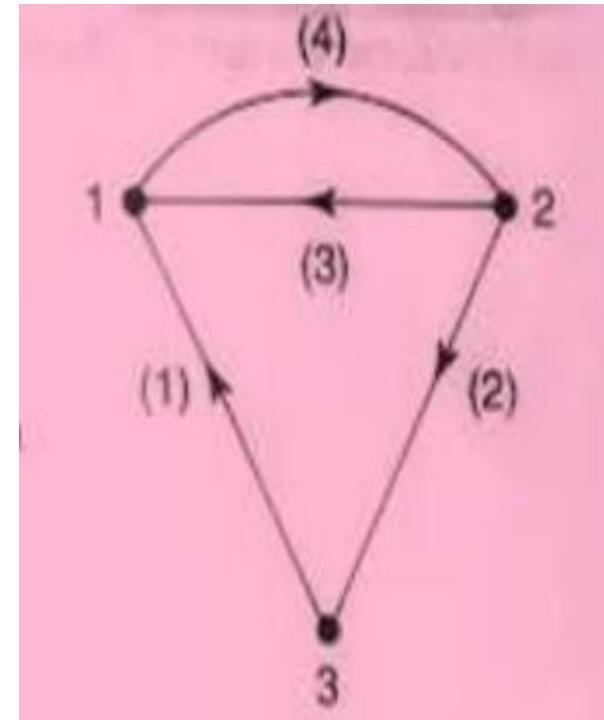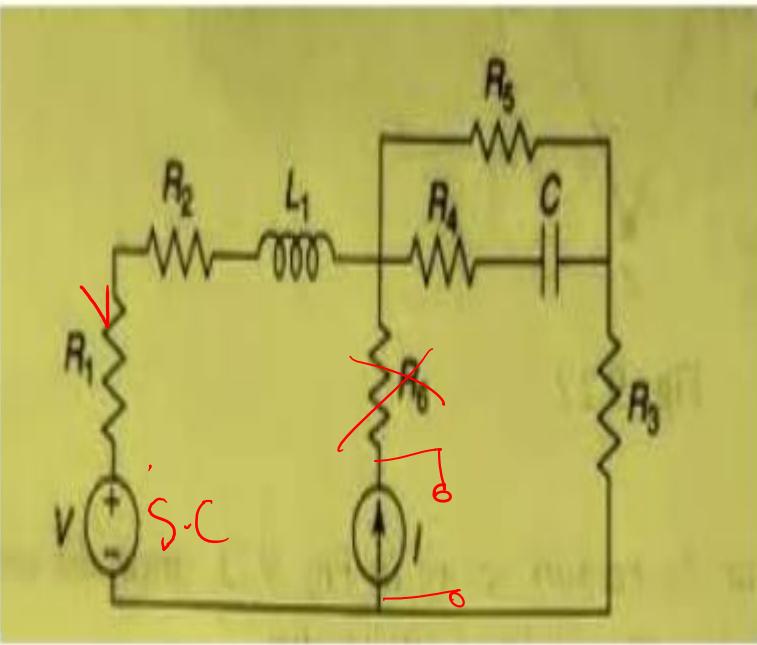

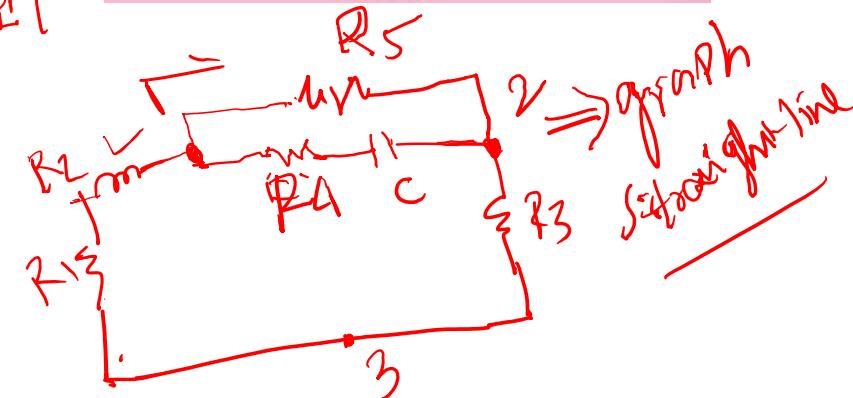- Draw the graph
- Draw oriented or directed graph
- Voltage → +
- Current → +
- Shorted → open



# Tree and Twigs of graph

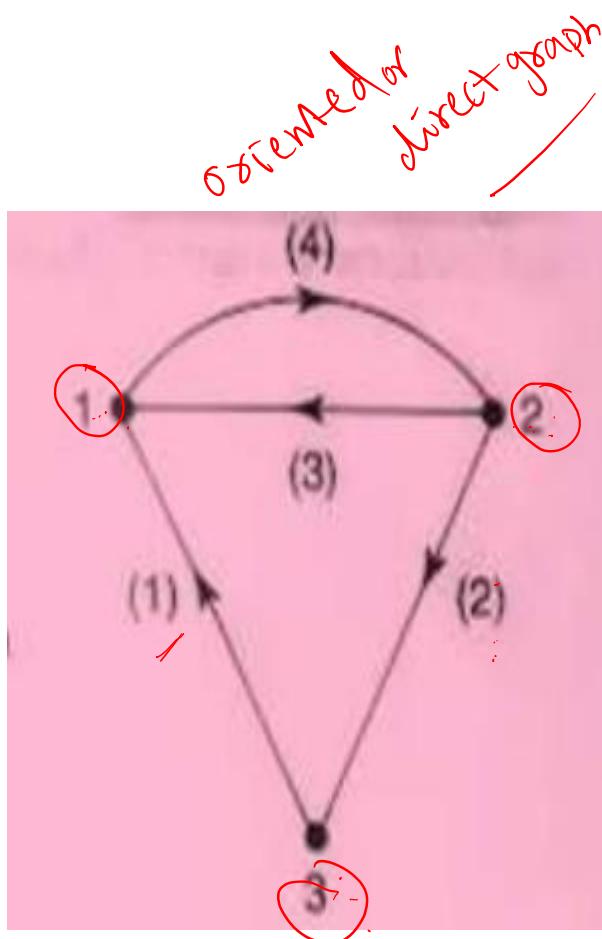

→ Incidence Matrix

(a) Incidence Matrix ( $A$ )

Nodes ↓	Branches →			
	1	2	3	4
1	-1	0	-1	1
2	0	1	1	-1
3	1	-1	0	0


$$A_d = \begin{bmatrix} -1 & 0 & -1 & 1 \\ 0 & 1 & 1 & -1 \\ 1 & -1 & 0 & 0 \end{bmatrix}$$

Eliminating the third row from the matrix  $A_d$ , we get the incidence matrix  $A$ .

$$A = \begin{bmatrix} -1 & 0 & -1 & 1 \\ 0 & 1 & 1 & -1 \end{bmatrix}$$



Reduced incident  
matrix

# Tree and Twigs of graph

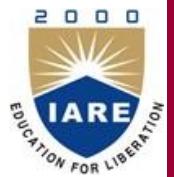

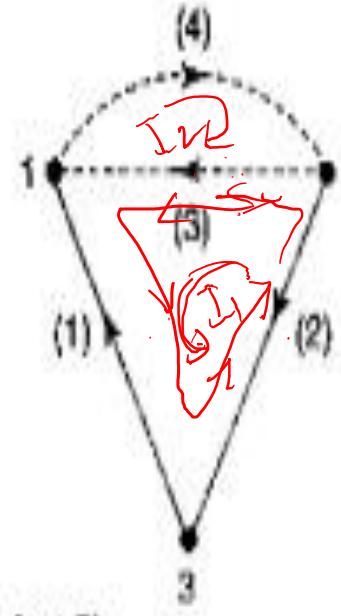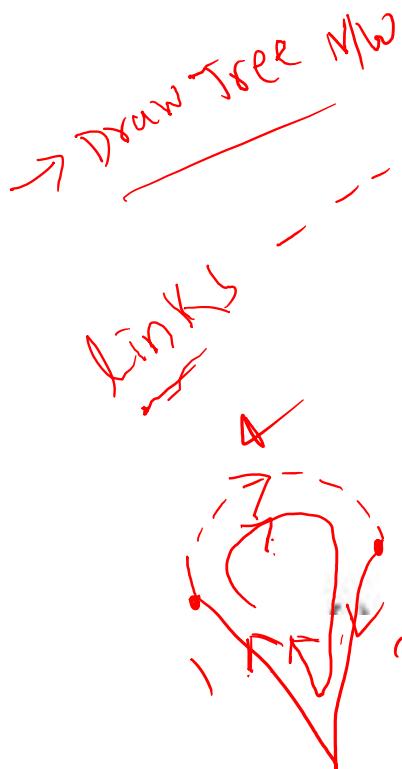
## (b) Tieset Matrix ( $B$ )

The oriented graph, selected tree and tiesets are shown in Fig. 9.21.



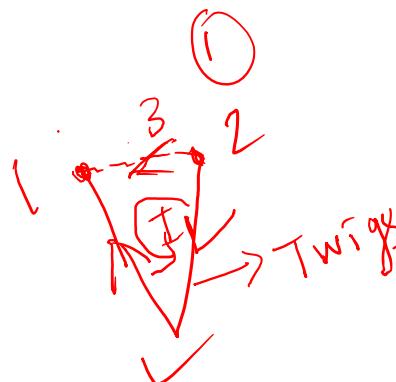Links:  $\{3, 4\}$   
Tieset 3:  $\{3, 1, 2\}$   
Tieset 4:  $\{4, 1, 2\}$



$$B = \begin{bmatrix} 1 & 2 & 3 & 4 \\ -1 & -1 & 1 & 0 \\ 1 & 1 & 0 & 1 \end{bmatrix}$$




①  
 $b = n + 1$

# Tree and Twigs of graph



(b) Tieset Matrix ( $B$ )

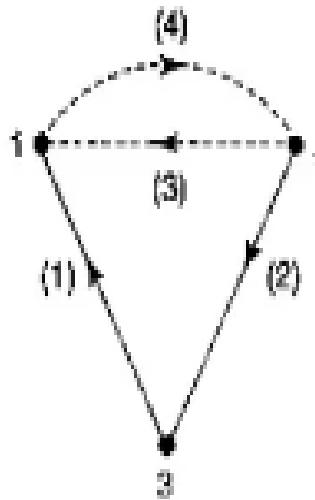

Links: {3, 4}  
Tieset 3: {3, 1, 2}  
Tieset 4: {4, 1, 2}



$$B = \begin{bmatrix} 1 & 2 & 3 & 4 \\ 3 & -1 & -1 & 1 \\ 4 & 1 & 0 & 1 \end{bmatrix}$$

# Tree and Twigs of graph




Cut set matrix

(c)  $f$ -cutset Matrix ( $Q$ )

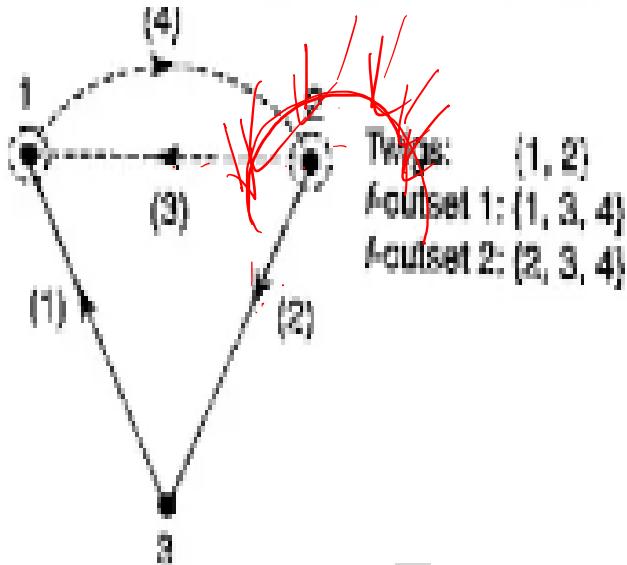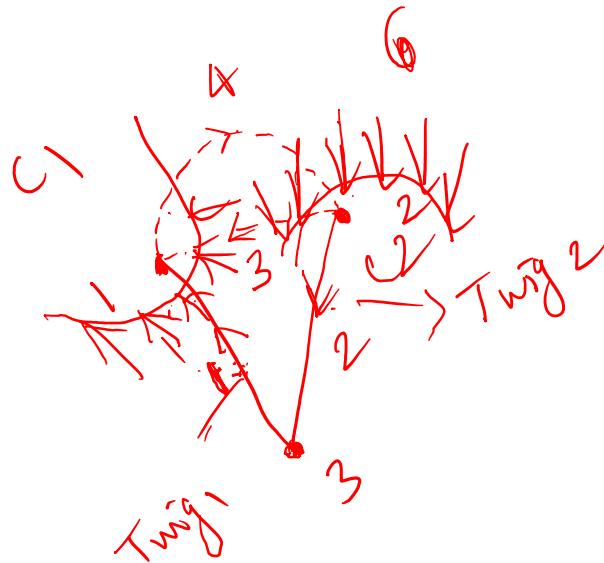


$$Q = \begin{bmatrix} \text{Cutset 1} \\ 1 & 2 & 3 & 4 \\ \text{Cutset 2} \\ 2 & 0 & 1 & -1 \\ 0 & 1 & -1 & +1 \end{bmatrix}$$

## Tree and Twigs of graph

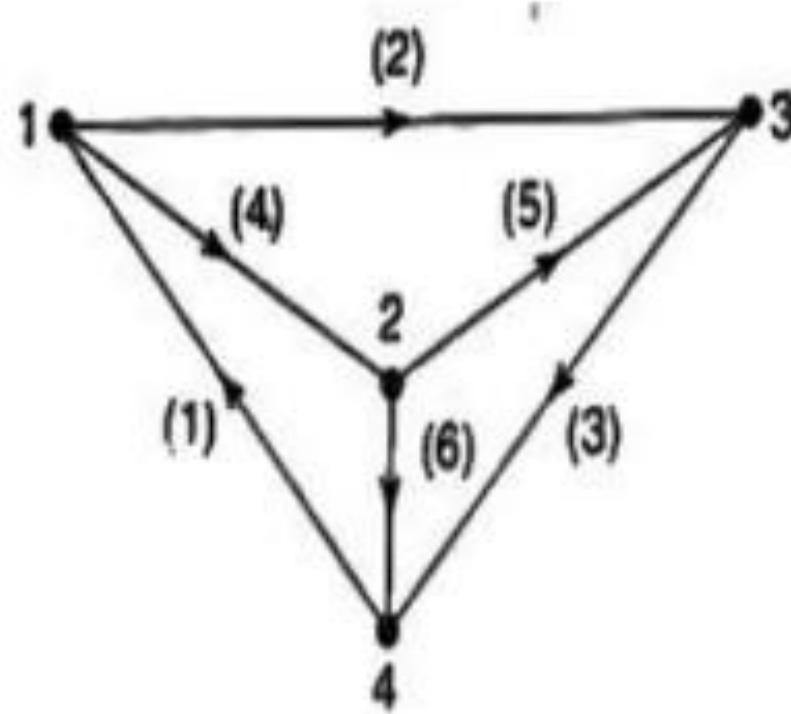

# Tree and Twigs of graph

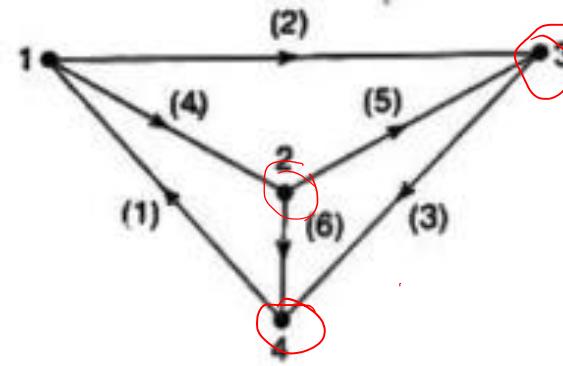

(a) Incidence Matrix ( $A$ )

*Nodes*                    *Branches*

$$A_a = \begin{bmatrix} -1 & 1 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & -1 & 1 & 1 \\ 0 & -1 & 1 & 0 & -1 & 0 \\ 1 & 0 & -1 & 0 & 0 & -1 \end{bmatrix}$$

The incidence matrix  $A$  is obtained by eliminating any row from the matrix  $A_a$ .

$$A = \begin{bmatrix} -1 & 1 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & -1 & 1 & 1 \\ 0 & -1 & 1 & 0 & -1 & 0 \end{bmatrix}$$

*Reduced incidence matrix*

# Tree and Twigs of graph


link 2  
twigs 5 & 6

(b) Tieset, Matrix ( $B$ )

The oriented graph, selected tree and tiesets are shown in Fig

1) Draw the Tree

Link 1, 4 & 5  
6th twig  
1, 2 & 3

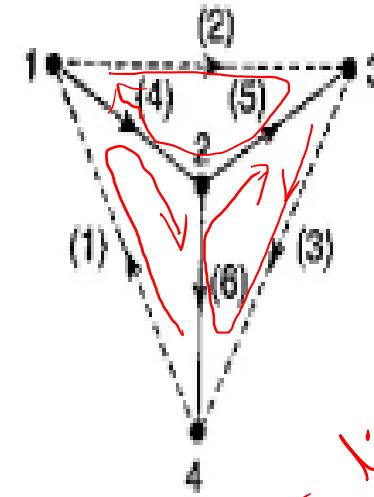


Links:  $\{1, 2, 3\}$   
Tieset 1:  $\{1, 4, 6\}$   
Tieset 2:  $\{2, 4, 5\}$   
Tieset 3:  $\{3, 5, 6\}$

Tieset 3, 5 & 6 twigs

branches


$$B = \begin{bmatrix} 1 & 0 & 0 & 1 & 0 & 1 \\ 0 & 1 & 0 & -1 & -1 & 0 \\ 0 & 0 & 1 & 0 & 1 & -1 \end{bmatrix}$$

# Tree and Twigs of graph

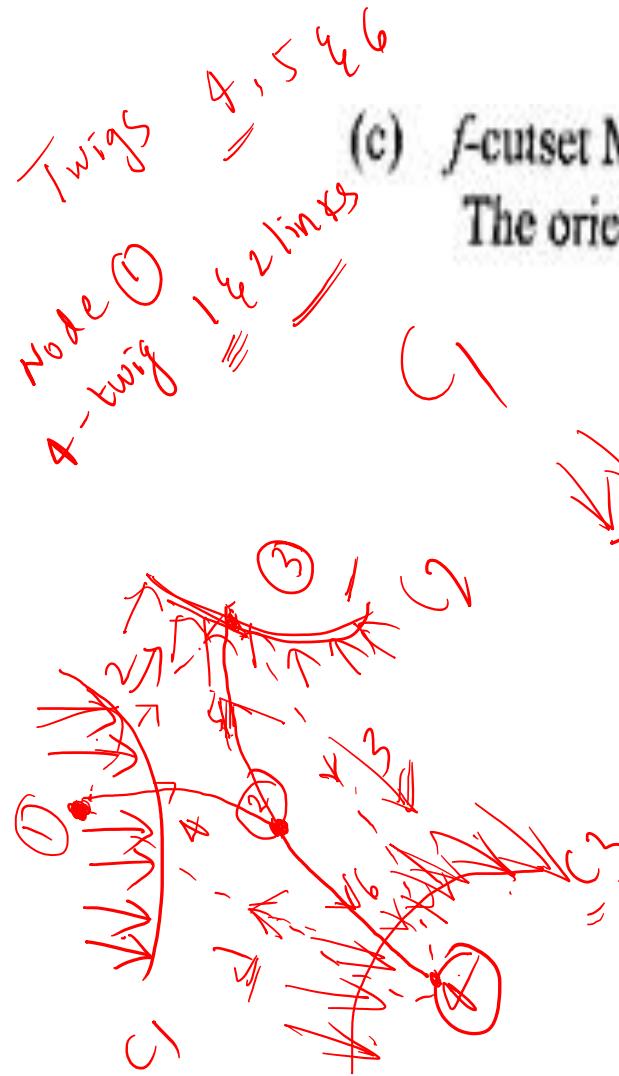

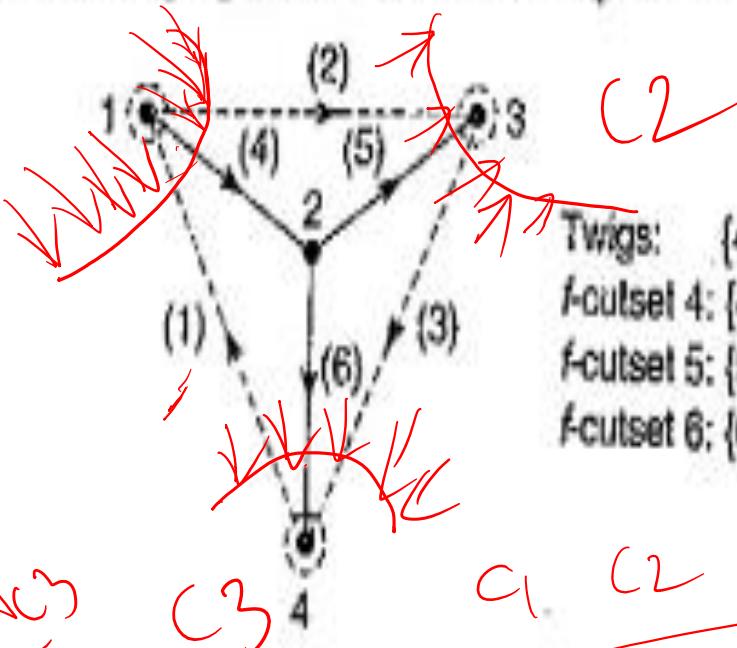(c)  $f$ -cutset Matrix ( $Q$ )

The oriented graph, selected tree and  $f$ -cutsets are shown in Fig.



Twigs:  $\{4, 5, 6\}$   
 $f$ -cutset 4:  $\{4, 1, 2\}$   
 $f$ -cutset 5:  $\{5, 2, 3\}$   
 $f$ -cutset 6:  $\{6, 1, 3\}$

$C_1 \quad C_2 \quad C_3$   
 Node 4  
 $\{1, 3, 4, 6\}$

$$Q = \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 \\ 4 & -1 & 1 & 0 & 1 & 0 \\ 5 & 0 & 1 & -1 & 0 & 1 \\ 6 & -1 & 0 & 1 & 0 & 0 \end{bmatrix}$$

*Branches*

# Tree and Twigs of graph

