

PART-A:-

1) Define the potential difference.

Potential difference is the different in the amount of energy that charge carriers have between two points in a circuit. The potential difference is measured in volts and is also called as voltage. We use a device named as voltmeter to measure potential difference.

2) Define Current.

An electric current is a stream of charged particle, such as electrons or ions, moving through an electric conductor or space. It is measured as the net rate of flow of electric charge through a surface or into a confined volume. Current is measured in amperes.

3) Write the expression for voltage in terms of C & Q.

The formula is ohm's law" for capacitors. Here C is no. of specific to capacitor, Q is the charge & V is voltage across across the capacitor

$$Q = CV$$

$$\text{or } V = \frac{Q}{C}$$

4) State Ohm's Law.

Ohm's law states that Current through a conductor between two points is directly proportional to the potential difference across two points. Introducing the constant of proportionality, the resistance, one arrives at the usual mathematical expression that describes the relationship: $I = V/R$.

5) State Kirchhoff's Law

There are basically two Kirchhoff's laws.

→ Kirchoff's Current Law:- Also called as KCL or Kirchhoff's first law and it states that the



total current in a closed circuit, the entering current at node is equal to the current leaving at the node or the algebraic sum of current at node is electronic circuit is equal to zero.

→ Kirchoff's Voltage Law:- KVL or Kirchhoff's 2nd law

states that the algebraic sum of voltage in a closed circuit is equal to zero or the algebraic sum of voltage at node is equal to zero. Hence the sum of voltage difference across all the elements in the circuit is always zero.

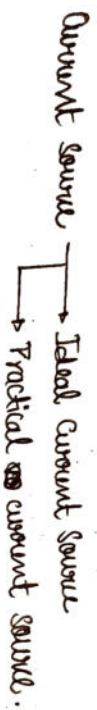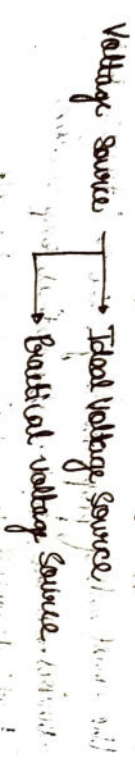
6) Compare between practical sources and ideal sources

Ans:- The various type of voltage sources available in electric network are voltage source & current sources. They are further divided into two types:-



A voltage source is a two terminal circuit, whose voltage at any instant of time is constant & is independent of the current drawn from it. Such voltage source is called as Ideal voltage source and have zero internal resistance.

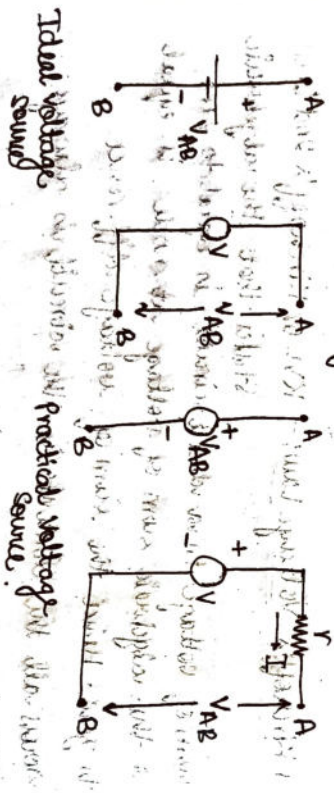Source having some amount of internal resistances are known as Practical Voltage Source.




An ideal current source is a two terminal circuit element which supplies the same current to any load resistance connected across the terminals.

A practical current source is represented as an ideal current source connected with resistance in parallel.


Ideal current source



Practical current source.

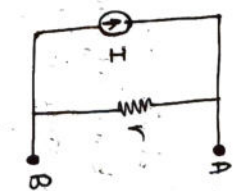

Ideal current source

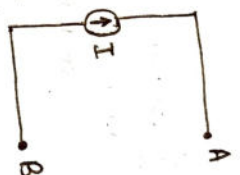


7) Explain with dependent diagrams of dependent sources

• Dependent Voltage Source:- Unlike ideal voltage source that produces a constant voltage across its terminals regardless of what is connected to it, a dependent voltage source changes its terminal voltage depending upon the voltage across or the current through, some other element connected to the circuit. It is sometimes difficult to specify the value of a dependent voltage source, unless you know the actual value of voltage or current on which it depends.

A voltage source that depends on voltage input is referred to as Voltage controlled Voltage source or VCVS. A voltage source that depends on current input is referred to as Voltage controlled Current source or VCCS.

VCVS, VCCS

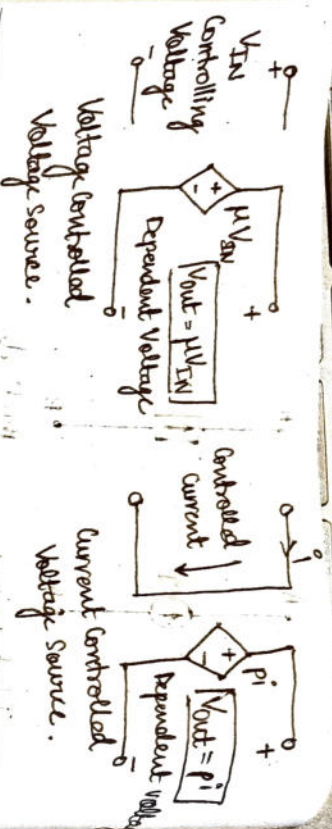

8) State two salient points of a series combination of resistors.

Ans:- In series combination the equivalent resistance is increased because of each resistance added. To increase resistance the resistors must be connected in series.
In series the potential difference was shared at different points.

9) Define Ideal Voltage Source & Current source.

Ideal Voltage Source:- An ideal voltage source is defined as a two-terminal active element that is capable of supplying and maintaining the same voltage across its terminal regardless of the current flowing through it. An ideal voltage source will supply a constant voltage at all times regardless of the value of the current being supplied producing an I-V characteristic represented by a straight line.

Ideal Current Source:- An ideal current source is a constant current source that supplies constant current to a circuit despite any other condition present in the circuit. An ideal current source provides a constant current with 100% efficiency.

10) Write the expression of energy stored in a inductor and capacitor.

For an inductor, the output is magnetic field. The energy stored by an inductor is equal to the work needed to produce a current through the inductor. The formula for energy is given as:

$$E = \frac{1}{2} L I^2$$

Inductance
(unit - Henry)

↘ current (unit - Ampere).

For a capacitor, if q is charge & C is capacitance and V is potential difference then

$$q = CV$$

$$dw = V dq = \frac{q}{C} dq$$

$$w = \int_0^q \frac{q}{C} dq = \frac{1}{C} \frac{q^2}{2} = \frac{1}{2} \frac{q^2}{C}$$

$$V = \frac{1}{2} \frac{q^2}{C} \quad [q = CV]$$

$$V = \frac{1}{2} CV^2 \rightarrow \text{potential difference}$$

$$\downarrow \text{capacitance}$$

Energy stored in capacitor.

11) State sum current point of parallel connections of resistor.

Ans:- The potential diff across each resistor is same which is equal to the potential difference across each terminal of the battery.

- The current in the resistor is inversely proportional to the resistance. The sum of currents in separate branches of the parallel circuit drawn from the sources i.e.,

$$I = I_1 + I_2 + I_3 + \dots$$

12) Write properties of inductor.

- Inductors store kinetic energy in the form of magnetic energy. The formula for energy stored in the magnetic field is equal to $E = \frac{1}{2} L I^2$, where L is inductance and I is current.

- Inductors allow only direct current (DC) to pass through it while blocking the AC. These types of inductors are called chokes.

- Inductors consume reactive power from the power source.
- In a pure inductive circuit, the circuit voltage lags behind voltage by 90° .
- Inductors oppose current change for alternating current.

13) Write properties of capacitor.

- Working Voltage:- This is one of the important properties of capacitor which is defined as the maximum continuous voltage that can be applied to a capacitor with before capacitor fails.

→ Tolerance:- Tolerance of a capacitor is determined with plus or minus values. These values are used for supervising the voltage percentage of a capacitor with higher value.

→ Working Temperature:- As the dielectric property changes, there will be change in temperature which impacts the capacitance value. The working temperature of capacitor is between -30°C to $+125^\circ\text{C}$.

→ Temperature Coefficient:- Temp coeff of capacitor is determined by calculating the maximum change in capacitance for specific temperature range.

Q14) State limitation of Ohm's law.

Ans:- The limitation of Ohm's law are explained below:-

1. This law cannot be applied to unilateral networks like diode, transistors, etc., which don't have same voltage current relation for both direction of current.
2. Ohm's law is not applicable for non-linear elements.

Q.15] Define conductance and state its units?

When voltage is applied to a piece of metal wire, the current flowing through the wire is proportional to the voltage V across two points in the wire. This property is known as

$$\text{Ohm's law: where } V = IR \quad \text{or } I = CV$$

where R is the Resistance and G is called Conductance.

The resistance R and conductance G of the same piece of wire is related by $R = 1/G$. Resistance is measured in ohms Ω and conductance is measured in Siemens (S).

When voltage is applied to a piece of metal wire, the current flowing through the wire is proportional to the voltage across two points in the wire. This property is known as Ohm's law, where $V = IR$ or $I = \frac{V}{R}$ where R is the resistance and G is called conductance. The resistance R and conductance G of the same piece of wire is related by $R = 1/G$. Resistance is measured in ohms Ω and conductance is measured in siemens (S).

PART-B:-

(1) Differentiate resistors, inductors and capacitor elements using their voltage current characteristics.

Ans:- When voltage is applied to a piece of metal wire, the current I flowing through the wire is proportional to the voltage V across two points in the wire. This proportionality is known as Ohm's law, which reads

$$V = IR \text{ or } I = \frac{V}{R} = GV$$

Here Resistance = $\frac{V}{I} \rightarrow$ Voltage
 $I \rightarrow$ current

Resistance R Resistor is directly proportional to length l inversely proportional to area.

The power can be expressed as follows

$$P = VI$$

$$P = V \times \frac{V}{R} = \frac{V^2}{R} = CR^2 = I^2 R$$

If a changing flux is linked with a coil of conductors there would be an emf induced in it. The property of the coil of inducing emf due to changing flux is known as inductance of the coil. Due to this property all electrical coil can be regarded as inductor.

Ohm's law for inductor is

$$V = L \frac{di}{dt}$$

where $V \rightarrow$ instantaneous voltage across the inductor.

$L \rightarrow$ inductance in Henry.

$\frac{di}{dt} \rightarrow$ instantaneous rate of current change (amps per second).

The capacitor is the component which has the ability to "store" energy in the form of an electrical charge producing potential difference across its plates, much like a small rechargeable battery.

Ohm's law for capacitor is

$$i = C \frac{dV}{dt}$$

where $i \rightarrow$ instantaneous current through capacitor.



$C \rightarrow$ capacitance in farads

$\frac{dV}{dt} \rightarrow$ instantaneous rate of voltage change (volt per second).

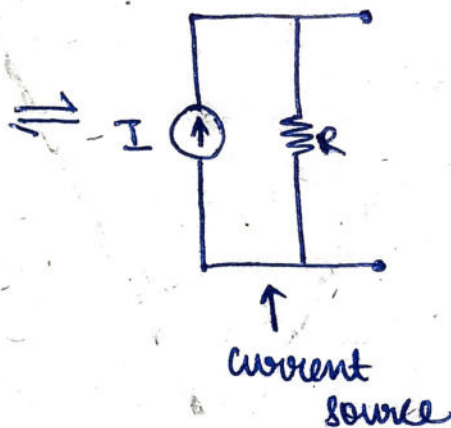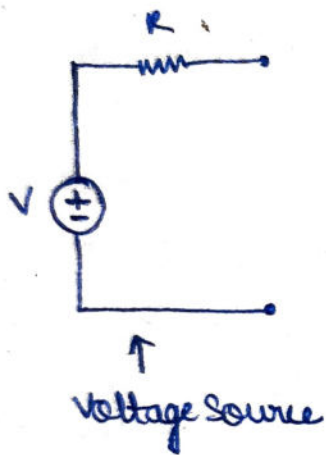2) Deduce the condition for source transformation and deduce one type of source from the other.



The condition for source transformation is that the voltage source should be in series with the resistor and the current source is required to be connected with a resistor parallel to the current source.

Source transformation for deducing current source from voltage source.



The current I is calculated by $\frac{V}{R}$.

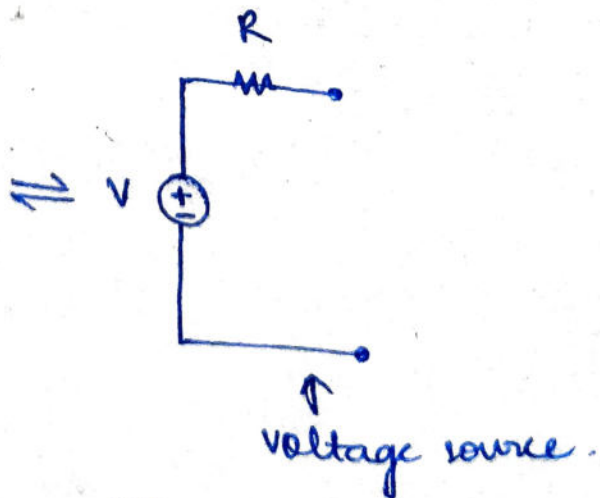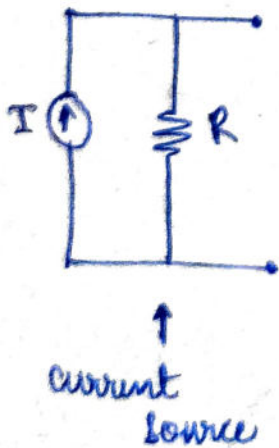Source transformation for deducing voltage source from that of current source.



The value of voltage V can be calculated by the formula

$$V = IR.$$

(4) Classify types of elements in electric circuit depending on characteristics and explain in detail.

• Active element:- An element capable of delivering power to some other devices or elements in the network.

Eg:- Energy sources.

• Passive element:- Element that are capable of absorbing power.

Eg:- Resistor, capacitors, inductors.

• Unilateral elements:- V-I relationship is different for two possible directions of current flow or

These elements will allow current to flow only in one direction in any circuit.

Eg:- Diode.

• Bilateral elements:- V-I relationship is same for either direction of current.

Eg:- High conductivity materials, Resistor.

• Linear elements:- The V-I characteristics is all the time a straight line passing through the origin.

• Linear networks satisfy the principle of superposition & homogeneity.

Eg:- Resistor.

• Non-linear elements:- The element which does not satisfy superposition principle or V-I characteristics are non-linear.

Eg:- Diode.

• Lumped Parameter:- Elements are small in size compared to the wavelength of applied signal.

Eg:- Resistor, capacitors, inductors.

• Distributed elements:- Elements can't be separated by electrically for analytical purpose.

Eg:- Transmission lines.

Q3 Distinguish b/w ideal & practical current sources.

• Ideal Voltage Source:- There is no resistance from the source and provide constant voltage independent of current type. Doesn't exist practically.

• Practical Voltage Source:- The source has some resistance & can't provide constant voltage for any load and can't provide unlimited current to load. It exists practically.

• Ideal current source:- An imaginary current source that provides constant current to any load ranging from zero to infinity. Current provided is independent of voltage.

• Practical current source:- Practical current source has some internal resistance and some of the current flows through it & the amount of flow depends upon the load.

Q4 State Ohm's law and give its applicability and electrical network. Explain conservation of current direction and voltage across an element.

• STATEMENT:- At constant temperature, the voltage across the terminal of conductors is proportional to the current flowing through it.

$$V \propto I$$

$$V = IR$$

R = Constant of proportionality known as resistance.

→ Applications:-

• Conventional use domestic fan regulator one way common devices where the current through the fan get regulated by controlling the resistance of the regulator circuit.

• In voltage divider circuit this law is used to divide source voltage across output resistance.

• In electronic circuit, there are many applications where intentional voltage drop is assigned to supply specific voltage across different elements.

• In dc ammeter and other dc measuring instruments shift is used to divert current.


$I_A = 1$ \rightarrow $\frac{1}{100\Omega}$ \rightarrow Then the sign convention is taken to be +ve so the value of V will be $100V$.

But $I = 1A$ \rightarrow $\frac{1}{100\Omega}$ \rightarrow Then the sign convention is taken to be -ve so we get the value of V to be $-100V$.

This shows that we have taken the polarity in opposite direction.

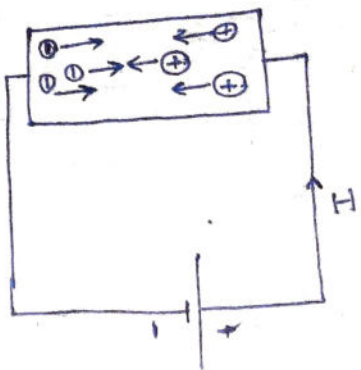(Q7) Write the convention to study any electrical circuit;

• Current flow:- The current flow is always taken in the direction of the charge movement, i.e., from the terminal to -ve terminal of the circuit.




Direction of current flow:- If a current with the charge is flowing in one direction then the same magnitude of current with negative charge will flow in the opposite direction.




Voltage polarity:- The higher potential value of voltage is accompanied with the terminal & the other with -ve terminal.

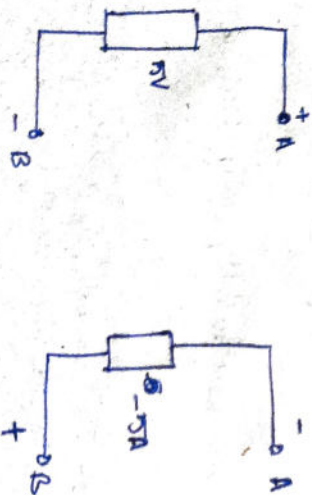Voltage drop from A to B is ~~equivalent~~ equivalent to voltage drop from B to A.



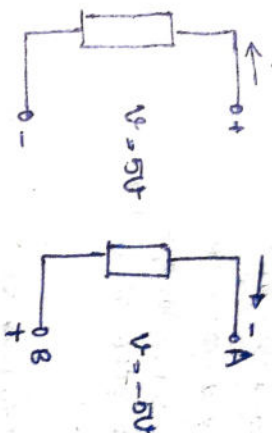Power absorbed / delivered:- The power delivered to an element is denoted by +ve sign whereas power by an element is denoted as negative sign.



(Q8) Define the term voltage, current, power, energy, work and degree of node.

→ Voltage:- Also called as electromotive force, it is a quantitative expression of potential difference in charge b/w two points in an electric field. Voltage is measured in volts & is measured by letter "V".

→ Current:- A flow of electricity that results from the ordered directional movement of electrically charged particle.

→ Power:- The rate at which the work is being done in an electrical circuit is called its power. The electric power is equal to rate of the transfer of energy.

→ Energy:- ~~The ability to do work~~ the energy derived from the potential or kinetic energy of the charged particle.

Q9). Define the term peak, peak to peak, average, RMS value, peak factor and form factor of sine wave.

→ Peak :- The maximum value attained by an alternating quantity during one cycle is called peak value. It's also known as maximum value or amplitude or crest value. The sinusoidal alternating quantity obtains its peak value at 90° degrees.

→ Peak to Peak :- Peak to peak value is the maximum voltage change during one cycle of alternating voltage or current. Also defined as the difference between positive peak and negative peak in A.C.

→ Average :- It is defined as "the average of all instantaneous values during one alternation". The ratio of the sum of all considered instantaneous values to the no of instantaneous values in one alternative alternation period.

→ RMS Value :- The "Root Mean Square" is the square root of the sum of squares of means of an alternating quantity.

→ Peak factor :- The ratio of max. value of the RMS value of an alternating current. For a sine wave it is 1.41.

→ Form factor :- ~~The ratio b/w the average value & the RMS~~ (of sine wave) used to describe the physical sig & shape. The form factor of sine wave is 1.11.

Q10). Derive the expression for average & rms value of sine wave.

Ans :- For a sine wave

Avg value = $0.637 \times$ Maximum value

rms value = $0.707 \times$ Maximum value.

Form factor = 1.11

Peak factor = 1.41

$$V_{avg} = \frac{1}{T} \int_0^T V_m \sin \omega t \, dt$$

$$V_{avg} = \frac{1}{T} \int_0^T V_m \sin \omega t \, dt = \frac{2V_m}{\pi}$$

$$V_{avg} = 0.637 V_m.$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V(t)^2 d(\omega t)}$$

$$= \sqrt{\frac{1}{T} \int_0^T (V_m \sin \omega t)^2 d(\omega t)}$$

$$= \sqrt{\frac{1}{T} \int_0^T (V_m^2) \left(\frac{1 - \cos 2\omega t}{2} \right) d(\omega t)}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} = 0.707 V_m.$$

Q11) Discuss the concept of Reactance and impedance offered by R, L, C parameters.

Reactance is ~~not~~ measured in Ohm's but is given the symbol "X" to distinguish from pure resistive 'R' value.

Inductor reactance is denoted as (X_L) measured in ohms

As the capacitor charges or discharges, a current flows through it which is restricted by internal impedance of the capacitor. This internal impedance is commonly known as capacitive reactance and symbol is (X_C) in ohm.

The impedance is defined as the ratio of sinusoidal voltage to the ~~same~~ sinusoidal current. Also defined as total opposition offered to the flow of sinusoidal current. Pure impedance is measured in ohms.

The real part of the impedance is resistance and imaginary part is reactance.

$$X_L = Z \sin \phi$$

The series RL circuit.

$$Z = R + jX_L = Z(\cos \phi + j \sin \phi)$$


$$Z = |Z| \angle \phi$$

$$|Z| = \sqrt{R^2 + X_L^2} \quad \phi = \tan^{-1} \left(\frac{X_L}{R} \right)$$

$$Z = R - jX_C = |Z| \angle -\phi$$

$$|Z| = \sqrt{R^2 + X_C^2} \quad \phi = \tan^{-1} \left[\frac{-X_C}{R} \right]$$

$$X = X_L - X_C$$

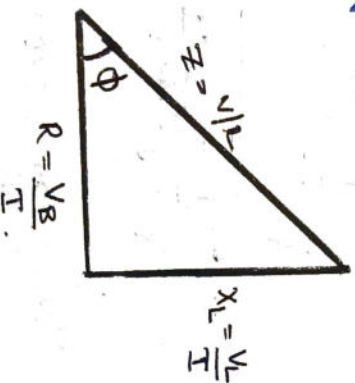

Q12) Explain the concept of susceptance and admittance offered by R, L, C ~~resist~~ parameters.

In parallel circuit the inverse of the parameters will be useful for analysis. The inverse of impedance is admittance. It is also defined as the ratio of sinusoidal current to voltage.

The general eq of admittance given by

$$Y = G + jB$$

$G \rightarrow$ conductance

$B \rightarrow$ susceptance

$$B = \frac{1}{X}$$

$$Y = \frac{1}{Z} = \frac{1}{R + jX} = \left(\frac{R}{R^2 + X^2} \right) + j \left(\frac{-X}{R^2 + X^2} \right)$$

and

$$B = \text{Im}(Y) = \frac{-X}{R^2 + X^2} = \frac{-X}{|Z|^2}$$


where

$$Y = G + j(B_L - B_C)$$

$$Y = \sqrt{G^2 + (B_L - B_C)^2}$$

$$Y = \frac{1}{Z}, \quad G = \frac{1}{R}$$

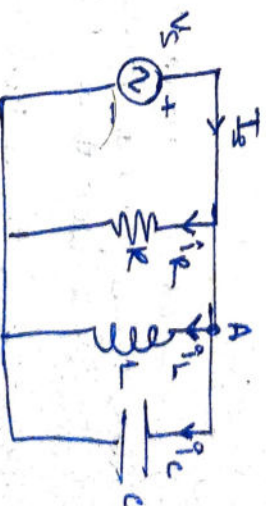
$$B_L = \frac{1}{\omega L}; \quad B_C = \omega C$$




3) Compute all types of solutions for two wave forms and write the relevant expressions.

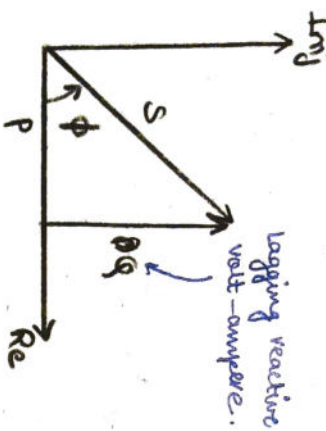14) Explain concept of active, reactive, apparent power and draw power triangle.

Power Δ^e is the representation of a right angle triangle showing the relation between active power, reactive power and apparent power. When each component of current i.e., active component ~~of the current~~ ($I \cos \phi$) or the reactive component ($I \sin \phi$) is multiplied by voltage V .



(i) lagging PF

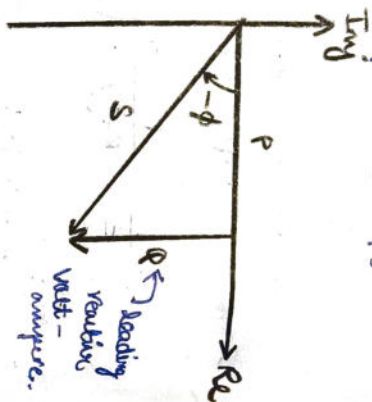

(ii) leading PF

The power which is consumed or utilized in an AC circuit is called True power or Active Power or real power. It is measured in kilowatt (or) kW.

The power which flows back and forth without means it never in both the directions in the circuit or watt upon it, it called Reactive Power. The reactive power is measured in kilovolt-ampere reactive (KVAR) or MVAR.


The product of root mean square (RMS) value of voltage & current is known as "Apparent Power". Measured in KVA or MVA.

15) (a) - relate the impedance triangle with power triangle and explain in detail.

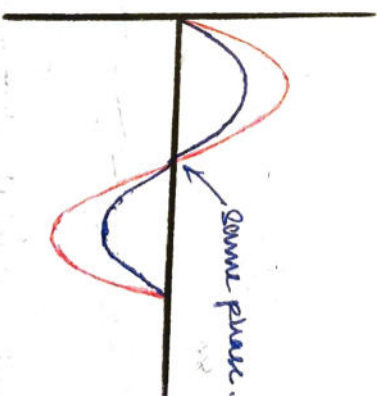
16) Explain the term phase, phase difference & phasor diagram with neat example.

→ Phase of wavefront :- The phase of an alternating quantity wave is defined as the divisional part of a cycle through which the quantity moves forward from a selected region.


When two quantities have the same frequency, and their maximum & minimum point occurs at the same point or else at some point, then the quantities are said to have in same phase.



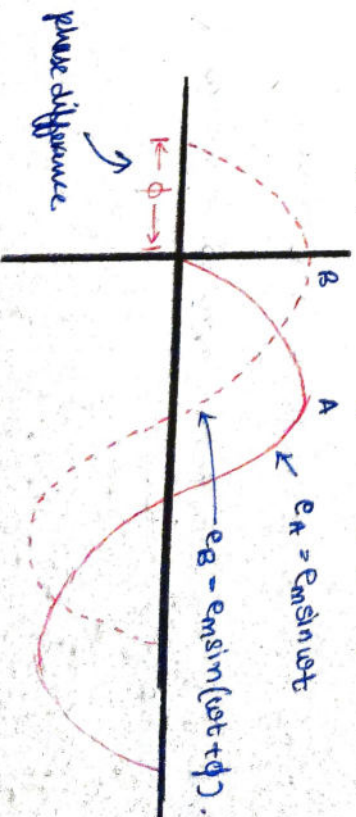→ Phase Difference :- The phase difference between the two electrical quantities is defined as the angular phase difference b/w the maximum possible value of two alternating quantities having same frequency.



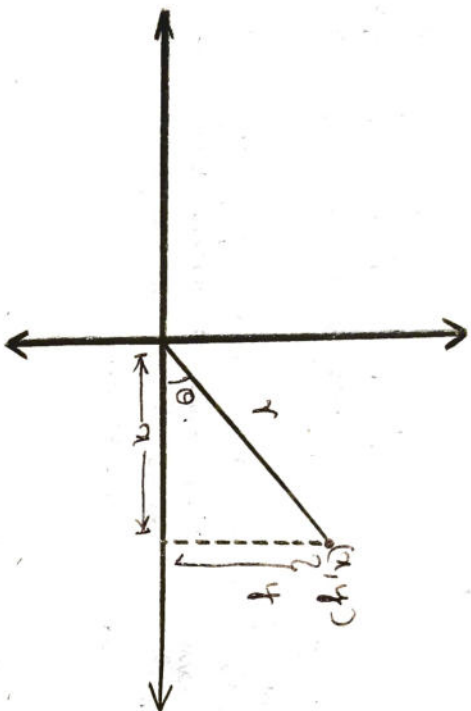→ Phasor diagram:- Sinusoids are easily expressed in terms of phasors, which are more convenient to the work with the sine and cosine function. Phasors in the complex form can be represented polar and rectangular form.



$$r = \sqrt{x^2 + y^2} ; \theta = \tan^{-1}\left(\frac{y}{x}\right)$$

$$x = r \cos \theta \text{ and } y = r \sin \theta$$

1. ~~Summarize the nature of power factor in inductive & capacitive circuit.~~

1.1) Summarize the feature of electrical network with DC and AC excitation.

1.2) Explain nature of power factor in inductive & capacitive circuits.

1.3) Derive expression for true power in AC circuits.

2.0) Derive the expression for reactance and impedance of inductor & capacitance.

2.1) An electrical heater draws 3.5A from a 110V source. The resistance of heating element is approximately.

According to Ohm's Law.

$$V = IR$$

↖ resistance

$$\text{So } R = \frac{V}{I}$$

$$R = \frac{110}{3.5} = 31.42 \Omega$$

2.3) A resistance is connected across 50V source.

What is current in the resistor if the colour code is red, orange, orange, silver.

$$R_{\text{red}} = 2$$

~~Orange~~

$$\text{Orange} = 3$$

$$\text{Silver} = 10^{-2}$$

$$\text{Tolerance} = \frac{\text{Silver}}{\text{resistor}} = 10\%$$

$$23 \times 10^3 \text{ or } 23 \text{ k}\Omega$$

$$V = IR$$

$$I = \frac{V}{R} = \frac{50}{23 \text{ k}\Omega} \approx 2.17 \text{ mA}$$